Name: _____ Page:1 EE411 – Summer 2008, Final Exam

Please, show all your work on the test sheets. A correct answer without supporting work gets no credit. One sheet of notes is permitted. You can also use your sheet of notes from tests #1 and #2. Write your name in all pages. Do not un-staple. You have 90 minutes to complete the test.

Problem 1 (30 points)

Consider the second order circuit in the figure and that the dc voltage source has been connected for a long time. Please answer the following questions:

- a) Write down the complete form of v(t) and i(t) from the time the switch is closed.
- b) Calculate the phasors V corresponding to v(t) and the phasor I corresponding to i(t) a long time after the switch was closed.
- c) Compare the answers for the two previous questions. What conclusions can you draw from the comparison?



 $i_{f}[t] = A_{3} s_{i}h_{2}t + A_{4} cos_{2}t, \frac{d^{2}i}{dt^{2}} + \frac{R}{L} \frac{di}{dt} + \frac{1}{Lc}i = -20 s_{i}h(2t)$ 0.1 -4 A3 SIN 2E - 4 A4 WSZE + 2 A3 WSZE - 2 A4SIN 2E + 0.1 A3 SIN 2E+ + 0.1 Ay cos2t = -20 Sh2t $\begin{cases} -4A_3 - 2A_4 + 0.1A_3 = -20 - \frac{3.9}{2} - \frac{3.9}{2$ $\Delta_3 = \frac{3.9}{2} \Delta_4 = 1.95 \Delta_7$ $-3.9 \cdot 1.950_{1} - 20_{4} = -10$ $A_{4} = \frac{20}{9.605} = 1.041$ $A_3 = 2.03$ $\dot{r}_{f}(t) = 2.03 \text{ sin } 2t + 1.041 \text{ cos } 2t = 2.28 \text{ cos}(2t - 62.85)$ (1) $i(t) = \Delta_1 e^{-0.887t} + \Delta_2 e^{-0.113t} + 2.28 \cos(2t - 62.85)$ $\dot{\kappa}(0) = 0 = \Delta_1 + \Delta_2 + 2.28 \cos(-62.85) = \Delta_1 + \Delta_2 + 1.041$ $N(0)=6 = 10 - V_{L}(0) - V_{R}(0) = 10 - Ldi - Ri = \frac{1}{40}$ $= 10 - 2(-0.887 A_1 - 0.113 A_2 + 4.055) - 2(A_1 + A_2 + 1.041) =$ G=- (2 x 2.20 xsin (-62.85))

 $6 = -0.226A_1 - 1.774A_2 - 0.192$

$$\begin{cases} -0.226A_{1} - 1.774A_{2} = 6.192 \\ A_{1} + A_{2} = -1.041 \\ A_{1} = 2.807 \\ A_{2} = -3.85 \end{cases}$$

$$\begin{aligned} \lambda : [4] = 2.87 e^{-0.884t} - 3.85 e^{-0.113t} + 2.28 \cos (2t - 62.85) \\ U(4) = \frac{1}{c} \int_{c}^{t} dt - 6 = \\ = \frac{1}{5} \left(\frac{2.607}{-0.884} e^{-0.884t} + \frac{3.85}{0.115} e^{-0.113t} + \frac{2.28}{2} \sin (2t + 62.85) \right)_{c}^{t} 6 = \\ = \frac{1}{5} \left(-3.165 e^{-0.884t} + \frac{3.85}{0.115} e^{-0.113t} + 4.14 \sin (2t + 62.85) \right)_{0}^{t} 6 = \\ \frac{14}{5} \left(-3.165 e^{-0.884t} + \frac{14.14}{2} \sin (2t - 62.85) + 0.228 \sin (2t - 62.85) \right)_{0}^{t} 6 = \\ \frac{14}{5} \left(-3.165 e^{-0.884t} + \frac{14.14}{2} \sin (2t - 62.85) + 0.228 \sin (2t - 62.85) \right)_{0}^{t} 6 = \\ \frac{14}{5} \left(-3.165 e^{-0.884t} + \frac{14.14}{2} \sin (2t - 62.85) + 0.228 \sin (2t - 62.85) \right)_{0}^{t} 6 = \\ \frac{15}{5} \left(-3.165 e^{-0.165t} + \frac{10.28}{2} \sin (2t - 62.85) + 0.228 \sin (2t - 62.85) \right)_{0}^{t} 6 = \\ \frac{15}{5} \left(-3.165 e^{-0.165t} + \frac{10.165}{5} + \frac{10.28}{5} \sin (2t - 62.85) \right)_{0}^{t} 6 = \\ \frac{15}{5} \left(-3.165 e^{-0.165t} + \frac{10.165}{5} + \frac{10.28}{5} \sin (2t - 62.85) \right)_{0}^{t} 6 = \\ \frac{15}{5} \left(-3.165 e^{-0.165t} + \frac{10.165}{5} + \frac{10.165}{5} + \frac{10.28}{5} \sin (2t - 62.85) \right)_{0}^{t} 6 = \\ \frac{15}{5} \left(-3.165 e^{-0.165t} + \frac{10.165}{5} \right)_{0}^{t} 6 = \\ \frac{15}{5} \left(-3.165 e^{-0.165t} + \frac{10.165}{5} + \frac{10.165}{5} + \frac{10.165}{5} + \frac{10.165}{5} + \frac{10.165}{5} \right)_{0}^{t} 6 = \\ \frac{15}{5} \left(-3.165 e^{-0.165t} + \frac{10.165}{5} +$$

EE411 – Summer 2008, Final Exam

Problem 2 (20 points)

For the circuit in the figure calculate.

- a) Active or reactive power of each of the passive elements as appropriate.
- b) Verify the conservation of both active and reactive power by calculating the complex power generated by the source.

You can assume that all voltages and currents are in rms values.



$$\omega = 2\pi f = 2.\pi 55 = 314.16$$

$$X_{c} = -\frac{1}{\omega c} = -\frac{1}{314.16475.10^{-5}} = -6.77$$

$$X_{L} = \omega L = 314.16 + 2.510^{-3} - 0.7855$$

$$\overline{E}_{1} = 1 + j 0.7854 = 1.27 (38.19)$$

$$\overline{E}_{2} = (j \times) / 2_{1} = \frac{1}{\frac{1}{1.27(38.19)}} = 1.418 (28.65)$$

 $Z_T = 2(0 + 1.418)(28.65 = 3.3)(11.84)$

$$\overline{U} = \frac{2200}{3.31(11.84)} = 66.35(-11.84)$$

 $\begin{aligned} \Re_{2} &= 2 \, \mathbb{I}^{2} = 2 \, \left(66.35 \right)^{2} = 8804.64 \ \omega \\ &\mathbb{Q}_{c} = \frac{\sqrt{a^{2}}}{\varkappa_{c}} = \frac{\left(84.14 \right)^{2}}{-6.77} = -1308 \ \sqrt{ar} \\ &\mathbb{P}_{e_{1}0} = \mathbb{I}_{1}^{2} \left(1 \right) = \left(24.12 \right)^{2} \ 1 = 54 \ 93.77 \ \omega \\ &\mathbb{Q}_{L} = \mathbb{I}_{1}^{2} \ \varkappa_{L} = \left(24.12 \right)^{2} \cdot 0.7854 = 43 \ 14.6 \ \omega \\ &\mathbb{S}_{s} = \sqrt{s} \ \mathbb{I}^{\varkappa_{s}} \ 220 \ (26.35 \left(44.84 = 14587 \right) \ (11.84 = -14587 \right) \ (11.84 = -14587 \right) \\ &\mathbb{R}_{s} = 14 \ 286.41 \ \simeq \right) \\ &\mathbb{R}_{s} = 48314.8 - 1308 = 3005.8 \ \simeq \right) \end{aligned}$

EE411 - Summer 2008, Final Exam

Problem 3 (25 points)

For the 3-phase circuit in the figure calculate:

- a) Load's phase and line voltage phasors (all 6 of them).
- b) Load's phase and line current phasors (all 6 of them)..
- c) Load's complex power.

Consider that all voltages and currents magnitudes are rms values.





 $V_{an} = V_{ao} - I I I_{e} = 4800 - 10^{\circ} 255.26 (-20.9) = 269.27 (22.1)$

 $V_{bn} = 264.27 \left(-\frac{97}{217}, 9\right)$ $V_{cn} = 264.27 \left(-\frac{217}{2}, 9\right)$

 $P = \sqrt{3} V_{L} I_{L} \cos P_{L_{q}} = \sqrt{3} 457.26 255.26 \cos 45 = 142952.9 W$

 $Q = \int 3V_{L} I_{L} = 5h R_{q} = 142852.8 VAC.$ S = 142.952.9 (1+j) = 202165.9 [45 VAC. Name: _____

EE411 - Summer 2008, Final Exam

Problem 4 (25 points)

Sketch the Bode plot for the magnitude of the following transfer function

$$H(s) = \frac{5s(100 - s^{2})}{(s+100)(s^{2}+20,000s+10^{8})}$$

$$H(s) = \frac{5s(100 - s^{2})}{(s+100)(s^{2}+20,000s+10^{8})} = -\frac{5 \cdot 49 \cdot 10}{(5 - 1)} \left(\frac{5}{10} - 1\right) \left(\frac{5}{10} - 1\right) \left(\frac{5}{10} + 1\right)^{2}$$

$$\int [H(s)] \left(\frac{5 + 10^{4}}{2}\right)^{2} \int \frac{100(\frac{5}{10} + 1)^{2}}{100(\frac{5}{10} + 1)^{2}} \int \frac{100(\frac{$$

