

FPGA Architecture

Mark McDermott

Fall 2009


Agenda

- **Applications of FPGAs**
- **Overview**
- **Basic Architecture of an FPGA**
 - Slice Resources
 - Memory
 - Clocking
 - I/O Resources
 - Programming Configuration
- **Self Reconfiguring FPGAs**

FPGAs Enable Massively Parallel DSP


Example 256 TAP Filter Implementation

Programmable DSP - Sequential

 

$$\frac{1 \text{ GHz}}{256 \text{ clock cycles}} = 4 \text{ MSPS}$$


FPGA - Fully Parallel Implementation

 

$$\frac{500 \text{ MHz}}{1 \text{ clock cycle}} = 500 \text{ MSPS}$$

Usual Parallel Adder Tree Implementation


Parallel Adder Tree Implementation

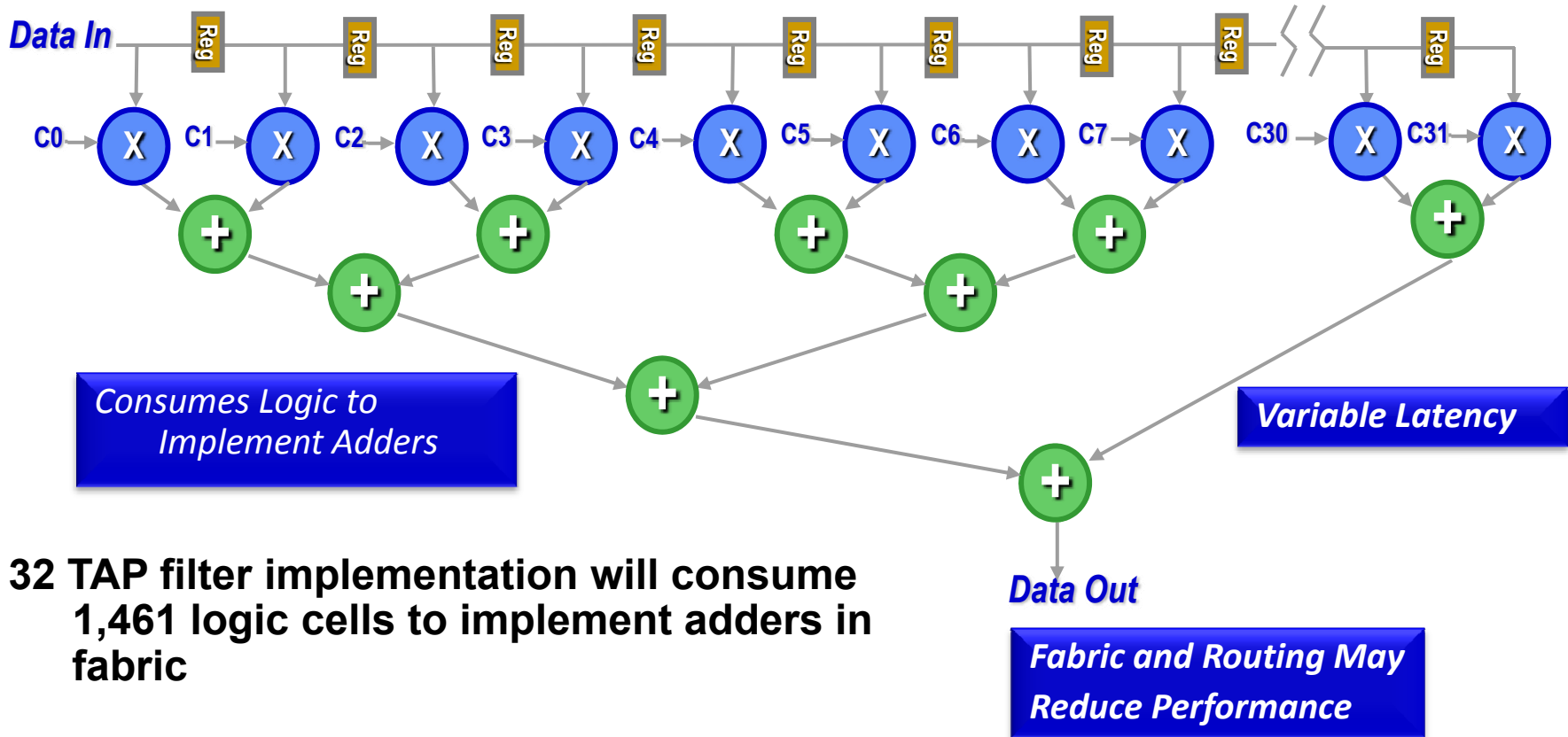

32 TAP filter implementation will consume 1,461 logic cells to implement adders in fabric

Pipelined Parallel Adder Implementation

Parallel Adder Cascade Implementation

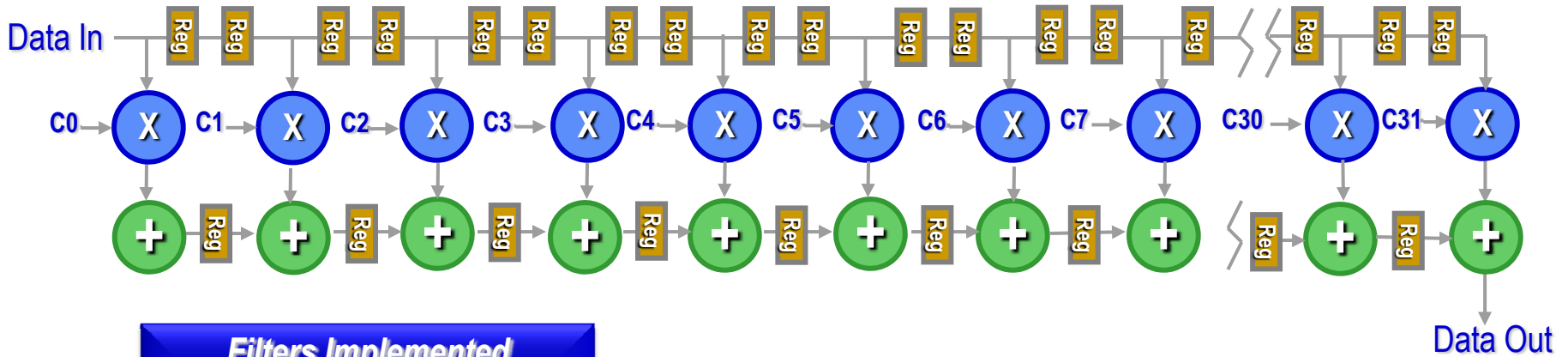

*Filters Implemented
Entirely Within the
XtremeDSP Slice*


*Guaranteed 500MHz Performance
Regardless of Filter Size*

- 32 TAP filter implementation using 32 XtremeDSP Slices


Overview

- **Most FPGAs contain the same basic resources**
 - **Slices grouped into combinational logic blocks (CLBs)**
 - **Contain combinatorial logic and register resources**
 - **Input/Output Blocks (IOBs)**
 - **Interface between the FPGA and the outside world**
 - **Programmable interconnect**
 - **Other resources**
 - **Memory**
 - **Multipliers**
 - **Global clock buffers**
 - **Boundary scan logic**

Altera Stratix Resource Block Diagram

 

Virtex-4 Resource Block Diagram

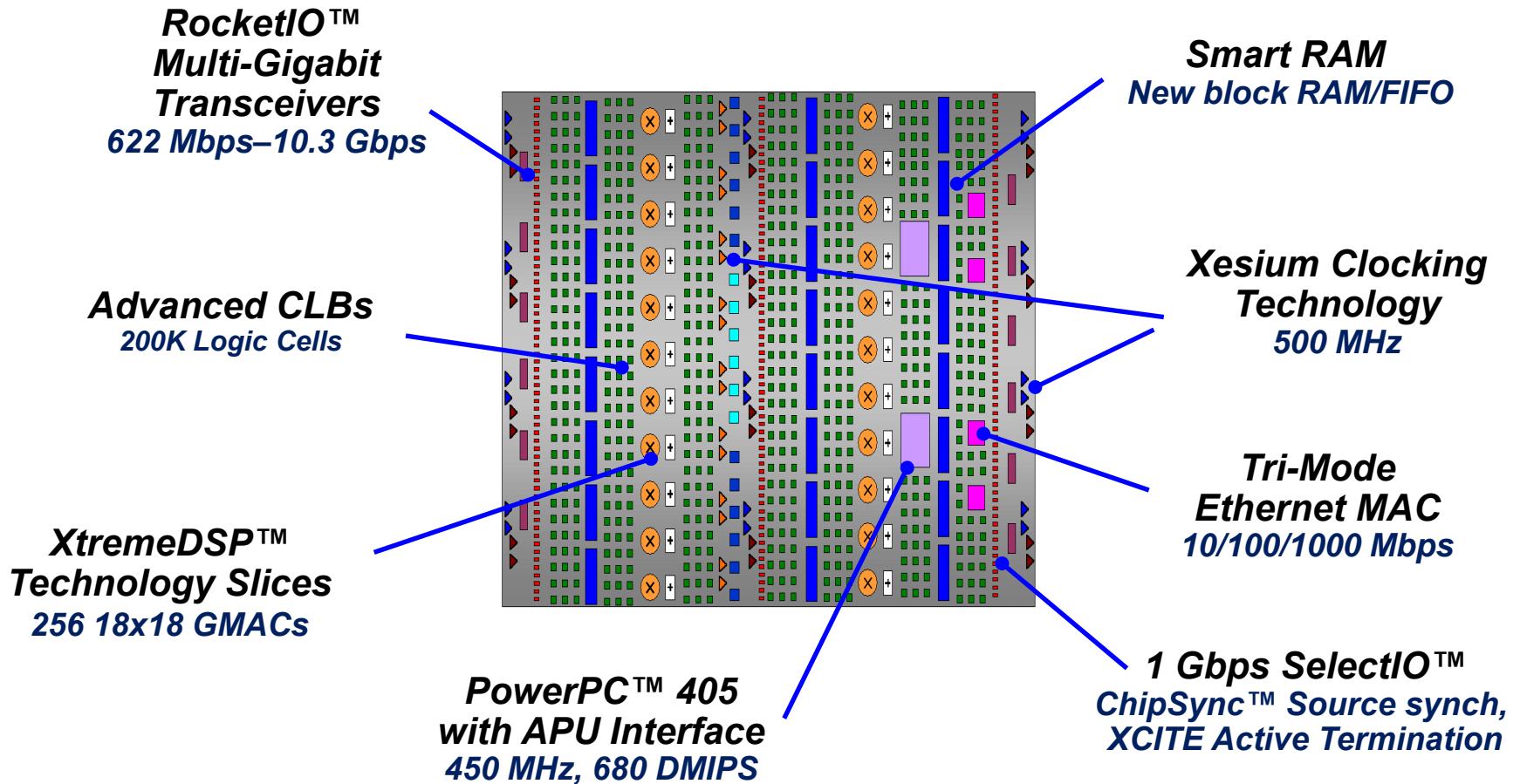

Basic Architecture of an FPGA

Logic Fabric

Logic Cell


- Lookup table (LUT)
- Flip-Flop
- Carry logic
- Muxes (not shown)

Slice

- Two Logic Cells

Spartan-3E FPGAs

- 2K to 33K logic cells

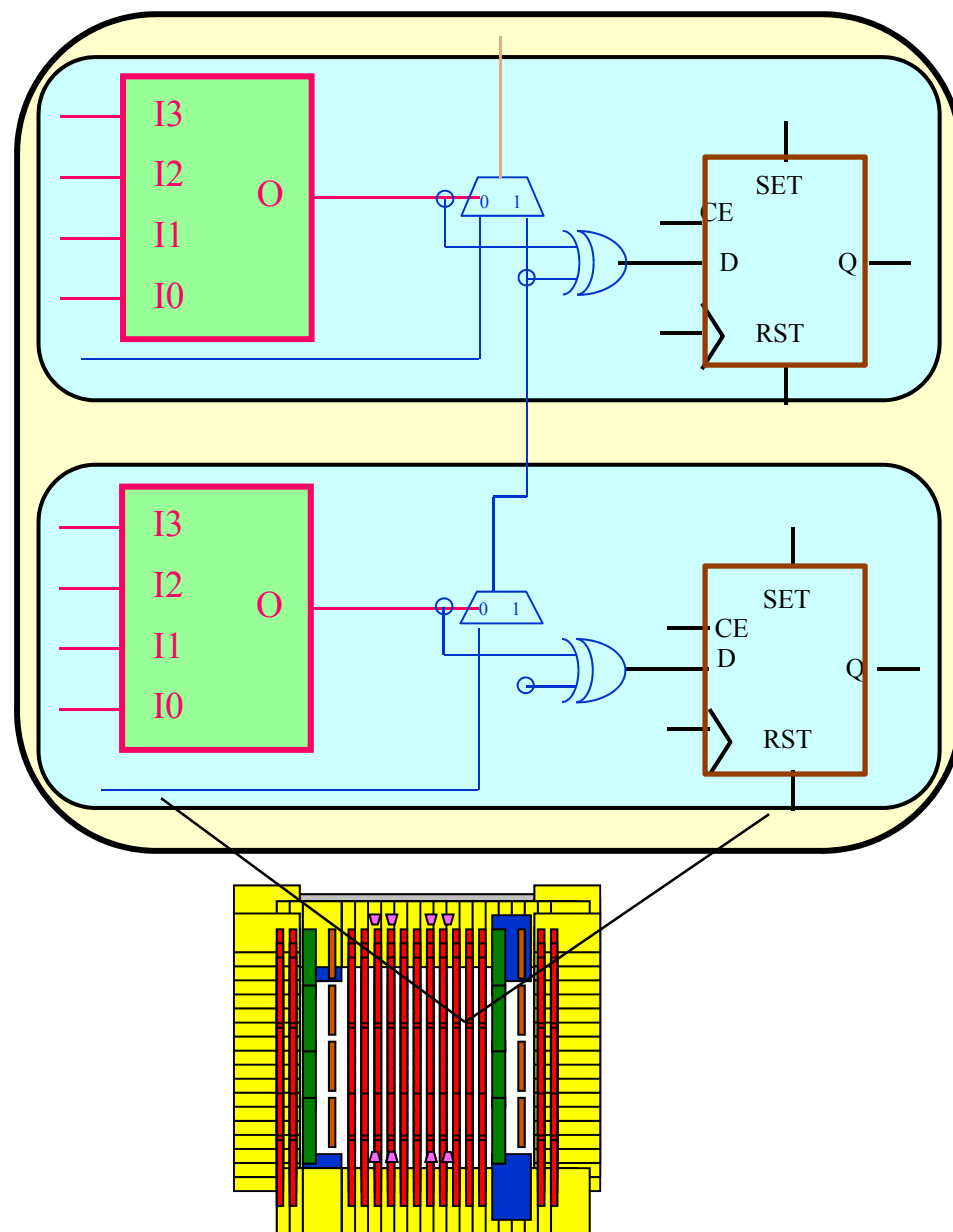


Slide courtesy of: XILINX®

Memory

- **Block RAM**
 - RAM or ROM
 - True dual port
 - Separate read and write ports
 - Independent port size
 - Data width translation
 - Excellent for FIFOs


Block RAM Configurations			
Configuration	Depth	Data bits	Parity bits
16K x 1	16Kb	1	0
8K x 2	8Kb	2	0
4K x 4	4Kb	4	0
2K x 9	2Kb	8	1
1K x 18	1Kb	16	2
512 x 36	512	32	4

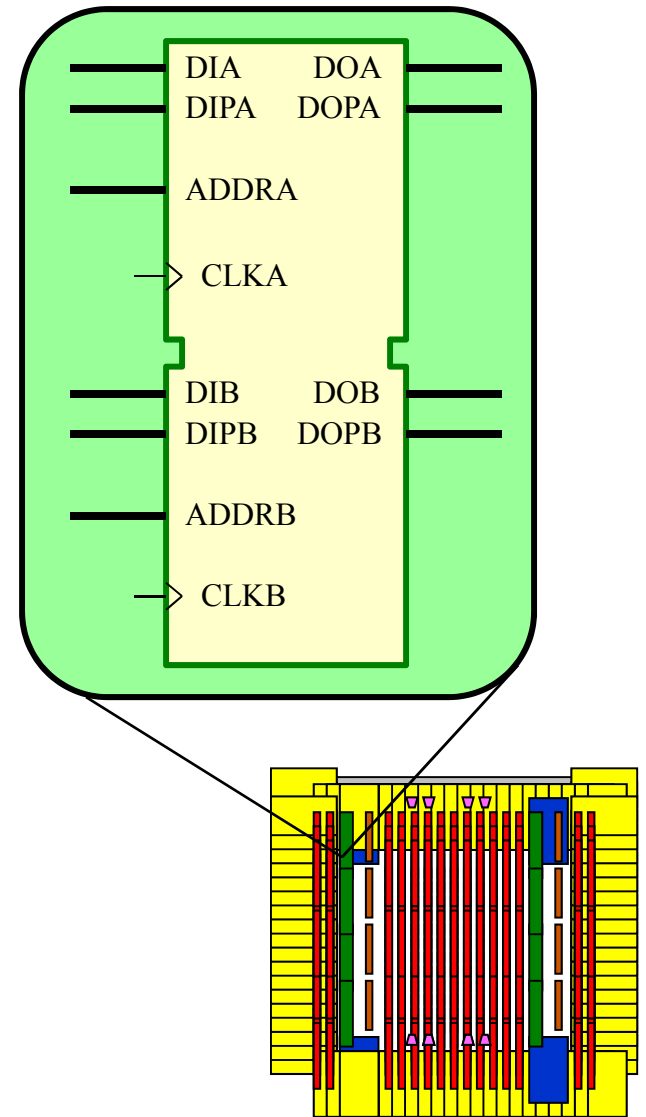

Slide courtesy of: XILINX®

Multipliers

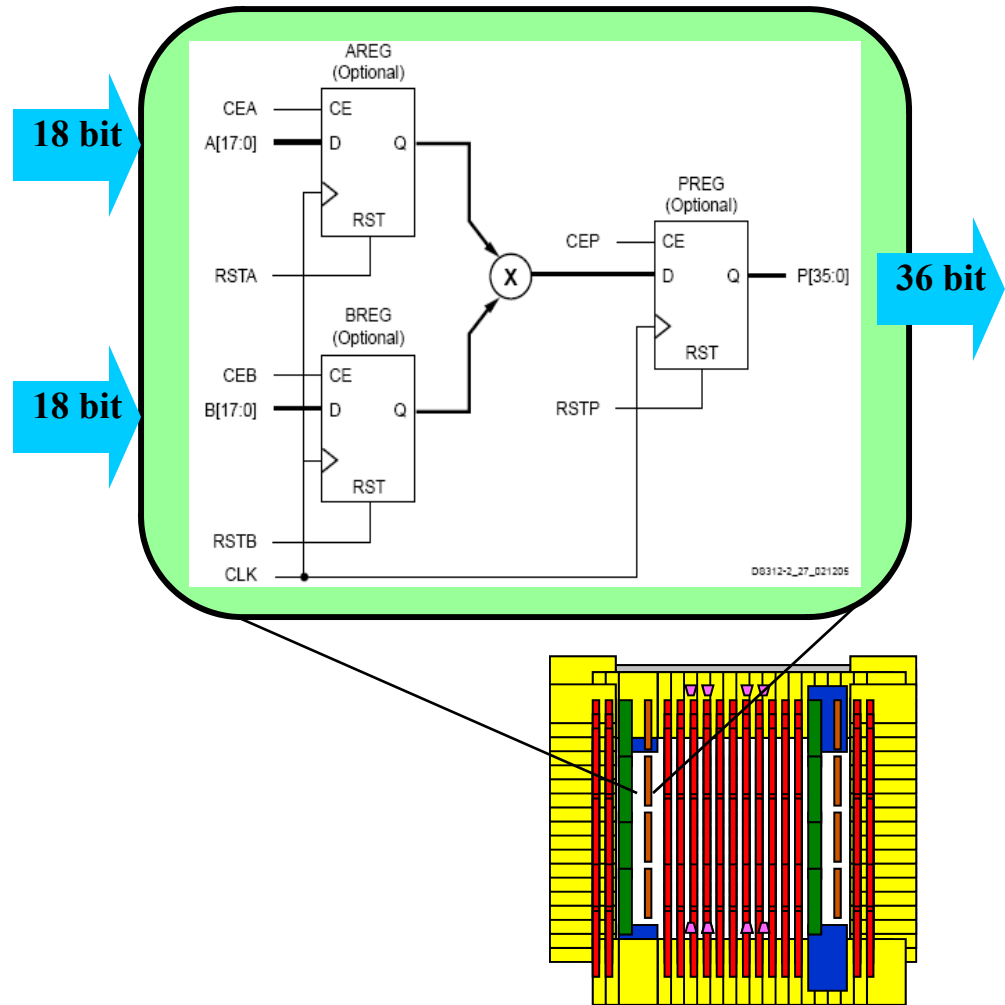
- **18 x 18 Multipliers**
 - Signed or unsigned
 - Optional pipeline stage
 - Cascadable



Clock Management


■ Digital Clock Managers (DCMs)

 - Clock de-skew
- Phase shifting
- Clock multiplication
- Clock division
- Frequency synthesis



Programmable I/Os

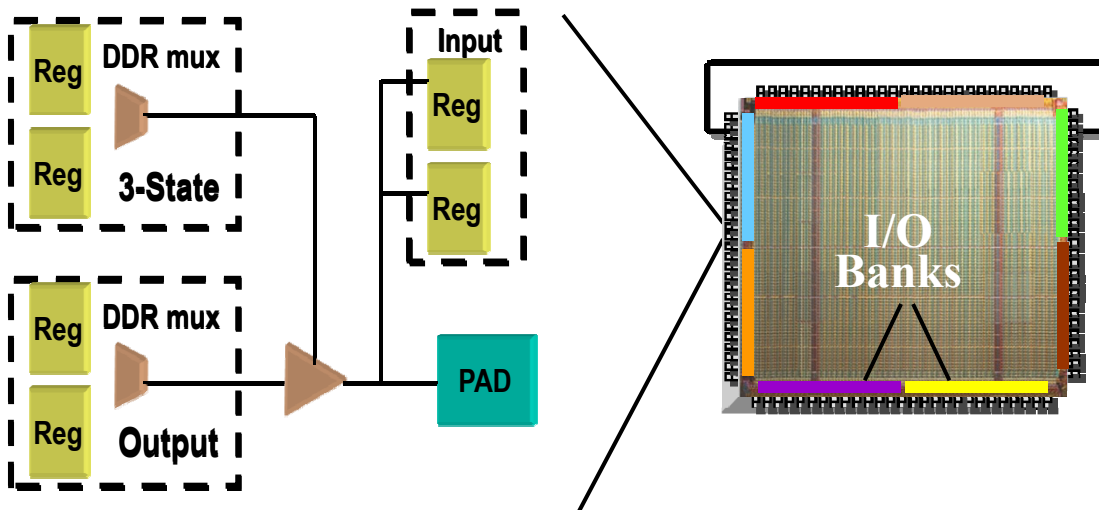- **Single-ended**
- **Differential / LVDS**
- **Programmable I/O standards**
 - Multiple I/O banks
- **DDR I/O registers**
- **On-chip termination**




	Standard	Output V_{CCO}	Input V_{REF}
Single ended	LVTTTL	3.3V	--
	LVC MOS33	3.3V	--
	LVC MOS25	2.5V	--
	LVC MOS18	1.8V	--
	LVC MOS15	1.5V	--
	LVC MOS12	1.2V	--
	PCI 32/64 bit 33MHz	3.3V	--
	SSTL2 Class I	2.5V	1.25V
	SSTL2 Class II	2.5V	1.25V
	SSTL18 Class I	1.8V	0.9V
	HSTL Class I	1.5V	0.75V
	HSTL Class III	1.5V	0.9V
	HSTL18 Class I	1.8V	0.9V
	HSTL18 Class II	1.8V	0.9V
HSTL18 Class III	1.8V	1.1V	
Differential	GTL	--	0.8V
	GTL+	--	1.0V
	LVDS2.5	2.5V	--
	Bus LVDS2.5	2.5V	--
	Ultra LVDS2.5	2.5V	--
	LVDS_ext2.5	2.5V	--
	RSDS	2.5V	--
LDT2.5	2.5V	--	

Logic Fabric


Slices and CLB

 - Each Virtex™-II CLB contains four slices
 - Local routing provides feedback between slices in the same CLB, and it provides routing to neighboring CLBs
 - A switch matrix provides access to general routing resources



Simplified Slice Structure

 
- **Each slice has four outputs**
 - Two registered outputs, two non-registered outputs
 - Two BUFTs associated with each CLB, accessible by all 16 CLB outputs
- **Carry logic runs vertically, up only**
 - Two independent carry chains per CLB



Detailed Slice Structure


The next few slides discuss the slice features

 - LUTs
- MUXF5, MUXF6, MUXF7, MUXF8 (only the F5 and F6 MUX are shown in this diagram)
- Carry Logic
- MULT_ANDs
- Sequential Elements




Look-Up Tables

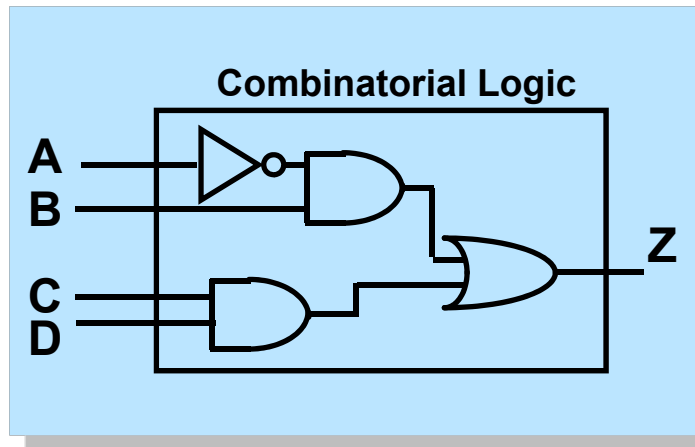- **Combinatorial logic is stored in Look-Up Tables (LUTs)**
 - Also called Function Generators (FGs)
 - Capacity is limited by the number of inputs, not by the complexity
- **Delay through the LUT is constant**




A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
	.	.	.	
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Connecting Look-Up Tables

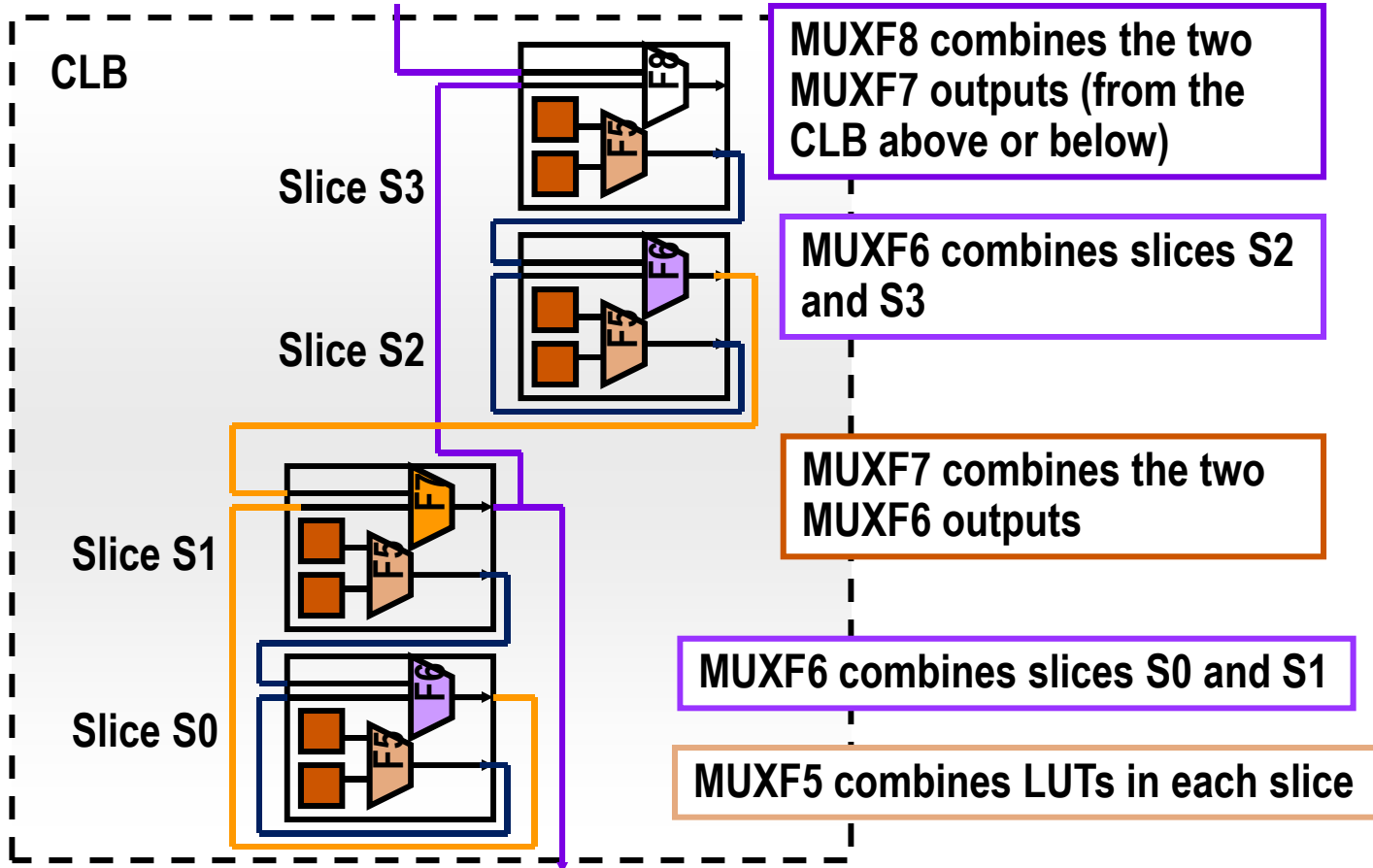


MULT_AND Gate

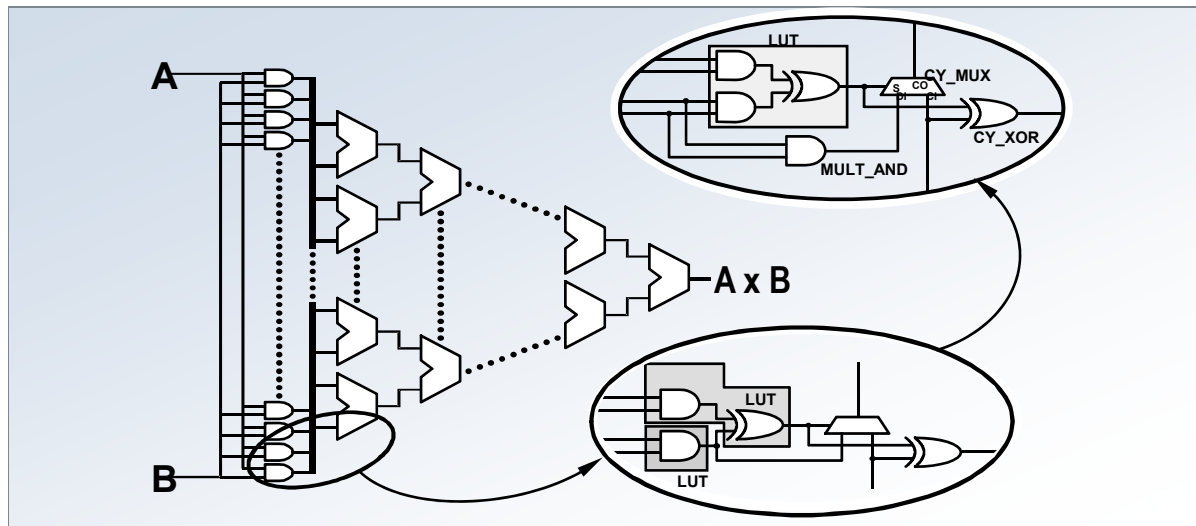- **Highly efficient multiply and add implementation**
 - Earlier FPGA architectures require two LUTs per bit to perform the multiplication and addition
 - The MULT_AND gate enables an area reduction by performing the *multiply* and the *add* in one LUT per bit




Flexible Sequential Elements

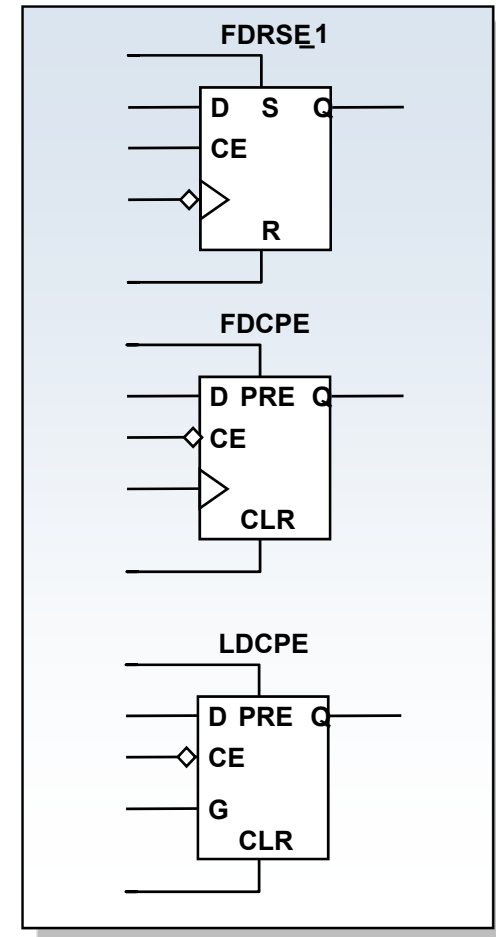- **Either flip-flops or latches**
- **Two in each slice; eight in each CLB**
- **Inputs come from LUTs or from an independent CLB input**
- **Separate set and reset controls**
 - Can be synchronous or asynchronous
- **All controls are shared within a slice**
 - Control signals can be inverted locally within a slice




Shift Register LUT (SRL16CE)

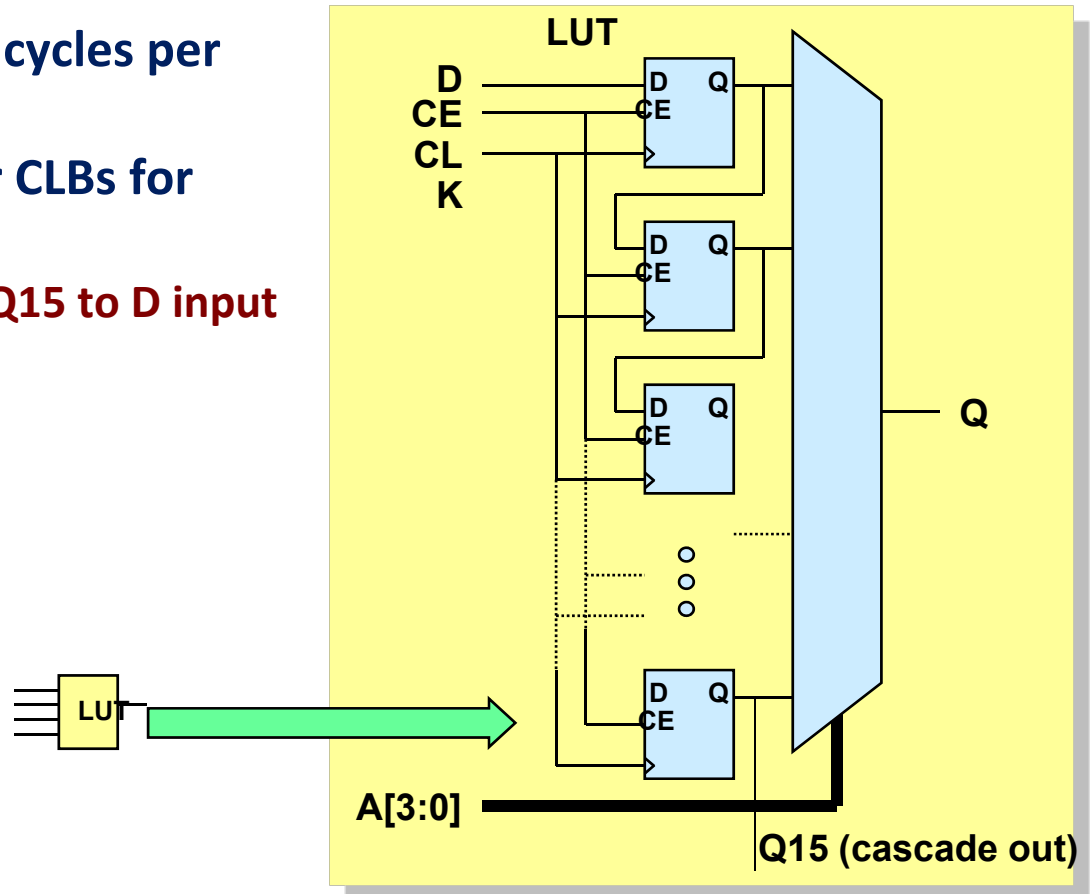- **Dynamically addressable serial shift registers**
 - Maximum delay of 16 clock cycles per LUT (128 per CLB)
 - Cascadable to other LUTs or CLBs for longer shift registers
 - **Dedicated connection from Q15 to D input of the next SRL16CE**
 - Shift register length can be changed asynchronously by toggling address A




Shift Register LUT Example

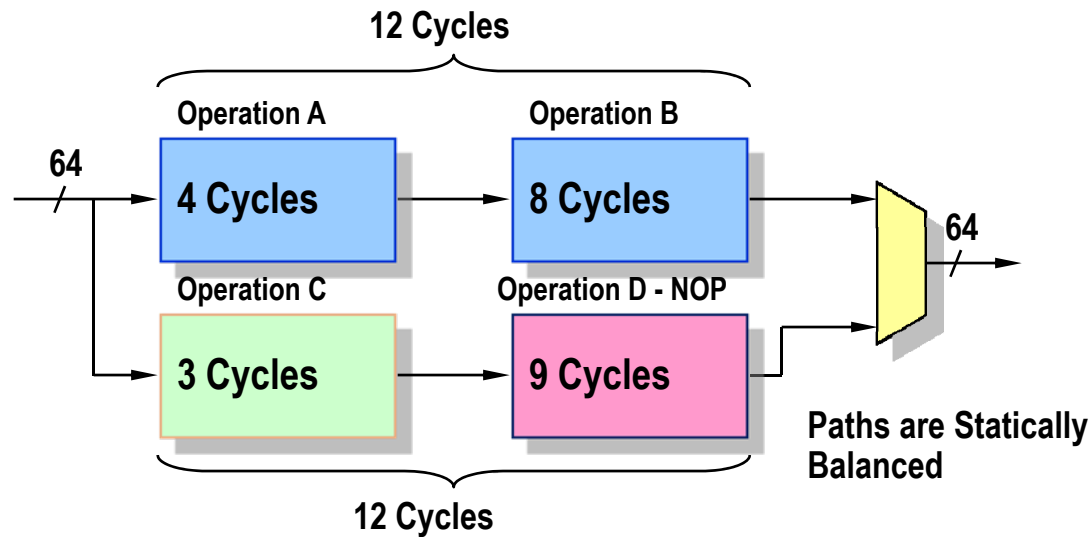- **The SRL can be used to create a No Operation (NOP)**
 - This example uses 64 LUTs (8 CLBs) to replace 576 flip-flops (72 CLBs) and associated routing and delays




Dedicated Multiplier Blocks

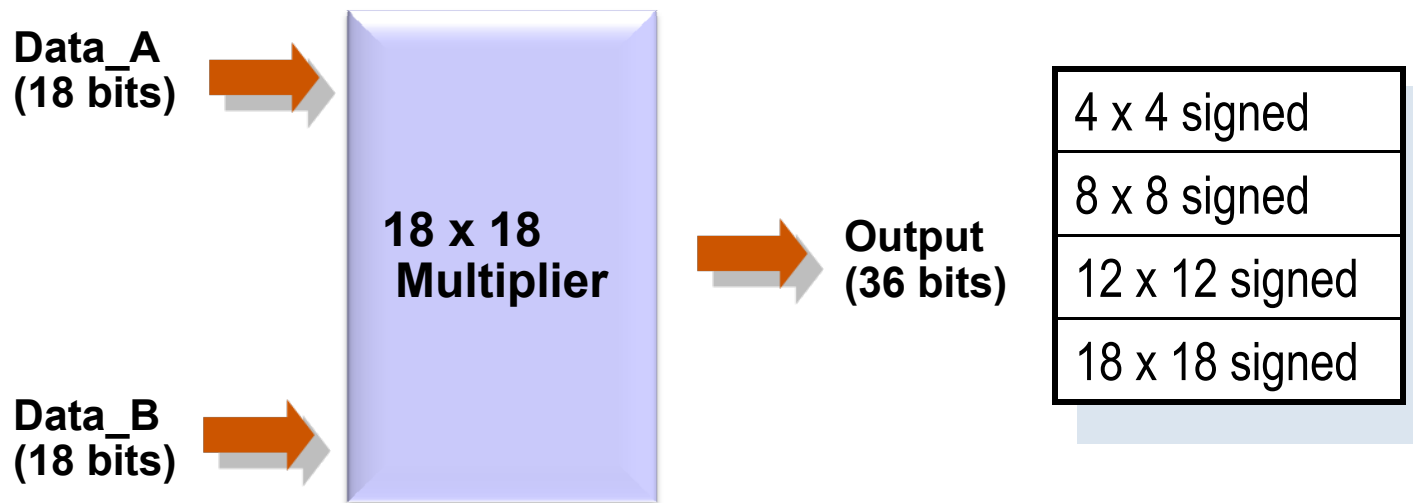- **18-bit two's complement signed operation**
- **Optimized to implement Multiply and Accumulate functions**
- **Multipliers are physically located next to block SelectRAM™ memory**




Switchbox Operation


Before Programming

 

After Programming

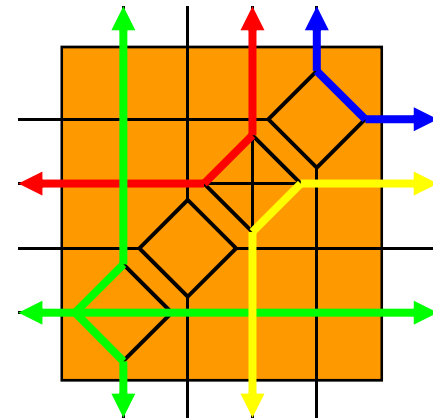


 - 6 pass transistors per switchbox interconnect point
- Pass transistors act as programmable switches
- Pass transistor gates are driven by configuration memory cells




Logic Cluster Size

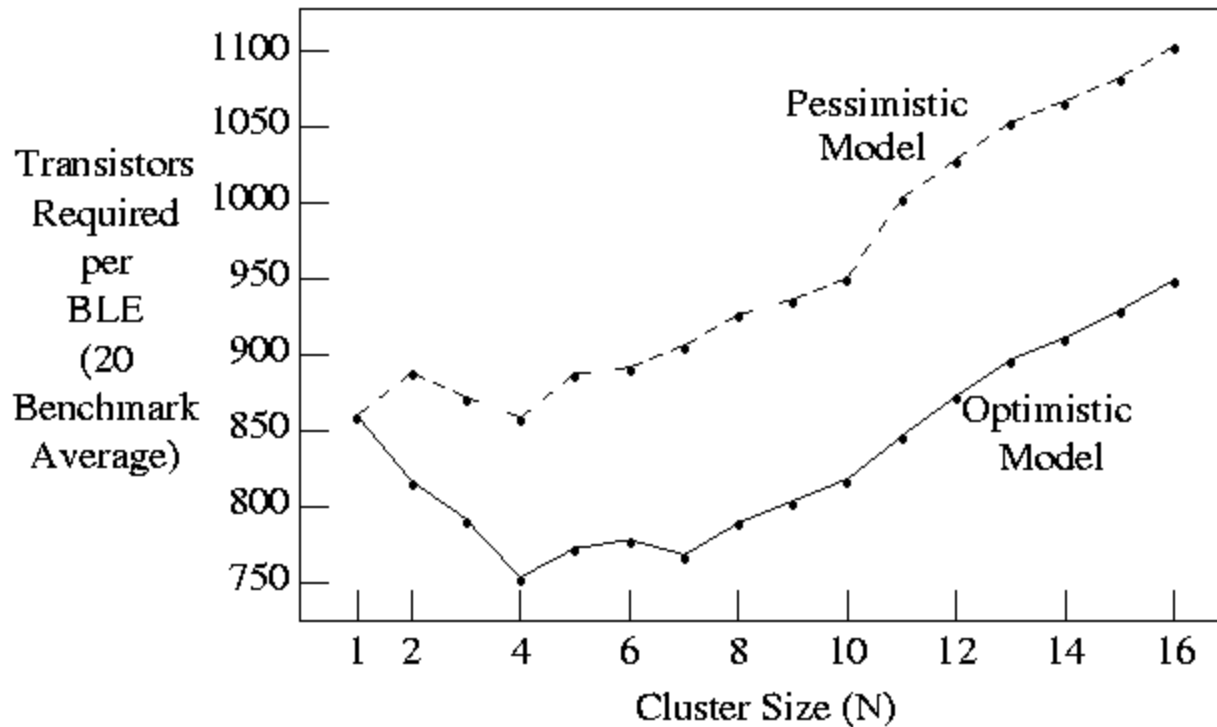- Interestingly, small block cluster more efficient (Betz – CICC’99)
- Includes area needed for routing.
- Small clusters (e.g. one BLE (Basic Logic Element) per cluster) are not “CAD friendly).
- Most commercial devices have 4-8 BLEs per cluster




Number of Inputs per Cluster

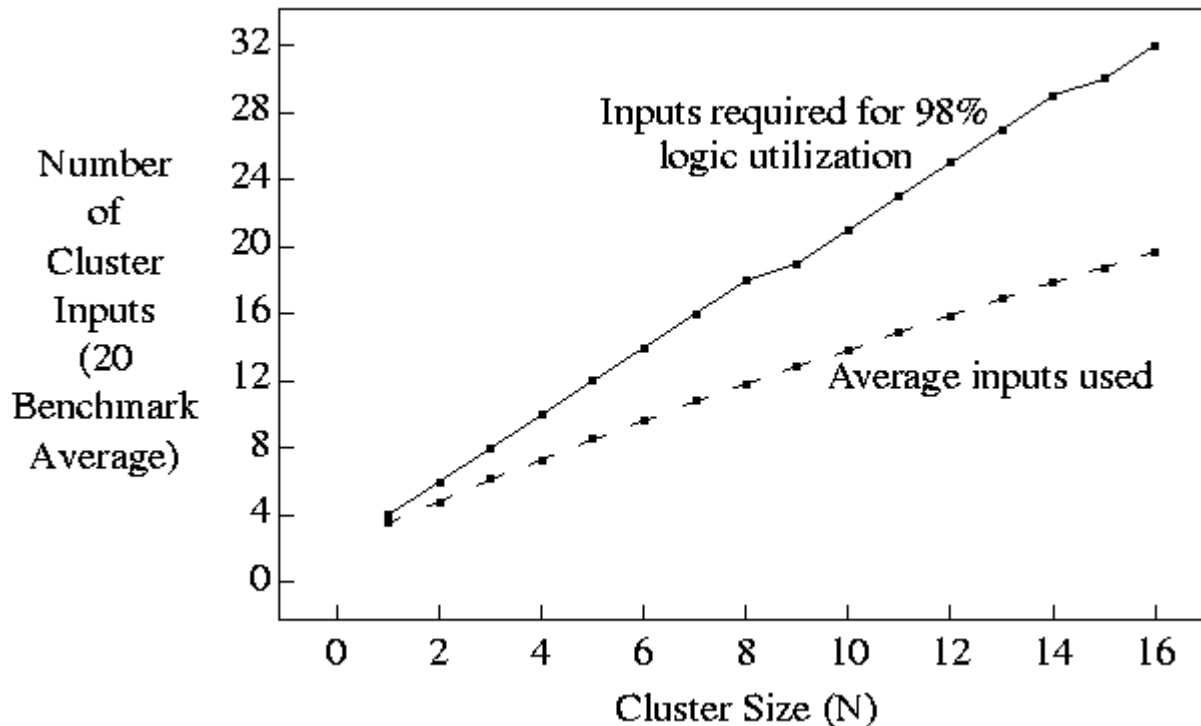- Lots of opportunities for input sharing in large clusters (Betz – CICC'99)
- Reducing inputs reduces the size of the device and makes it faster.
- Most FPGA devices (Xilinx, Lucent) have 4 BLE per cluster with more inputs than actually needed.




Connection Box Flexibility

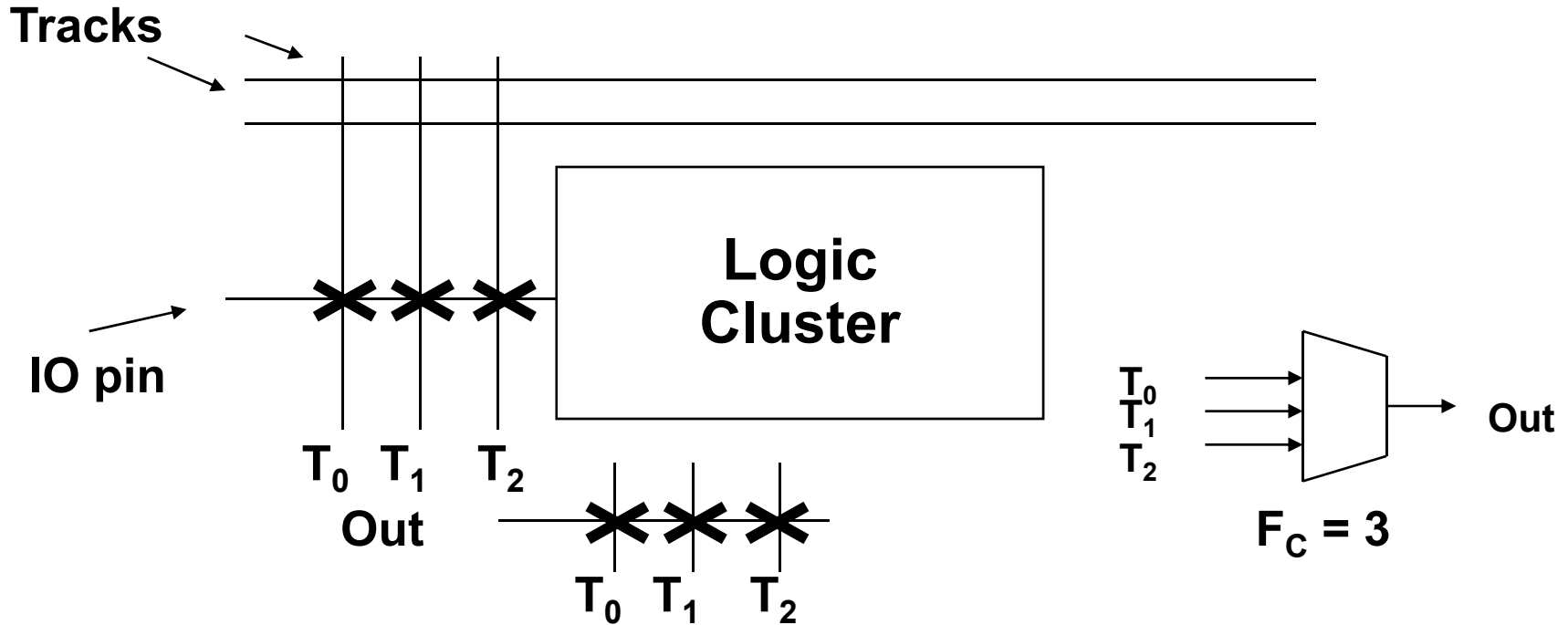

- F_c -> How many tracks does an input pin connect to?
- If logic cluster is small, F_c is large $F_c = W$
- If logic cluster is large, F_c can be less.
 - Approximately $0.2W$ for Xilinx XC4000EX

Switchbox Flexibility

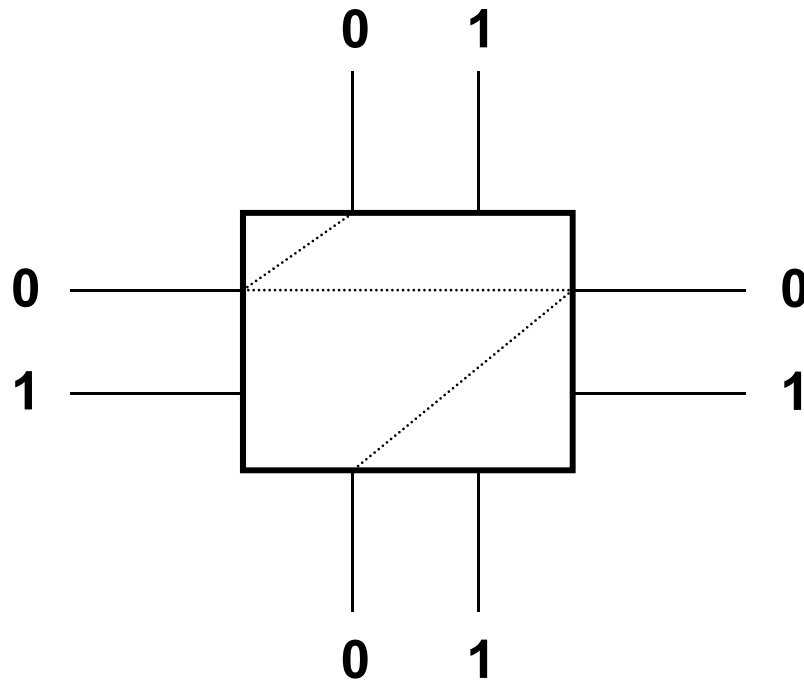- Switch box provides optimized interconnection area.
- Flexibility found to be not as important as F_C
- Six transistors needed for $F_S = 3$



Putting it all together

- **Xilinx XC4000EX family**

- $F_S = 3$
- $F_C = 0.2$
- $I = 8$
- Num BLE – about 2.5

- **Altera Flex10K family**


- $F_S = 3$
- $F_C = 0.25$
- $I = 22$
- Num BLE – about 28

- **NOTE: Altera doesn't use segmentation. All lines span large fraction of device.**

Memory


Distributed SelectRAM Resources

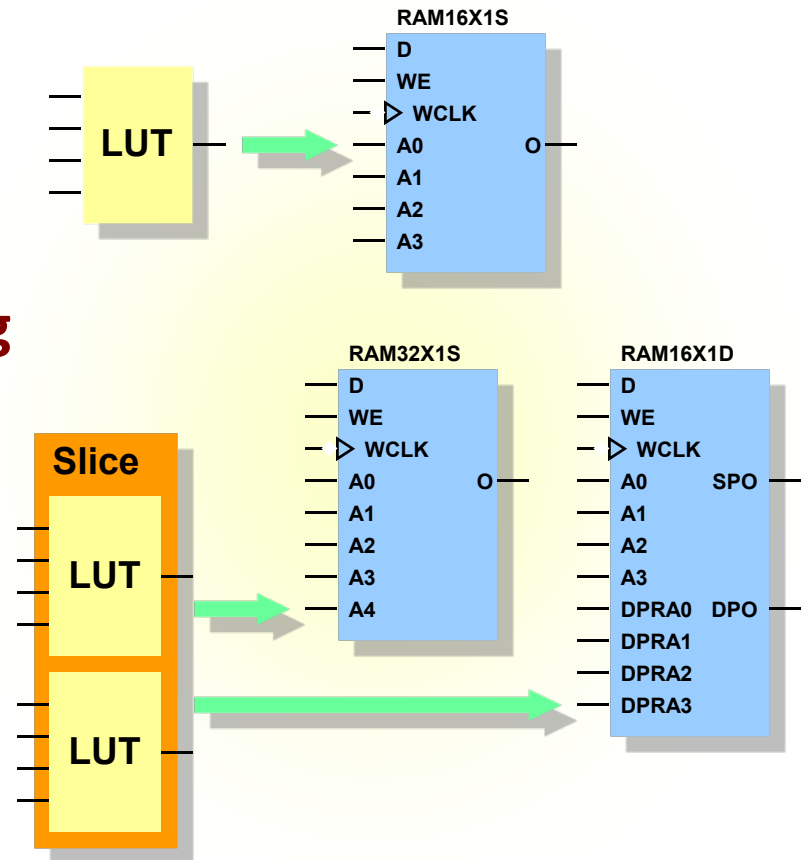- **Uses a LUT in a slice as memory**
- **Synchronous write**
- **Asynchronous read**
 - Accompanying flip-flops can be used to create synchronous read
- **RAM and ROM are initialized during configuration**
 - Data can be written to RAM after configuration
- **Emulated dual-port RAM**
 - One read/write port
 - One read-only port



Block SelectRAM Resources

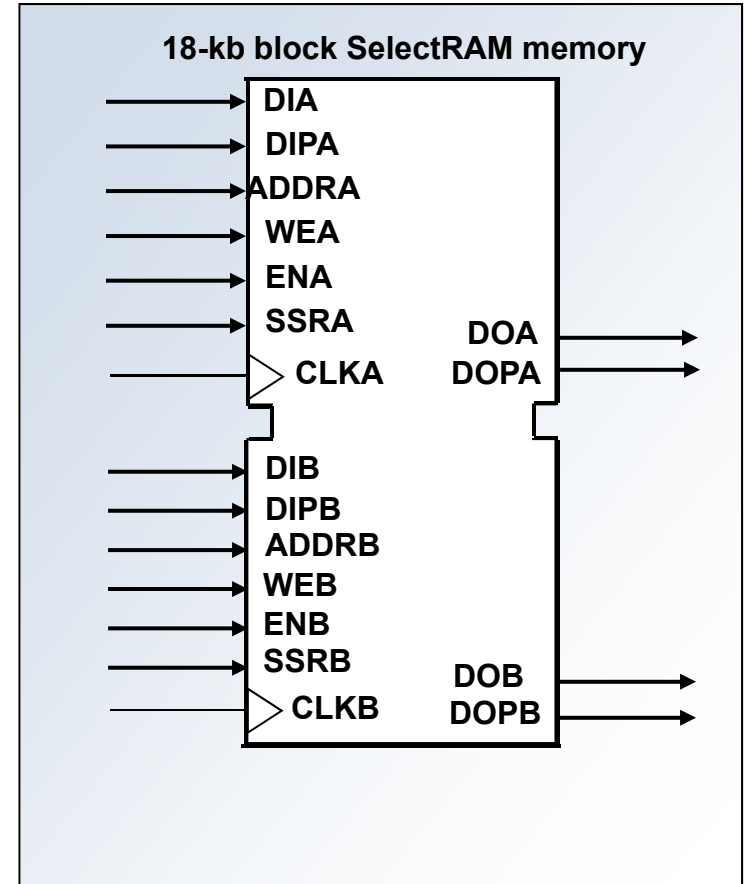- **Up to 3.5 Mb of RAM in 18-kb blocks**
 - Synchronous read and write
- **True dual-port memory**
 - Each port has synchronous read and write capability
 - Different clocks for each port
- **Supports initial values**
- **Synchronous reset on output latches**
- **Supports parity bits**
 - One parity bit per eight data bits



Clocking

Global Clock Routing Resources

- **Sixteen dedicated global clock multiplexers**
 - Eight on the top-center of the die, eight on the bottom-center
 - Driven by a clock input pad, a DCM, or local routing
- **Global clock multiplexers provide the following:**
 - Traditional clock buffer (BUFG) function
 - Global clock enable capability (BUFGCE)
 - Glitch-free switching between clock signals (BUFGMUX)
- **Up to eight clock nets can be used in each clock region of the device**
 - Each device contains four or more clock regions


Digital Clock Manager (DCM)

- **Up to twelve DCMs per device**
 - Located on the top and bottom edges of the die
 - Driven by clock input pads
- **DCMs provide the following:**
 - Delay-Locked Loop (DLL)
 - Digital Frequency Synthesizer (DFS)
 - Digital Phase Shifter (DPS)
- **Up to four outputs of each DCM can drive onto global clock buffers**
 - All DCM outputs can drive general routing

Input Output Resources

IOB Element

 - **Input path**
 - Two DDR registers
- **Output path**
 - Two DDR registers
 - Two 3-state enable DDR registers
- **Separate clocks and clock enables for I and O**
- **Set and reset signals are shared**



SelectIO Standard

- **Allows direct connections to external signals of varied voltages and thresholds**
 - Optimizes the speed/noise tradeoff
 - Saves having to place interface components onto your board
- **Differential signaling standards**
 - LVDS, BLVDS, ULVDS
 - LDT
 - LVPECL
- **Single-ended I/O standards**
 - LVTTTL, LVCMOS (3.3V, 2.5V, 1.8V, and 1.5V)
 - PCI-X at 133 MHz, PCI (3.3V at 33 MHz and 66 MHz)
 - GTL, GTLP
 - and more!

Digital Controlled Impedance (DCI)

■ DCI provides

- Output drivers that match the impedance of the traces
- On-chip termination for receivers and transmitters


■ DCI advantages

- Improves signal integrity by eliminating stub reflections
- Reduces board routing complexity and component count by eliminating external resistors
- Eliminates the effects of temperature, voltage, and process variations by using an internal feedback circuit

Programming Configurations


Anti-fuse Switch

 - **Anti-fuses are one-time programmable.**
 - Pulse eliminates dielectric
 - Only need to program once.




Anti-Fuse FPGA

 - Negligible programming overhead
- Low capacitance routing (fast)
- Security
- Tolerant of firm errors
- Resistance of about 100Ω




Typical Actel Anti-fuse Interconnect

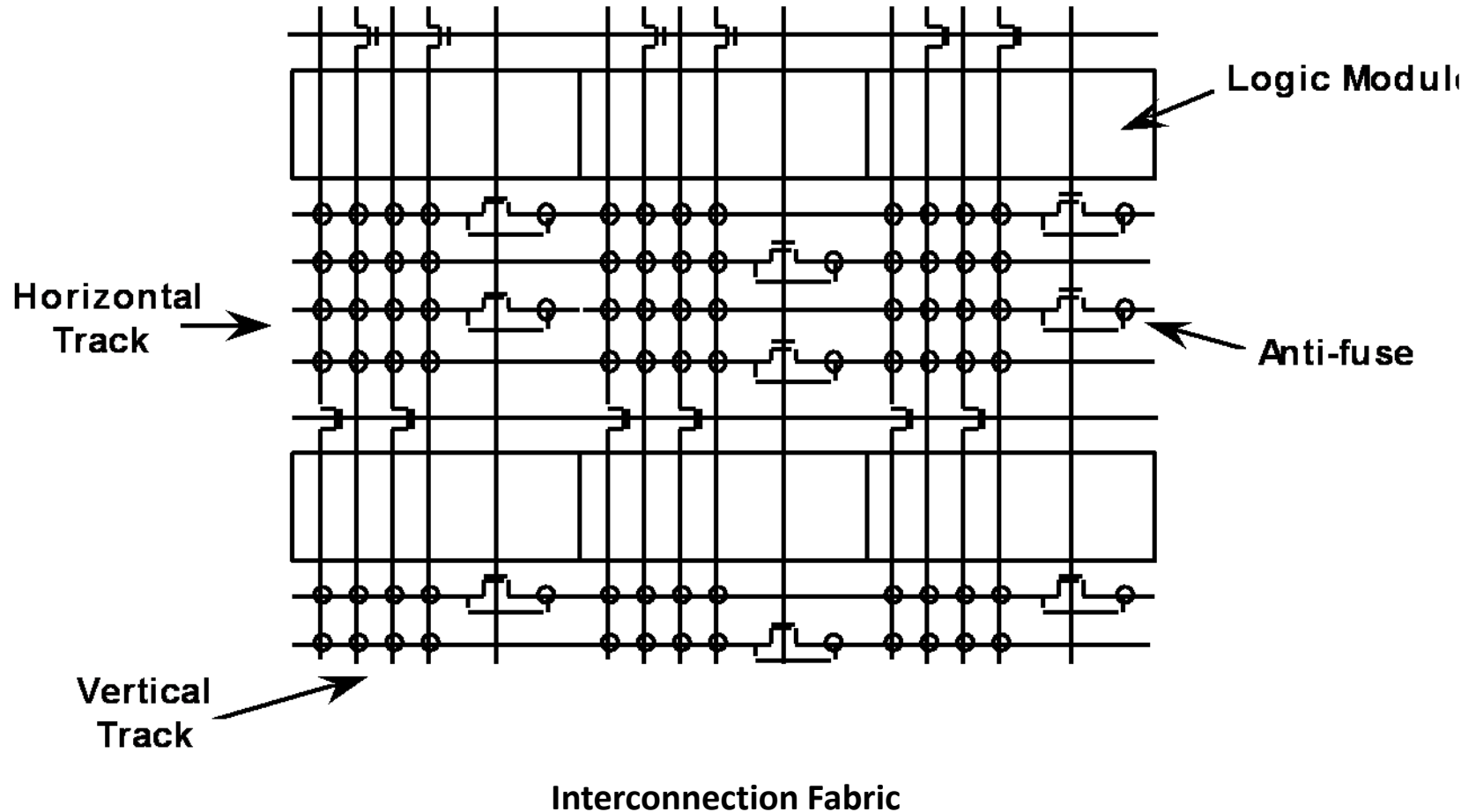


Anti-fuse Security

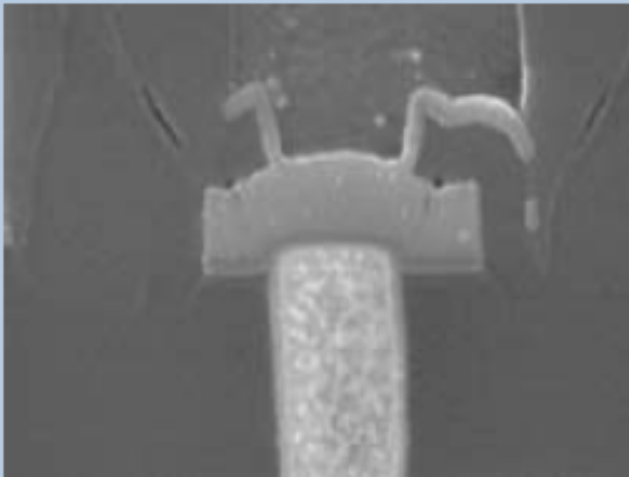- **Very good for design security**
 - No bitstream can be intercepted in the field (no bitstream transfer, no external configuration device)
 - Need a Scanning Electron Microscope (SEM) to try to know the antifuse states (an Actel AX2000 antifuse FPGA contains 53 million antifuses with only 2-5% programmed in an average design)




Unprogrammed Antifuse Element

 

Programmed Antifuse Element


Flash / EEPROM Devices

- Migrated from early PLD technology
- Traditionally based on AND/OR architecture
- Most often used for glue logic, state machines, etc
- High ratio of logic-to-registers

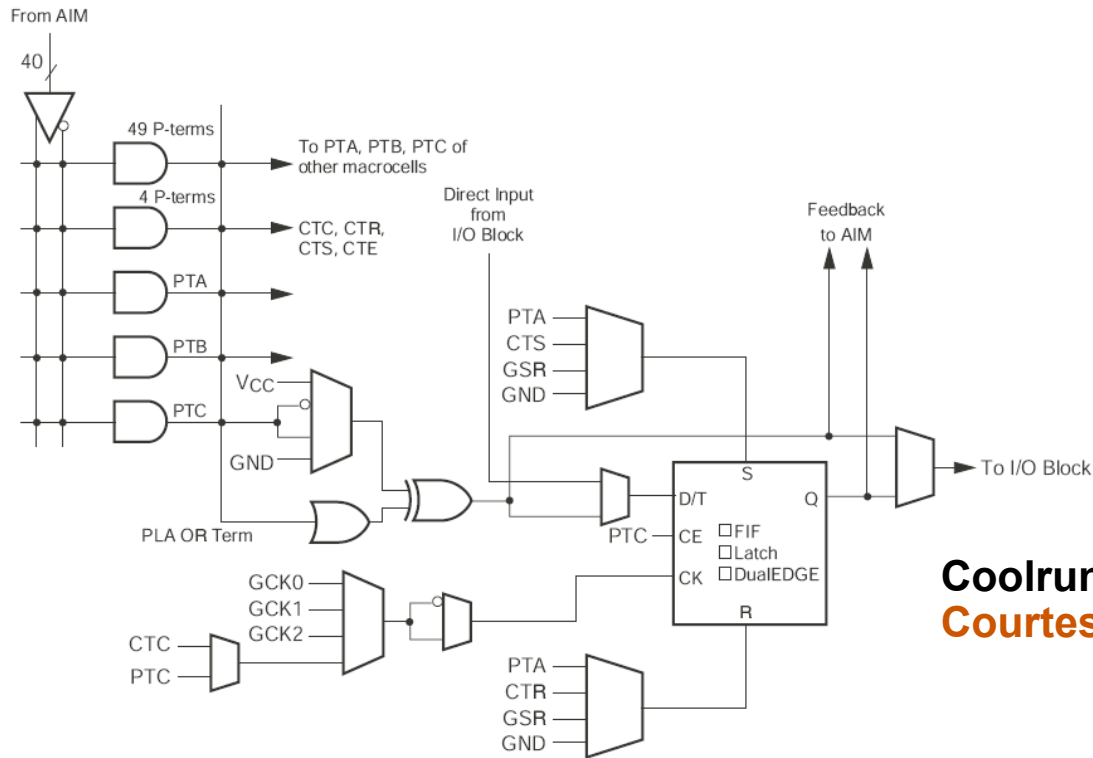


Coolrunner II
Courtesy: Xilinx

FLASH-Memory Switch


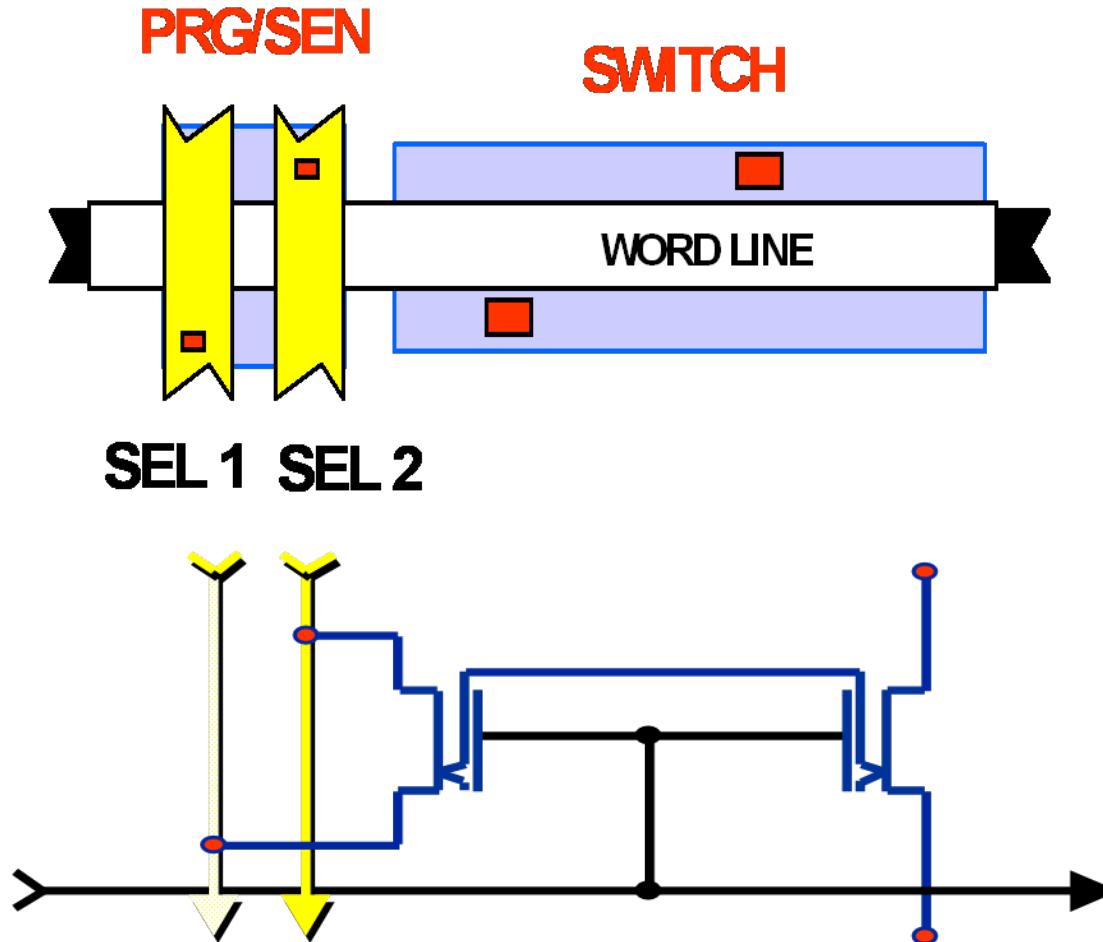


Altera Max 7000 Macrocell

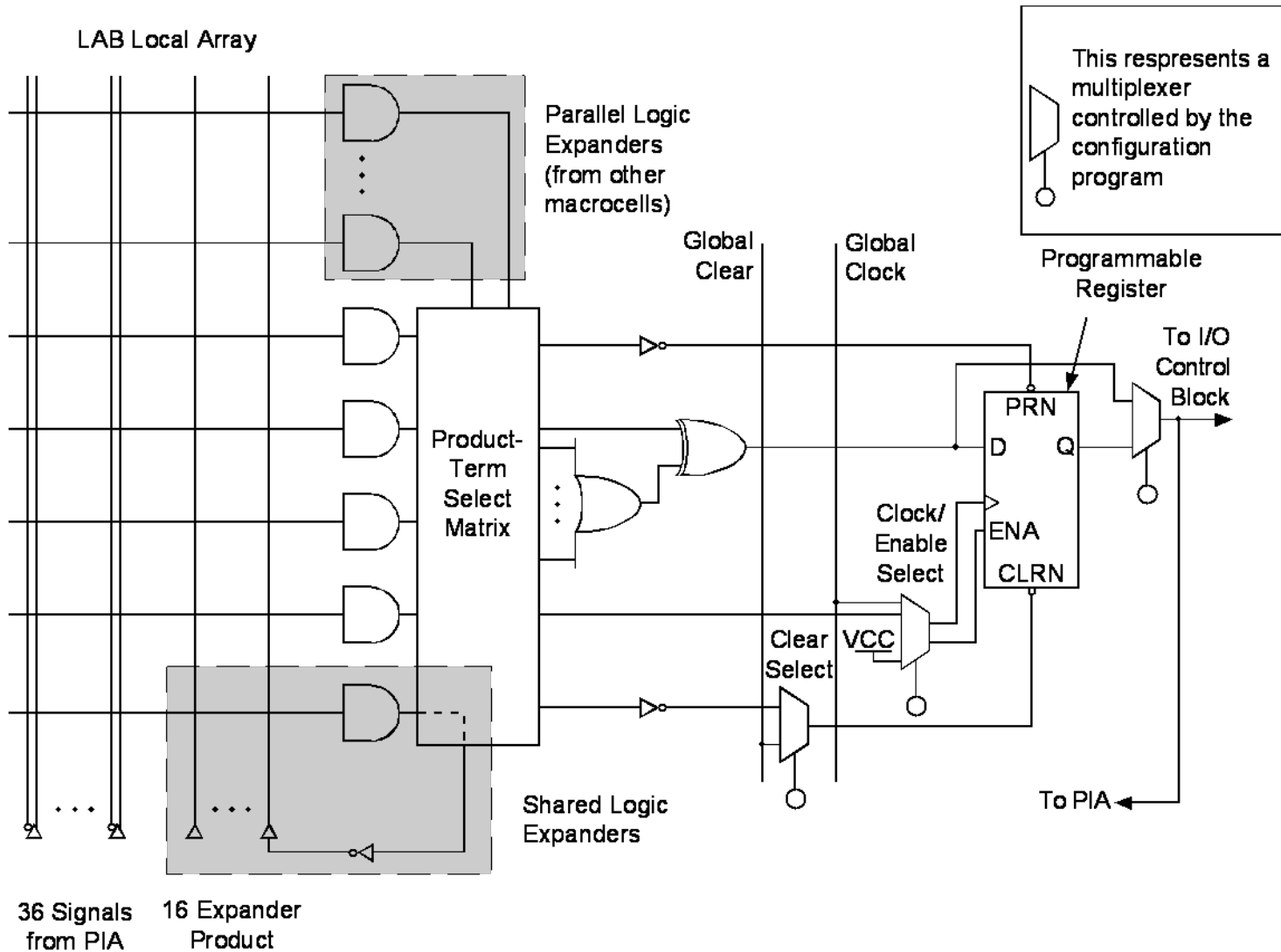

SRAM-based FPGA

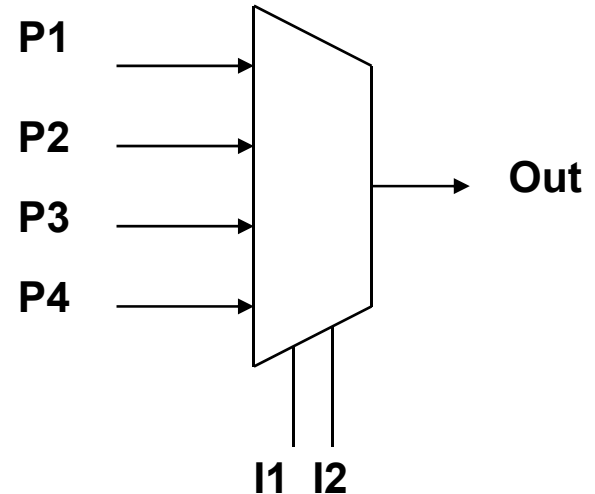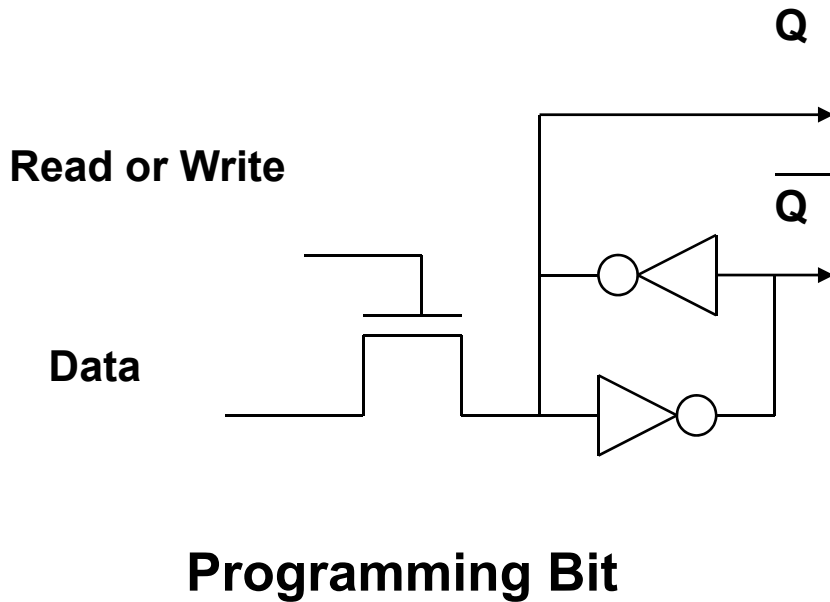- SRAM bits can be programmed many times
- Each programming bit takes up five transistors
- Larger device area reduces speed versus EPROM and anti-fuse.



2-Input LUT

Heterogeneous FPGA Architectures


Heterogeneity in FPGA Architectures

■ Heterogeneity among SLICES

- Programmable logic and routing
- Tiles are not identical
 - soft logic fabric [Kaviani, FPGA'96]]
 - hard structures [Jamieson, FPL'05]
- Dedicated hard structures
 - e.g. DSP
 - e.g. memory block

■ Heterogeneity within a SLICE

 - Programmable logic and routing
- Tiles (SLICES) are identical
- Different logics exist within a SLICE
 - e.g. LUTs with different size [Cong, FPGA'99]
 - e.g. mixed PLAs and LUTs [Cong, TODAES'05]
 - e.g. mixed macro-gates and LUT




(source: Jamieson@FPL'05)

Heterogeneous FPGA with Macro-Gates


- **There exists programmability and cost trade-off between LUTs and macrogates**
 - Xilinx V4 benefits from small gates (MUX2, XOR2) built in SLICES.
- **The benefit of wider macro-gates**
 - Effectiveness of the incorporation of wider logic functions (macro gates) is not clear.
- **Our contributions**
 - Design a new FPGA architecture with mixed LUTs and macro-gates
 - Propose a new automatic synthesis flow for mapping a circuit to the proposed FPGA architecture
 - Evaluate the architecture and show that the proposed architecture reduces delay and area by 16.5% and 30%, respective, compared to the LUT-only architecture.

Reconfigurable FPGAs

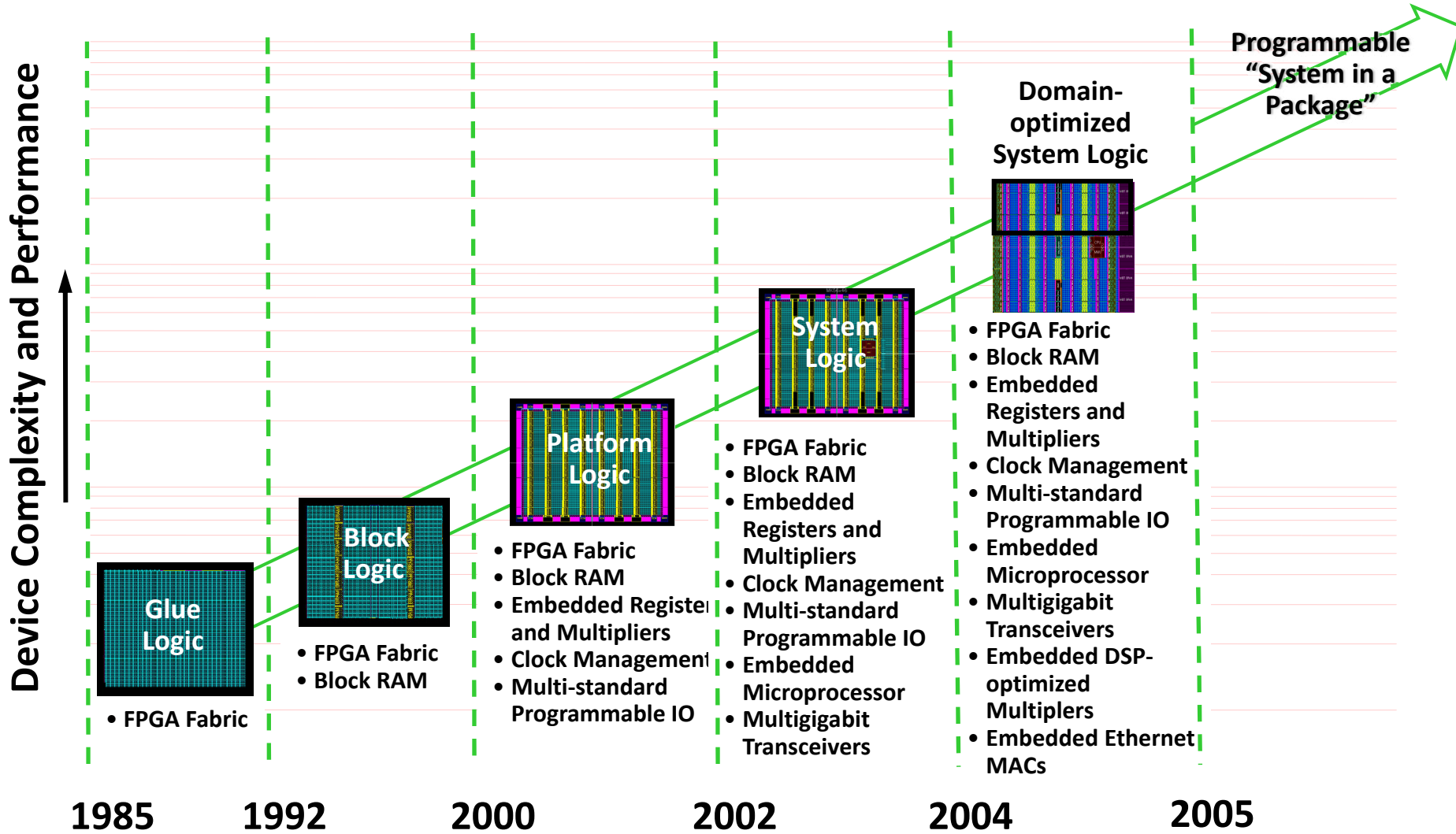Architectural Evolution Reconfigurable FPGAs



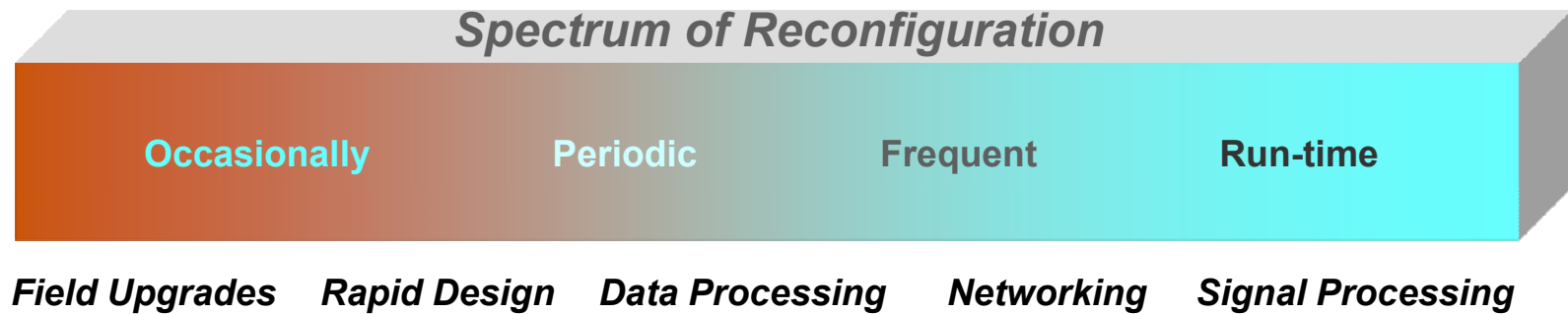
New use models enabled with Reconfigurable FPGAs



- **More efficient use of hardware**
 - Adaptive hardware algorithms
 - Design modules that time share device resources
 - Reduced device count and lower power consumption

FPGA Partial Reconfiguration

 - **Think of an FPGA as Two Layers**
 - Configuration Memory Layer
 - User Logic Layer
- **Configuration memory controls functions on user logic layer**
- **Partial Reconfiguration allows a portion of device to be changed while the rest is still running**
- **Documented in XAPP 290**




What FPGA Configuration Memory Controls

- All interconnection (wiring)
- Logic Definition (Look-up Tables or "LUTs")
- Multiply by, divide by, etc.
- Inversion
- Feature selection
- Interface to hardwired blocks, e.g. PPC
- Pipeline on/off
- ECC enable/disable
- BRAM width
- I/O Modes

Partial Reconfiguration Modules (PRMs)

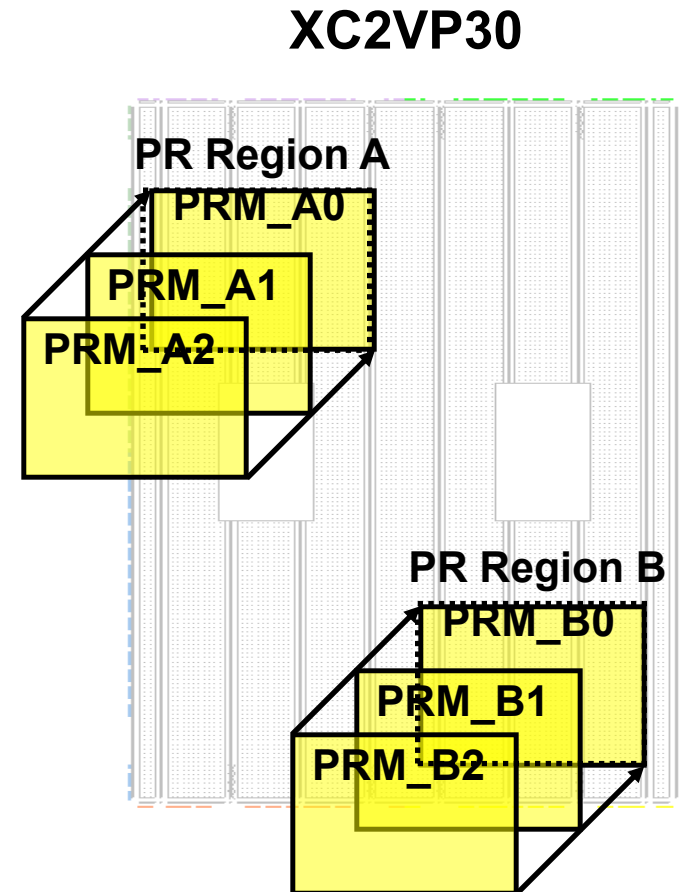- One or more PR regions can be defined
- Multiple PRMs can be defined for each region



References

- http://toolbox.xilinx.com/docsan/xilinx8/books/data/docs/dev/dev0001_1.html
- http://www.xilinx.com/support/documentation/application_notes/xapp466.pdf
- http://www.xilinx.com/support/documentation/application_notes/xapp290.pdf

Backup

Timing

Timing Constraints

- **Timing Constraints give the tools a performance goal**
- **Place & Route uses timing constraints**
 - PAR runs the timing analysis tool in the background
 - Real-time analysis of current results against performance goals
- **Without constraints, PAR tries to reduce run-time**
 - Finishes quickly
 - Modest effort to optimize performance
- **With constraints, PAR tries to meet performance goals**
 - Run-time may be longer
 - Aggressive time constraints and higher effort levels can significantly increase run-time

Basic Timing Constraints

- **PERIOD** – Target clock period for internal sequential paths

- **OFFSET IN BEFORE** – Target “input setup” time (T_{su})
 - Reference between *external INPUT pin* and *CLK pin*

- **OFFSET OUT AFTER** – Target “clock to out” time (T_{co})
 - Reference between *external CLK pin* and *OUTPUT pin*



PERIOD Constraint

■ CLOCK PERIOD

NET "MYCLK" TNM_NET = " MYCLK ";

TIMESPEC "TS_MYCLK" = PERIOD " MYCLK " 10 ns HIGH 50 %;

 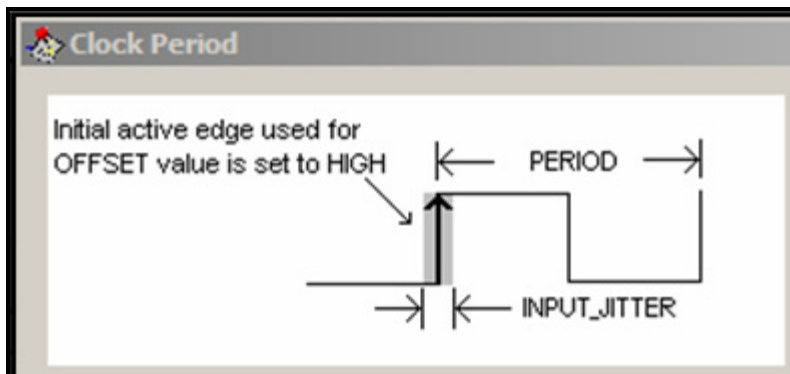- Data paths between synchronous elements only
- Does not cover
 - Cross clock domains between unrelated clocks





OFFSET IN BEFORE Constraint

■ OFFSET IN BEFORE



OFFSET = IN 5 ns BEFORE "MYCLK" ;

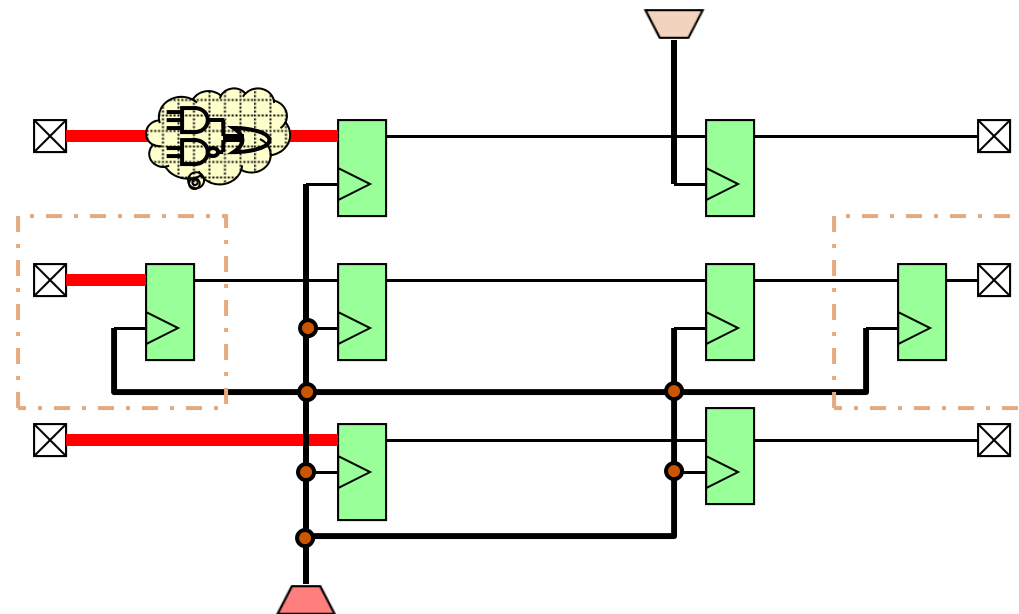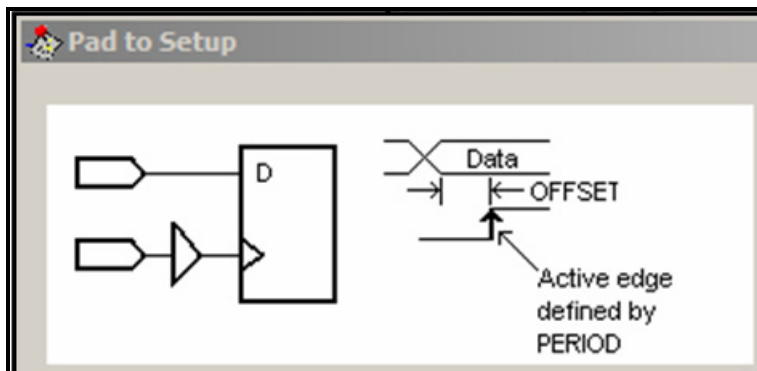- “The signal will be valid at the pad X nanoseconds before the clock appears at the clock pad...”
- Covers the first path to a synchronous element
- Recommendation for high performance:
 - Use the IOB registers



OFFSET OUT AFTER Constraint

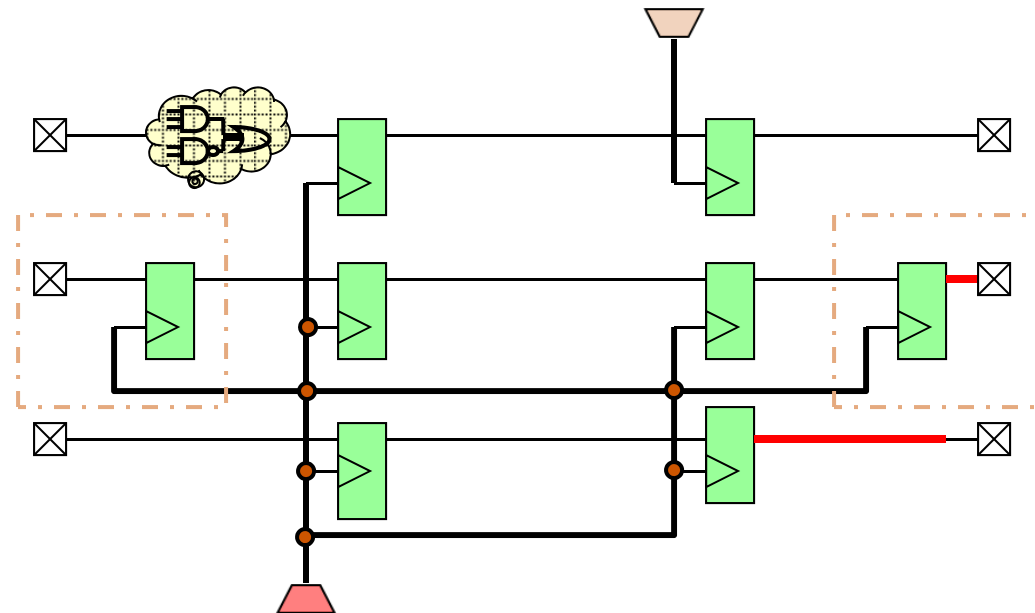
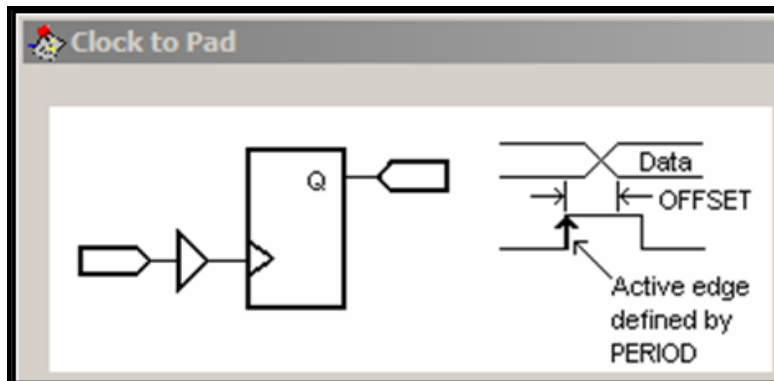
- **OFFSET OUT AFTER**
 - OFFSET = OUT 7 ns AFTER " MYCLK " ;*
 - “The signal will be valid at the pad X nanoseconds after the clock appears at the clock pad...”
 - Covers the last path from a synchronous element
 - **Recommendation for high performance:**
 - Use the IOB registers



UCF – User Constraints File

```
#  
#Global Clock Constraint  
# constrain net on external pin  
NET "CLK" TNM_NET = "CLK":  
TIMESPEC "TS_CLK" = PERIOD "CLK" 20 ns HIGH 50%  
#  
#Input Timing  
OFFSET = IN 8 ns BEFORE "CLK" ;  
#  
#Output Timing  
OFFSET = OUT 5 ns AFTER "CLK" ;  
#  
#Pad-pad combinatorial timing  
TIMESPEC "TS_P2P" = FROM "PADS" TO "PADS" 15 ns;  
#  
# Input timing exception from global input constraint  
NET "STRTSTOP" OFFSET = IN 3 ns BEFORE "CLK" ;
```

Timing Constraints Editor

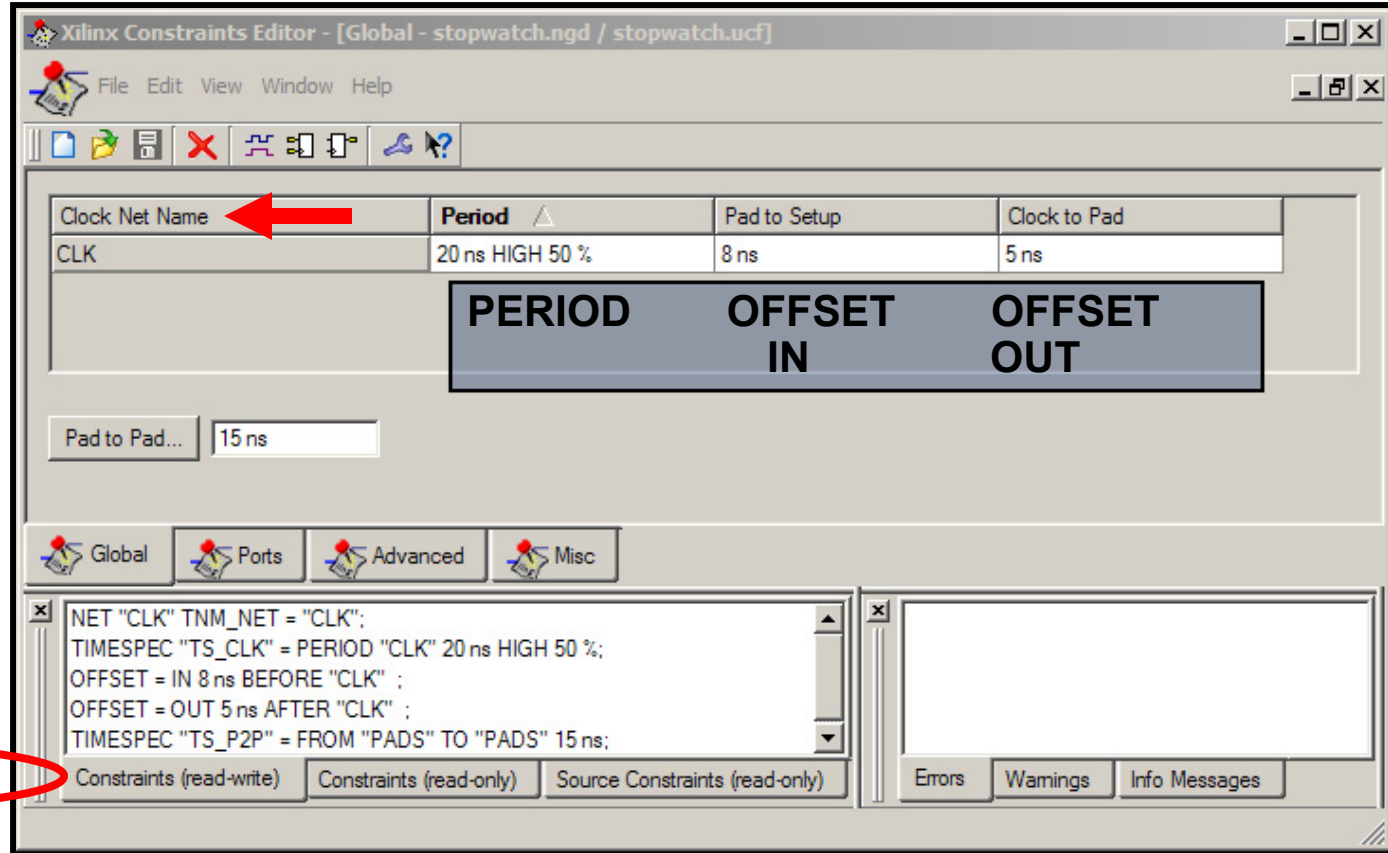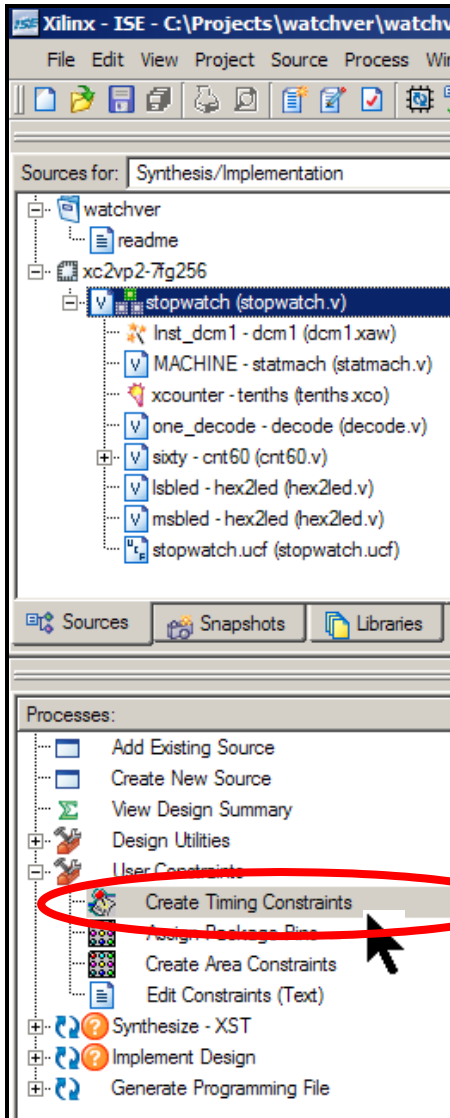

Timing Analysis

