


**EE 382M.8**  
**VLSI-II**  
**Non-Volatile Memory Design**  
**Spring 2017**

**Syed M. Alam ([salam@alum.mit.edu](mailto:salam@alum.mit.edu))**  
**Everspin Technologies, Inc.**


## Lecture Objectives

- 1) Understand technology, design, and application interaction
- 2) Learn fundamentals to pursue self-study and research

## Lecture Outline

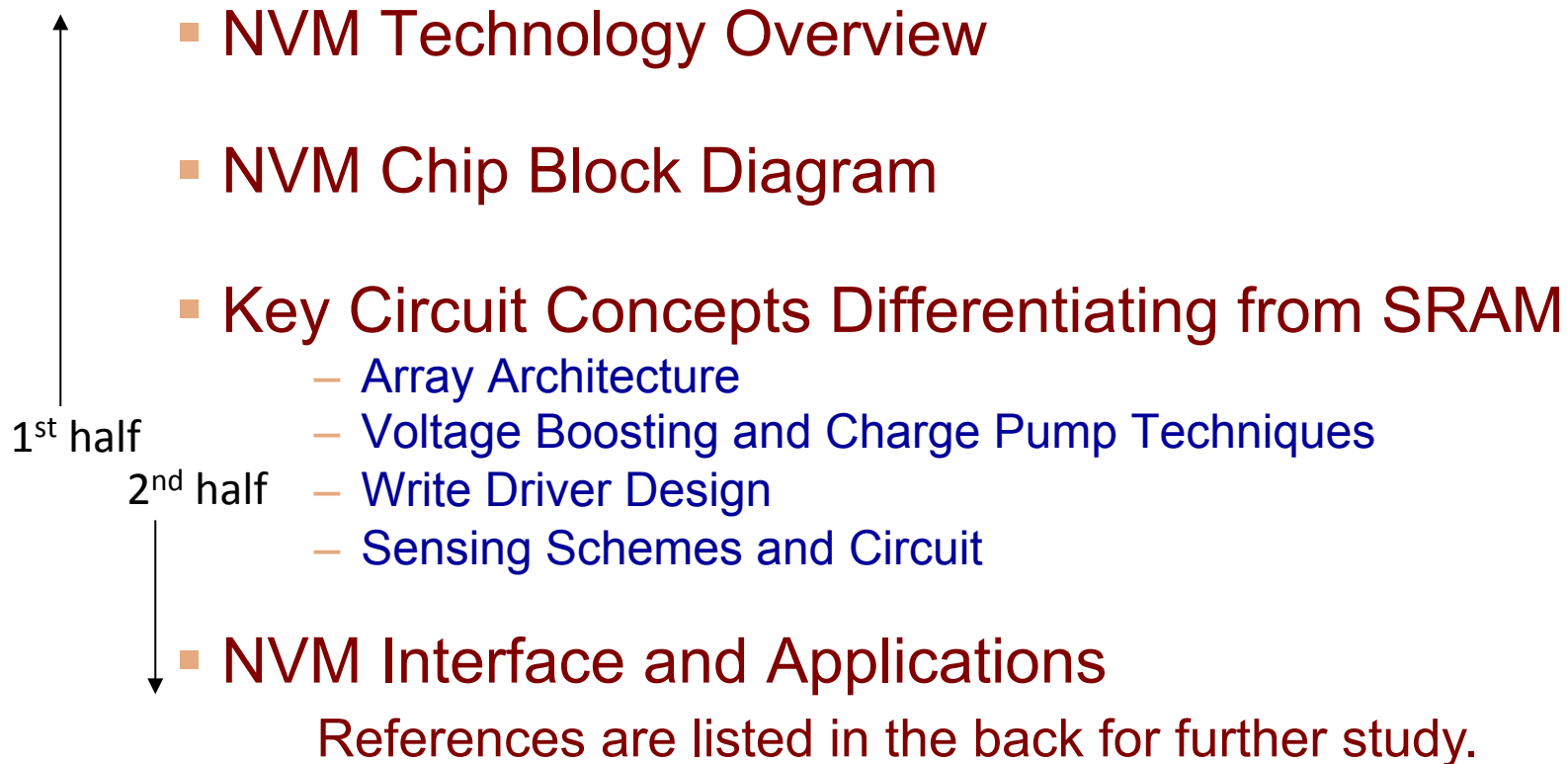
- 
- A diagram showing the lecture outline. A vertical line on the left has an upward-pointing arrow at the top and a downward-pointing arrow at the bottom. The text '1st half' is positioned to the right of the upward arrow, and '2nd half' is positioned to the right of the downward arrow. The outline items are listed to the right of this line, with the first three items (NVM Technology Overview, NVM Chip Block Diagram, and Key Circuit Concepts) corresponding to the 1st half, and the last item (NVM Interface and Applications) corresponding to the 2nd half. The sub-items under 'Key Circuit Concepts' are listed in blue text.
- NVM Technology Overview
  - NVM Chip Block Diagram
  - Key Circuit Concepts Differentiating from SRAM
    - Array Architecture
    - Voltage Boosting and Charge Pump Techniques
    - Write Driver Design
    - Sensing Schemes and Circuit
  - NVM Interface and Applications
- References are listed in the back for further study.

# Semiconductor Memory Types

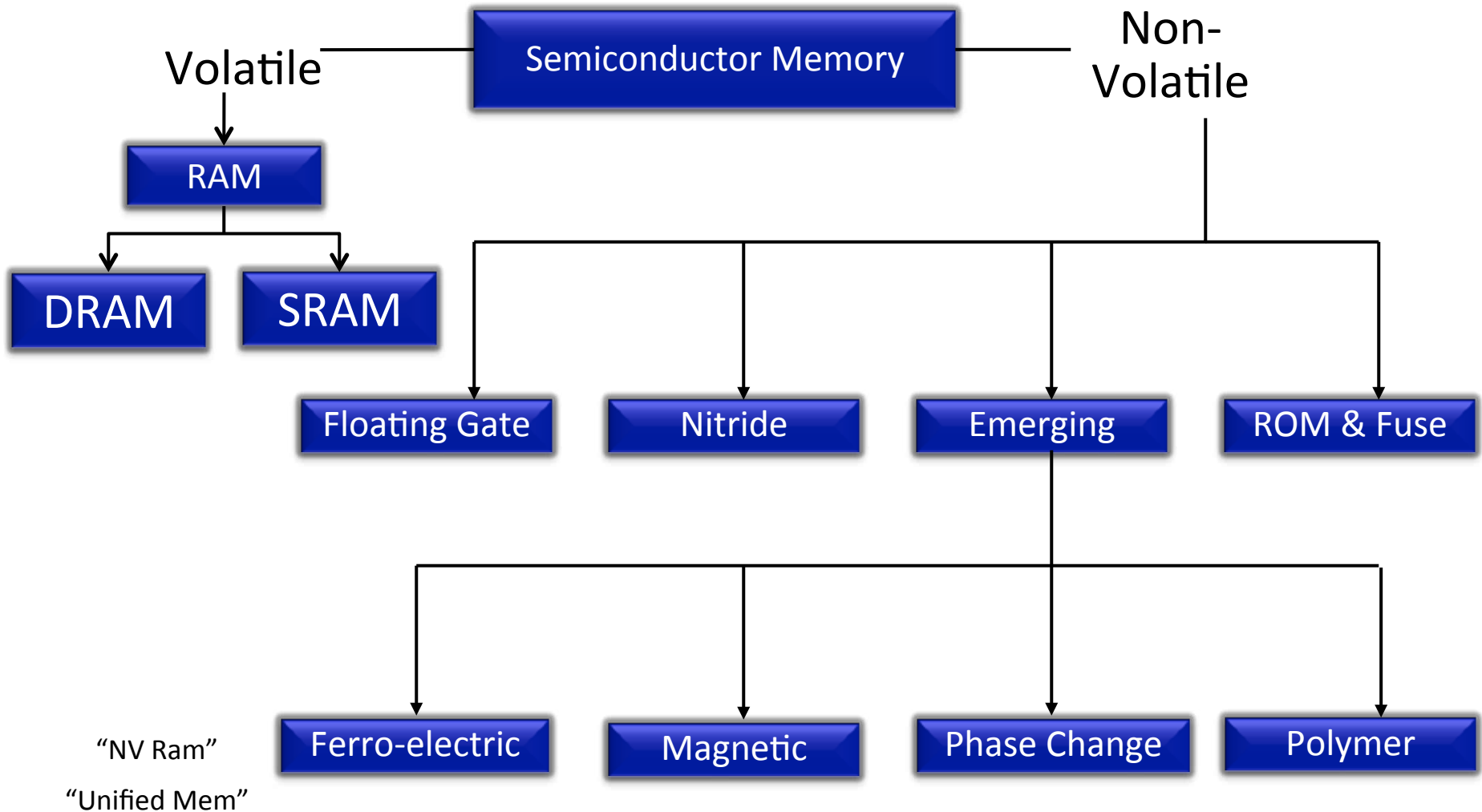

Courtesy Intel

# Non-Volatile Memory History

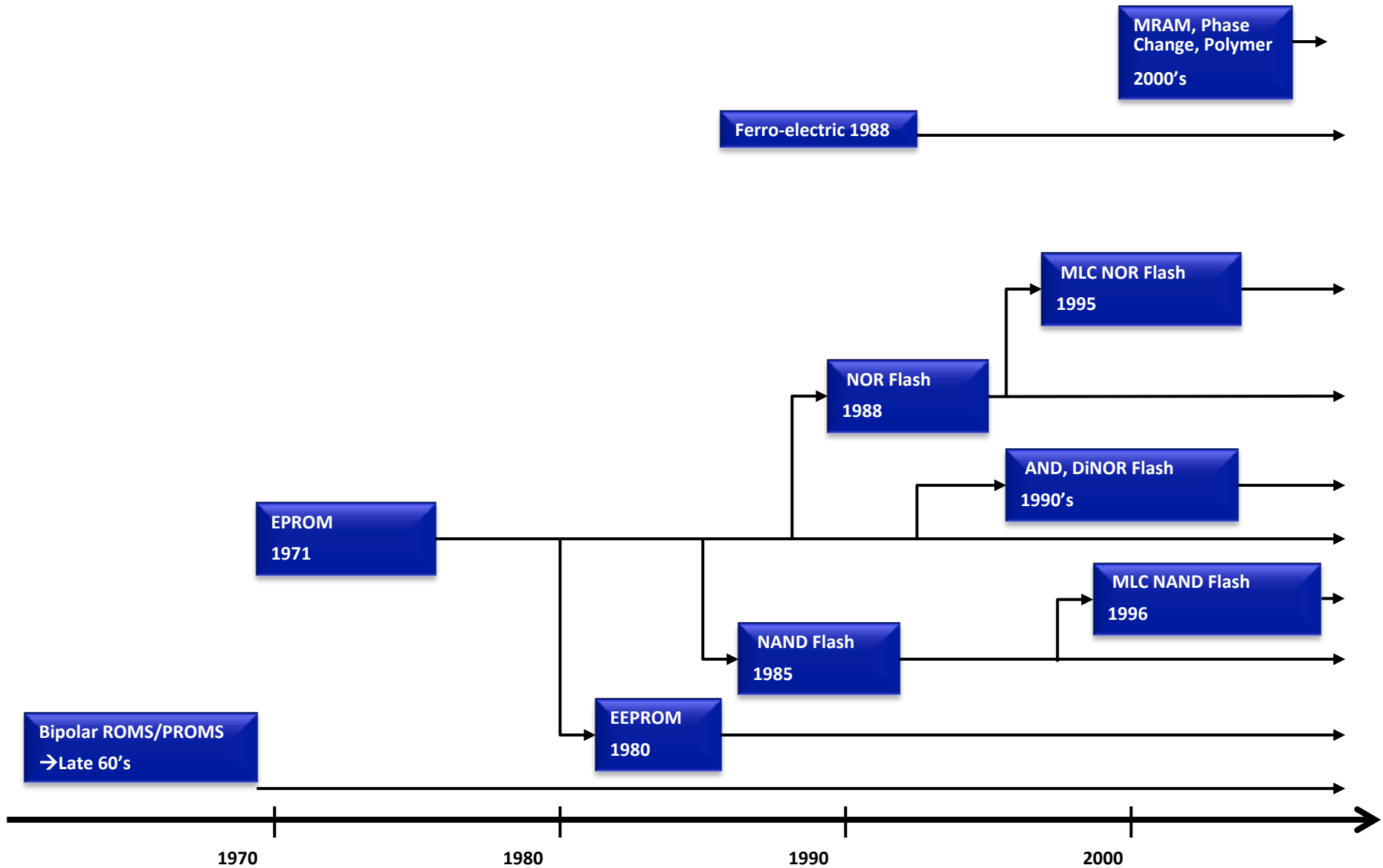

Courtesy Intel

MLC = Multi-Level Cell


# Understanding Key Memory Properties

Features	SRAM	PCRAM	STT-RAM	RRAM
Nonvolatility	No	Yes	Yes	Yes
Memory Cell Factor ( $F^2$ )	50-120	6-12	4-20	<1
Read Time (ns)	1	20-50	2-20	<50
Write/Erase Time (ns)	1	50-120	2-20	<100
Number of Rewrites	$10^{16}$	$10^{10}$	$10^{15}$	$10^{15}$
Power Consumption – Read/Write	Low	Low	Low	Low
Power Consumption – Other than R/W	Leakage Current	None	None	None

## Key Properties:

- Cell size:** Area defined in units of minimum feature ( $F$ )
- Access time:** Read / write latency. Also impacts bandwidth (bits/s)
- Access mode:** Random byte or block access. Impacts bandwidth.
- Endurance:** # of writes, program, erase, or read cycles.
- Retention:** Length of time memory bit holds the state.
- Power/Energy:** Write energy can be a concern.
- Cost per bit:** Has many facets including area, technology, test...
- Non-volatility:** Non-volatility and underlying storage mechanism
- Scalability:** Key to large density memory and cost reduction.

# Flash Memory Storage

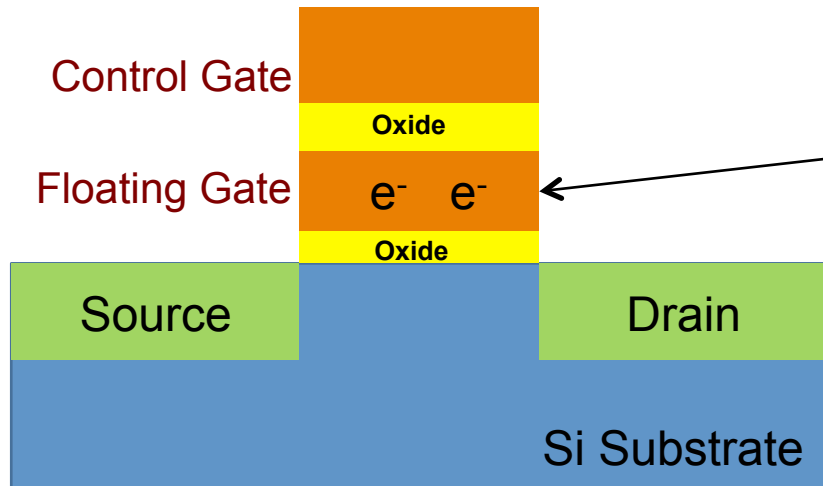


MOSFET device with floating gate

Very low density of trapped electrons

MOSFET  $V_{\text{threshold}}$  low

Memory state: Logic 1 or high

Erased cell

 


Very high density of trapped electrons

MOSFET  $V_{\text{threshold}}$  high


Memory state: Logic 0 or low

Programmed cell

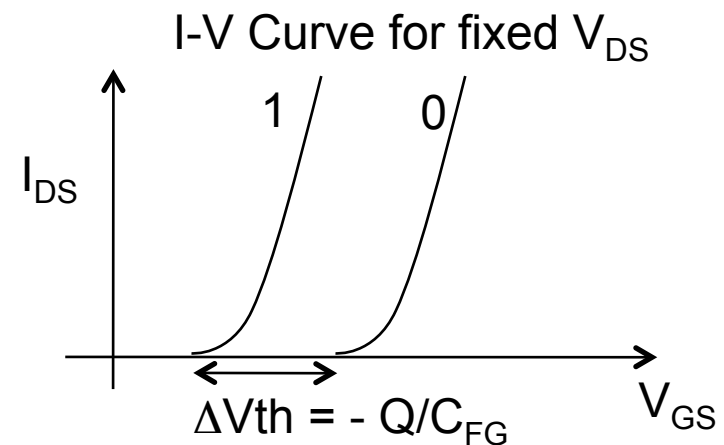


Ref. 1, 3

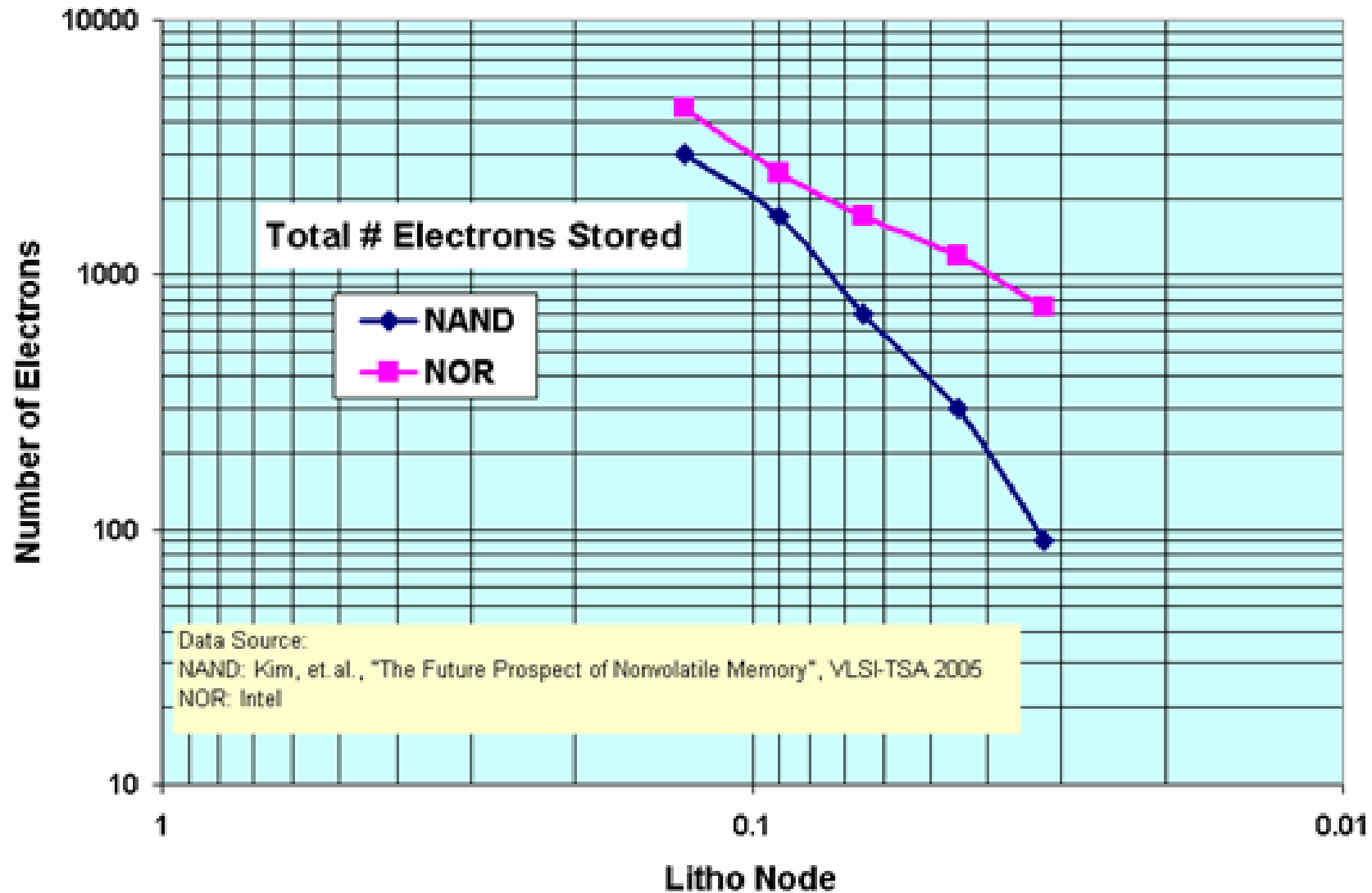
# Floating Gate Electrons vs. Lithography



# Single-Level Cell (SLC) vs. Multi-Level Cell (MLC)

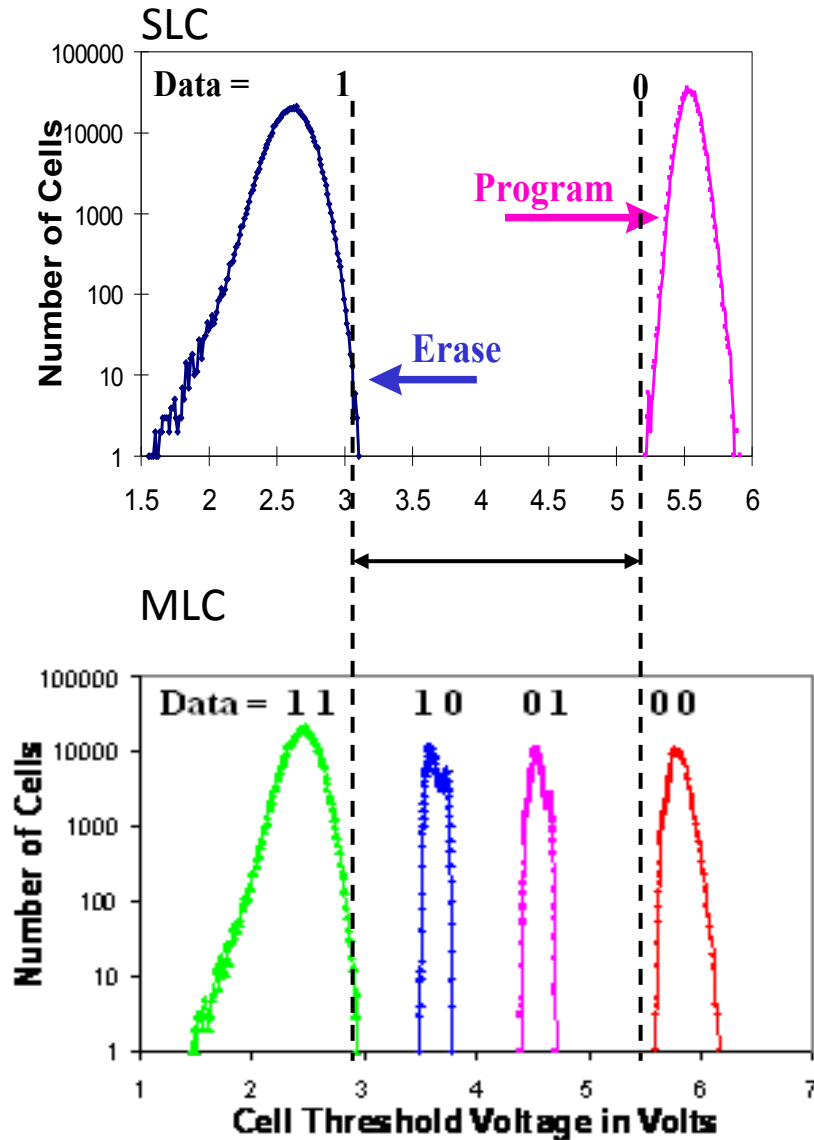 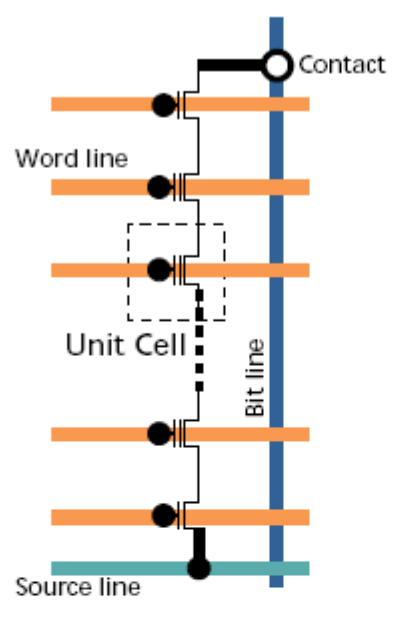
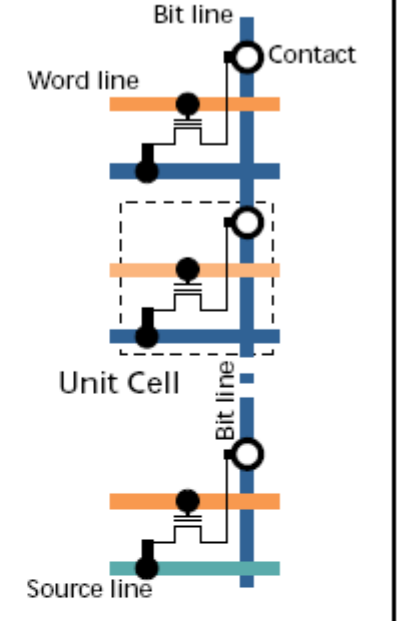
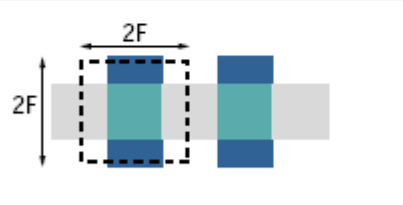
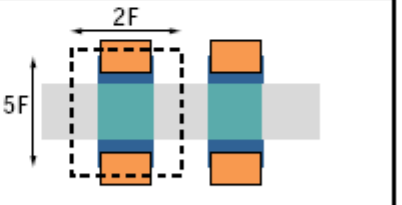

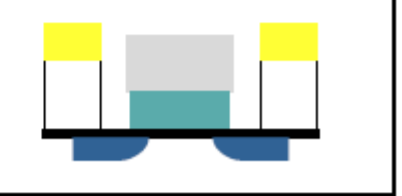


- Take advantage of the threshold voltage difference between the erased and programmed states of the single-level-cell case
  - Two levels = 1 bit/cell
  - Four levels = 2 bits/cell
  - In general:  $n \text{ bits/cell} = \log_2(\text{\#levels})$
- Need additional reference cells for program / read
  - One read reference cell for 1 bit/cell
  - Three read reference cells for 2 bits/cell
  - $N-1$  reference cells for  $n$  bits/cell
  - Corresponding reference cells for program




Courtesy Intel


# NAND vs. NOR Flash Array

	NAND	NOR
Cell Array		
Layout		
Cross Section		
Cell Size	$4F^2$	$10F^2$

### NAND Array Equiv. Circuit

 


### NOR Array Equiv. Circuit

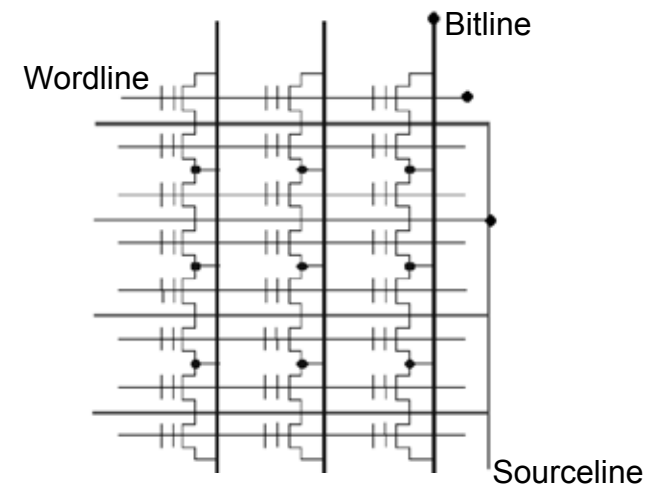

# NAND vs. NOR Program and Erase Examples


**Program**

**NAND**

 


Fowler-Nordheim (FN)  
Tunneling (low current)  
e.g. 1 cell = 5nA

**NOR**

 


Channel Hot Electron  
High current  
e.g. 1 cell = 0.1mA

**Erase**

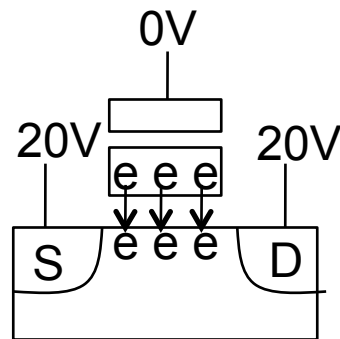

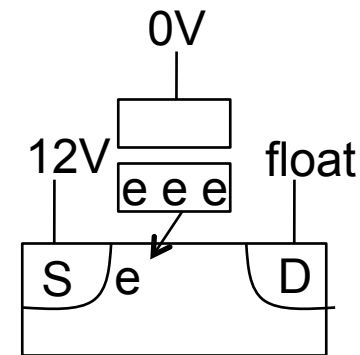Uniform FN Tunneling  
(can also float S,D and raise B to ~20V)



Local FN Tunneling

# Flash Key Memory Parameters

Example Micron Flash Memory Products

Characteristic	NAND Flash: MT29F2G08A	NOR Flash: TE28F128J3
Random access READ	25 $\mu$ s (first byte) 0.025 $\mu$ s each for remaining 2111 bytes	0.075 $\mu$ s
Sustained READ speed (sector basis)	26 MB/s (x8) or 41 MB/s (x16)	31 MB/s (x8) or 62 MB/s (x16)
Random WRITE speed	$\approx$ 220 $\mu$ s/2112 bytes	128 $\mu$ s/32 bytes
Sustained WRITE speed (sector basis)	7.5 MB/s	0.250 MB/s
Erase block size	128KB	128KB
ERASE time per block (TYP)	500 $\mu$ s	1 sec


**Access Time**

**Access Mode**


**Retention:** Bit flipping due to leakage, radiation.

**Endurance:** Fail mechanism is oxide forming electron traps with cycling.  $\sim 10^6$  cycles. Apply wear leveling and ECC to increase lifetime.

 **Scalability:** Tunnel oxide thickness scaling is the limit. Multi-level cell and new materials for scaling.





# Phase Change Memory (PCM)

 

Chalcogenide sandwich  
 $\text{Ge}_2\text{Sb}_2\text{Te}_5$  : GST  
 Germanium Antimony  
 Tellurium

Phases:	Crystalline	Amorphous
Resistance:	Low ( $\text{k}\Omega$ )	High ( $\text{M}\Omega$ )
Logic state:	Logic 0	Logic 1
Programming Methods:	Set current pulse Anneal $T_{\text{crys}} < T < T_{\text{melt}}$	Reset current pulse Melt->cool fast

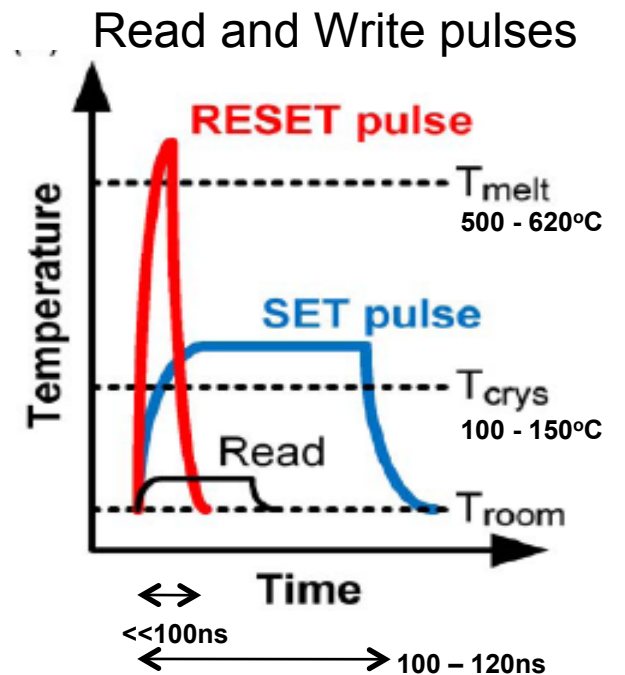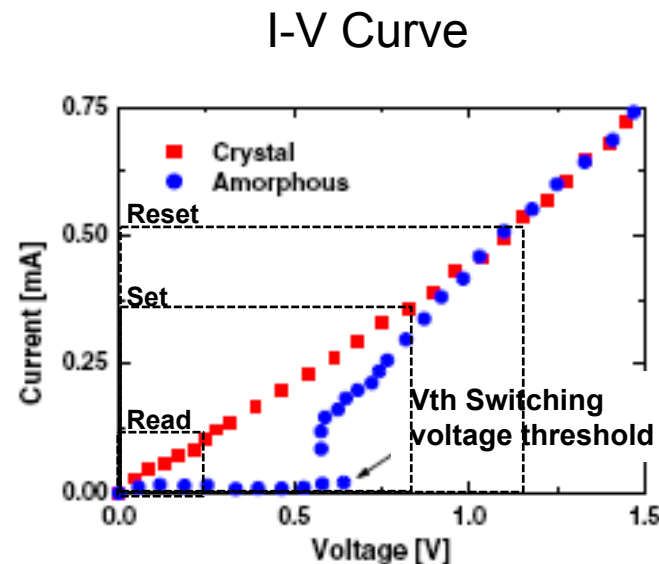

Ref. 4, 5

# PCM Key Memory Parameters

**Endurance:** Stuck open or short due to stress and void formation at bottom interface upon cycling.  $10^9$ -- $10^{12}$  cycles of endurance

**Retention:** Bit flipping due to thermal disturbance. 10 years retention of crystalline state requires operation below  $110^\circ\text{C}$ .

## Scalability:

Write current reduces with smaller geometry !!

$$\Delta T = P \times R_{th} \quad \text{where} \quad P = V_{GST} \times I_{GST}$$

$$\text{Therefore} \quad I_{GST} = \Delta T / (V_{GST} \times R_{th})$$

$$R_{th} \propto \text{contact area}$$

$\Delta T$  temperature rise for writing

$P$  joule heating power


$R_{th}$  thermal R to metal sink

$V_{GST}$  voltage across GST cell

$I_{GST}$  current through GST cell

$\Delta T$  and  $V_{GST}$  are physical quantities that do not scale.


Thermal disturbance is a scaling limit.

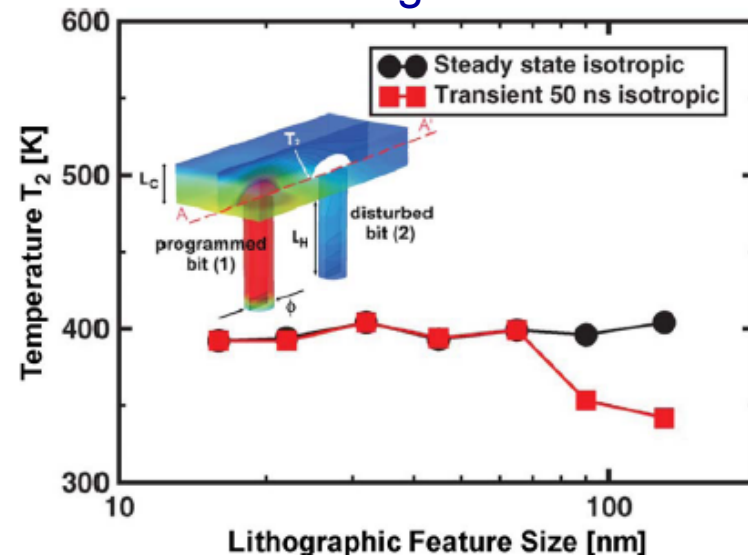

Constant  $V_{GST}$  can be a CMOS reliability limit.

# Resistive Random Access Memory (RRAM)

Metal Insulator Metal  
MIM structure

 


	<b>Examples</b>
Top electrode	Pt, TiN/Ti, TiN, Ru, Ni ...
Transition Metal Oxide	TiO <sub>x</sub> , NiO <sub>x</sub> , HfO <sub>x</sub> , WO <sub>x</sub> , TaO <sub>x</sub> , VO <sub>x</sub> , CuO <sub>x</sub> , ...
Bottom Electrode	TiN, TaN, W, Pt, ...

## Basic Idea:

- Normally insulating dielectric (metal oxide) is made to conduct through a filament formed by applying a sufficiently high voltage.
- Filament is reset or broken for high resistance
- Filament is set or formed for low resistance


# RRAM Switching Mechanism Example

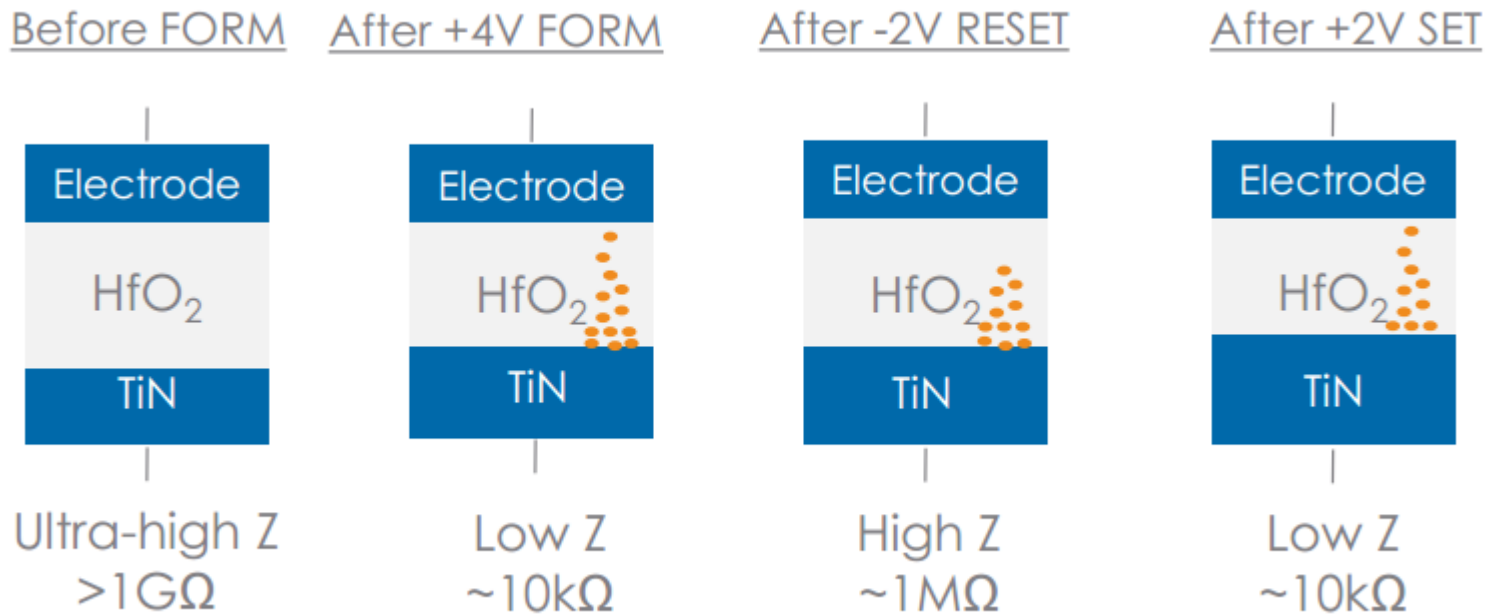

Ref. 14

Oxygen vacancies are created by hot electrons. Conductive filament is made of Oxygen vacancies.

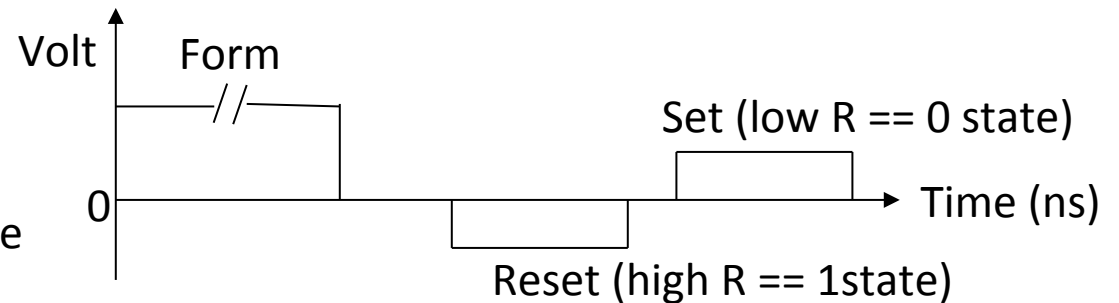Bipolar switching  
Set / Reset pulse widths are  
5-100ns



# RRAM Key Parameters


Bipolar RRAM Devices	Repeatable Results
Write Voltage	<2.5V
Write Current	~20-100uA
Switching Time	<10ns
Endurance	$10^6$ ( $10^{10}$ reported in IEDM)
Data Retention at 85C	1 year with 20-50uA 10 years with 100uA

Rambus RRAM Status [14]:

# RRAM Device Specs from reported literature


	ITRI, IEDM 2008	NEC, VLSI 2010	Panasonic, IEDM 2008	Univ. + IMEC, IMW 2010	Fujitsu, IEDM 2007
Device	TiN/Ti/HfO <sub>x</sub> /TiN	Ru/TiO <sub>x</sub> /TaO <sub>x</sub> /Ru	Pt/TaO <sub>x</sub> /Pt	Au/NiO <sub>x</sub> /TiN	Pt/Ti-doped NiO/Pt
Test chip	1T-1R	1T-1R	1T-1R	1T-1R	1T-1R
Polarity	Bipolar	Unipolar	Bipolar	Unipolar	Unipolar
Reset	2V, 25uA	0.65V, 200uA	1.5V, 100uA	0.5V DC, 9.5uA	1.9V, 100uA
Set	2.3V	2.8V	2V	2.7V DC	2.8V
Form Voltage	3V	?	?	3.7V DC	3V
Switching Time	<10ns	<1us	<100ns	NA	10ns
On/off ratio	~100x	100x	10x	5x-10x	90x
Endurance, Data Retention	10 <sup>6</sup> , 10 years	10 <sup>5</sup> , 10 years	10 <sup>9</sup> , 10 years	130 cycles, ?	100, 10 years
Comments	Typical data	Worst case data	Typical data	Typical data	Typical
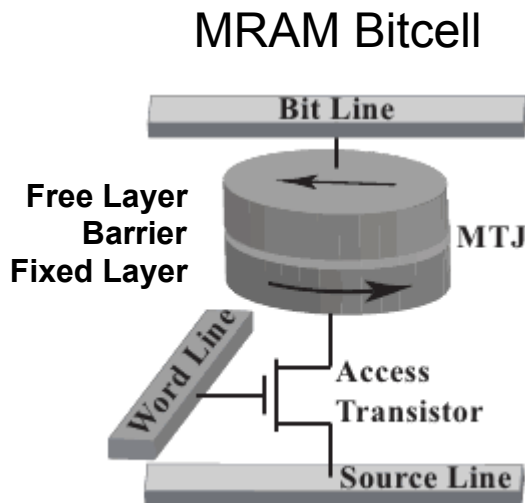
# Magnetoresistive Random Access Memory (MRAM)



- Sandwich of magnetic (CoFeB ) fixed and free layers with oxide (AlO or MgO) barrier in between
- Magnetic Tunnel Junction (MTJ) with Anti-parallel: Logic 1 – high resistance  
Parallel: Logic 0 – Low resistance
- Spin Transfer Torque (STT) current based switching between logic states
  - Direct torque transfer (Logic 1 to 0 switch)
  - Reflective torque transfer (Logic 0 to 1)
- TMR (tunnel magnetoresistance) read


R-I Curve

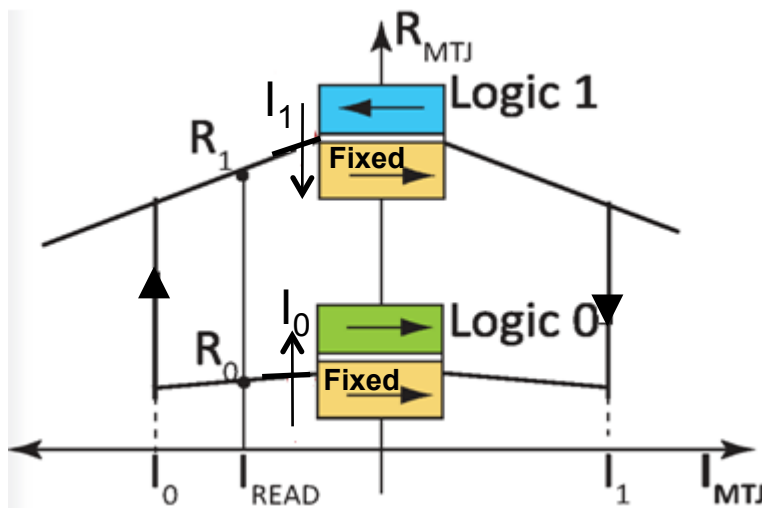

$$TMR = \frac{R_1 - R_0}{R_0}$$

Typical TMR with MgO barrier is >100%

# MRAM Bitcell

 


MRAM module

Magnetic Tunnel Junction (MTJ)


No Impact on CMOS !

Cross-sectional view

 


Circuit

MTJ Layers

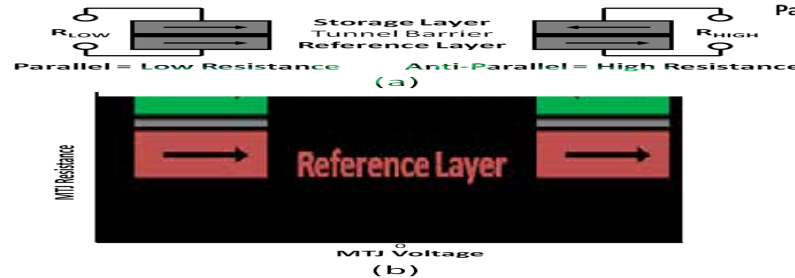

MTJ R vs. V

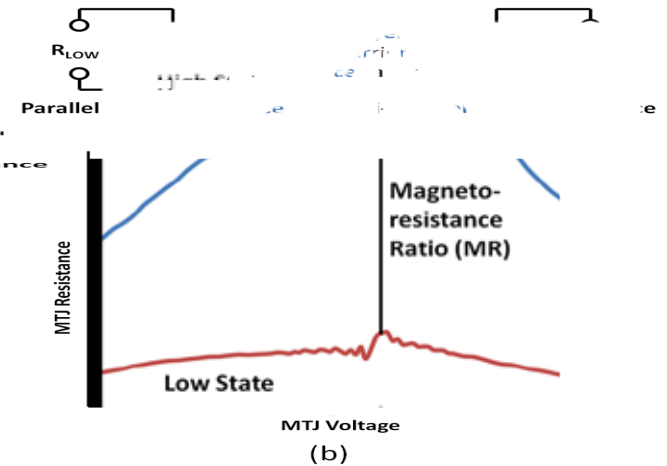


# Spin-Torque MRAM – Next Generation MRAM


Current Generation MRAM uses a magnetic field for switching  
*Limits scaling due to constant magnetic field*

**Next generation MRAM enables scaling to Gb densities**


## Toggle Write

 

## Spin-Torque Write

 


# Writing in Spin-Torque MRAM

 


## Bi-directional current through the MTJ
 
### Advantages:

- Switching current scales with smaller cell size.
- Lower write current (100s uA instead of >10mA per axis in Toggle MRAM)



 AP-to-P Switching (Write 0)  
Direct Spin-torque transfer




P-to-AP Switching (Write 1)  
Reflected electron  
Spin-torque transfer


 
# MRAM Key Memory Parameters

**Endurance:** Stuck-at low due to time-dependent dielectric breakdown.  $>10^{12}$  cycles of endurance expected. Need separation between  $V_c$  and  $V_{bd}$  distributions

**Retention:** Bit flipping due to low energy barrier to switching,  $E_b$ .



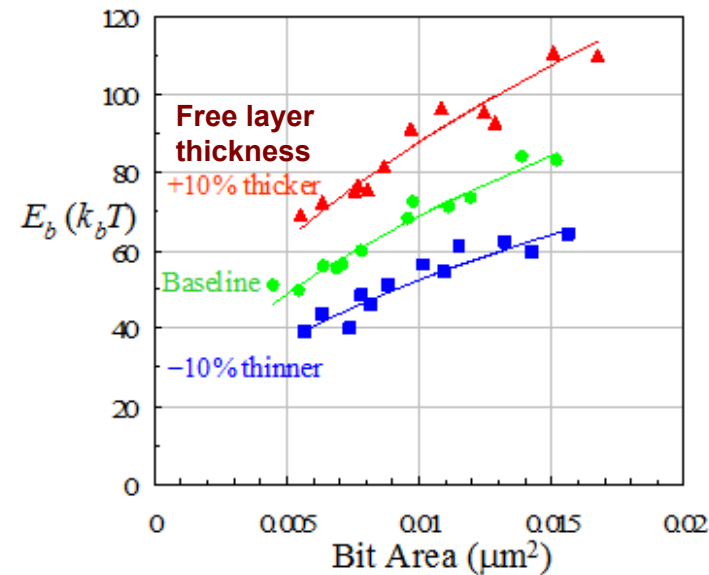 **Scalability:** Smaller  $A \rightarrow$  lower  $V_c \rightarrow$  lower  $E_b \rightarrow$  wider  $R_{MTJ}$  distributions




Ref. 6,7

6F<sup>2</sup> cell is possible with scaling

Research  to  for increased  $E_b$

# Storage Capacity Trend

## Non-Volatile Memory Trend

 

Storage capacity trend of emerging non-volatile memories.

Source: ISSCC

# Summarizing Key Properties from ITRS

	Volatile			Non-volatile				
	SRAM	DRAM		Flash		FeRAM	STT-MRAM	PCM
		Stand-alone	Embedded	NOR Embedded	NAND Stand-alone			
Storage mechanism	Inter-locked logic state	Charge on a capacitor		Trapped charge in floating gate or gate insulator		Polarization in a ferroelectric capacitor	Magnetization of ferrromagnetic layers	Amorphous and crystalline phases
Cell element	6T	1T1C		1T		1T1C	1T1R	1T1R / 1D1R
Feature size, F, nm	45	36	65	90	22	180	65	45
Cell area F <sup>2</sup>	140	6	12 - 30	10	4	22	20	4
Read time	0.2 ns	<10 ns	2 ns	15 ns	0.1 ms	40 ns	35 ns	12 ns
Write / Erase time	0.2 ns	<10 ns	2 ns	1 us / 10 ms	1 ms / 0.1 ms	65 ns	35 ns	100 ns
Retention	-	64 ms	4 ms	10 y	10 y	10 y	> 10 y	> 10 y
Endurance cycles	> 1E16	> 1E16	> 1E16	1E5	1E4	1E14	> 1E12	1E9
Write operating voltage V	1	2.5	2.5	10	15	1.3 - 3.3	1.8	3
Read operating voltage V	1	1.8	1.7	1.8	1.8	1.3 - 3.3	1.8	1.2
Write energy J/bit	5E-16	4E-15	5E-15	1E-10	2E-16	3E-14	2.5E-12	6E-12


Emerging technology: ReRAM (resistive switching in metal-insulator-metal)

Ref. 2

- NVM Technology Overview
- **NVM Chip Block Diagram**
- **Key Circuit Concepts Differentiating from SRAM**
  - Array Architecture
  - Voltage Boosting and Charge Pump Techniques
  - Write Driver Design
  - Sensing Schemes and Circuit
- NVM Interface and Applications
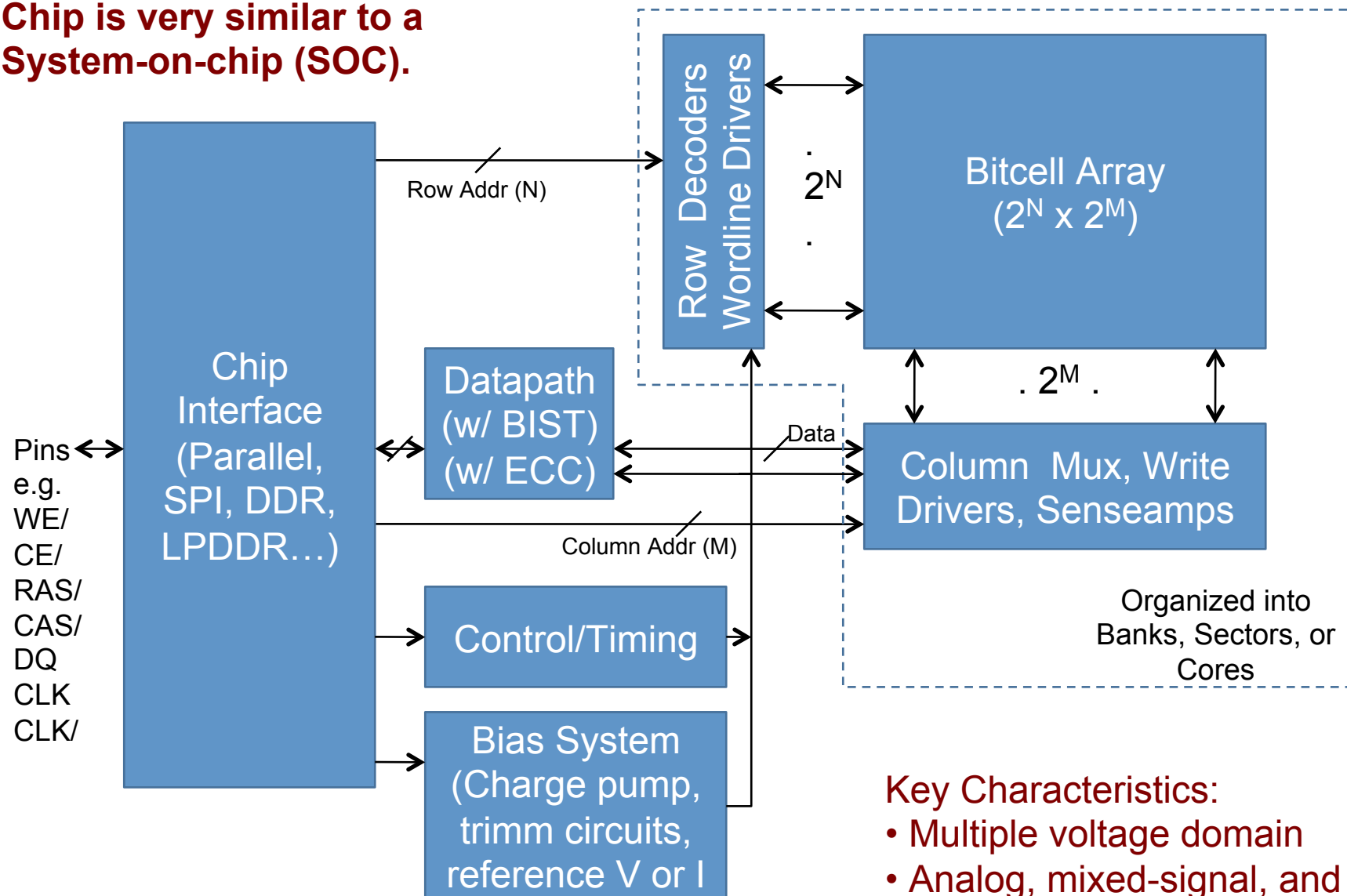
# NVM Chip Generic Block Diagram

Chip is very similar to a System-on-chip (SOC).




## Key Characteristics:


- Multiple voltage domain
- Analog, mixed-signal, and digital
- Regular and area efficient layout

# Memory Array and Cell Selector Choices

Cross-point Array

 

MOS/BJT select-device Array

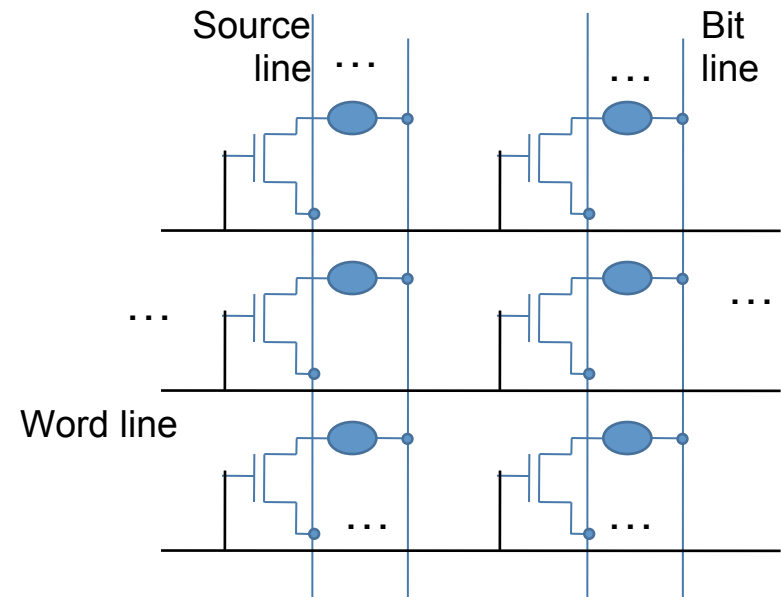


**Array density is mostly determined by memory cell selector size !!**

	<b>PN diode</b>	<b>MOSFET</b>	<b>BJT</b>
Bidirectional current:	No	Yes	No
Current drive:	8-30 MA/cm <sup>2</sup>	800uA-1.2mA/um-W	8-30 MA/cm <sup>2</sup>
Cell size:	~4F <sup>2</sup>	17-22F <sup>2</sup>	5-8F <sup>2</sup>



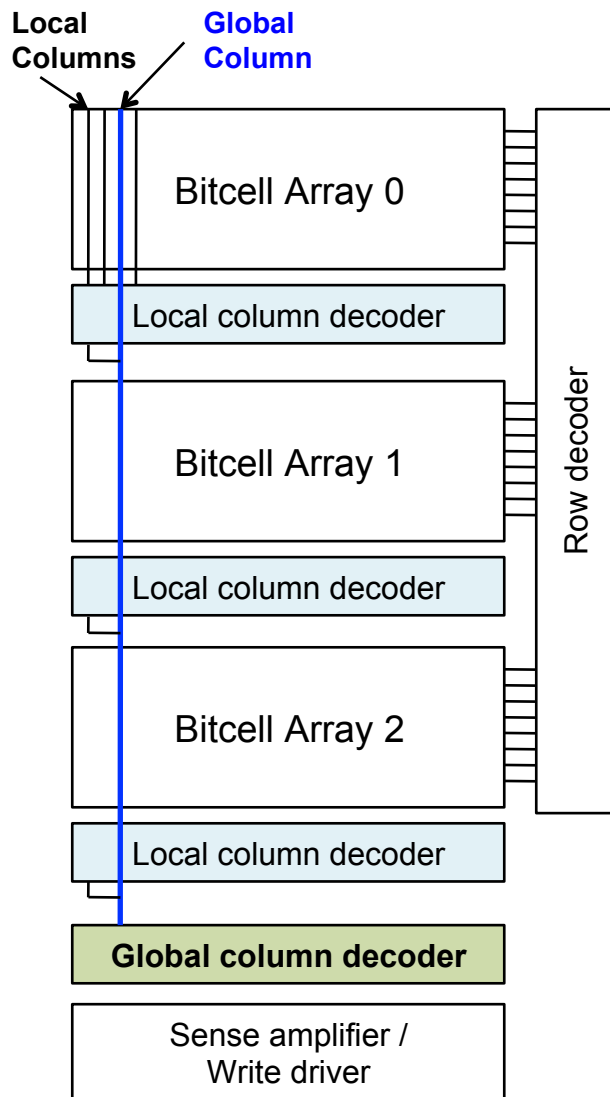
# Memory Column Selection Scheme

Global-local scheme increases bitcell array to circuit area ratio



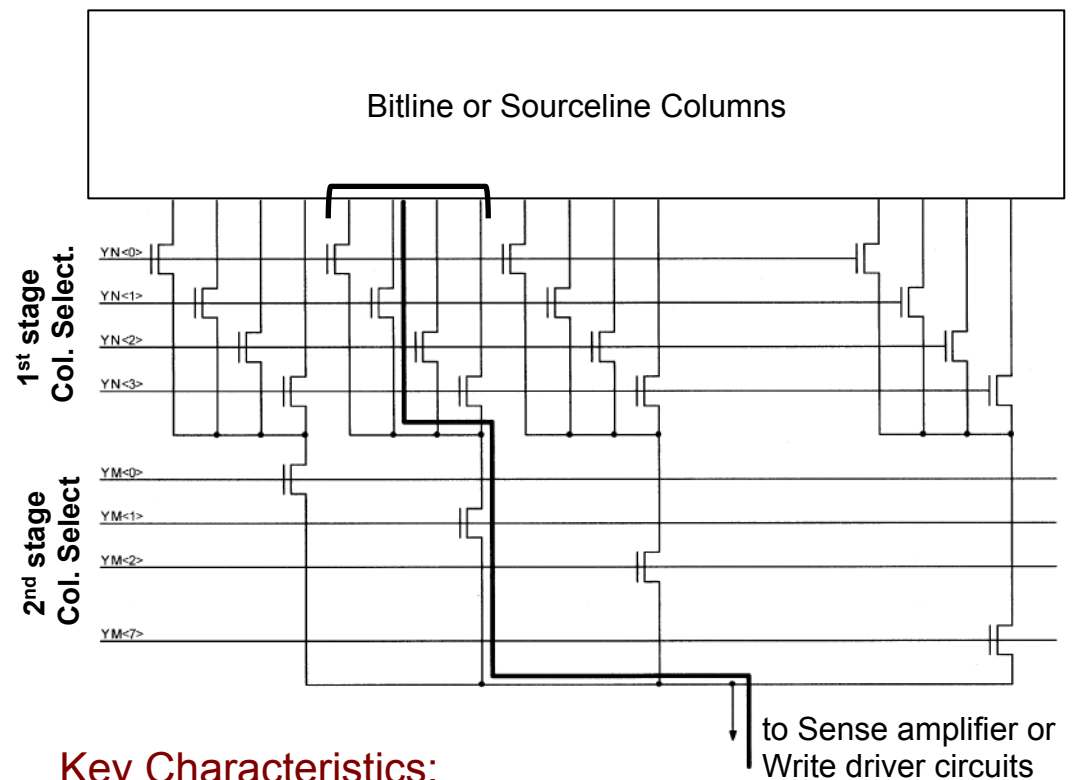Schematic of a two-stage Column Selection Circuit





Key Characteristics:

- Two-stage reduces capacitive load of column decode signals and column circuit
- Pitch-matched layout with bitcell columns
- Prefer NMOS transistor . Why?

Drawback: higher resistance in column path
 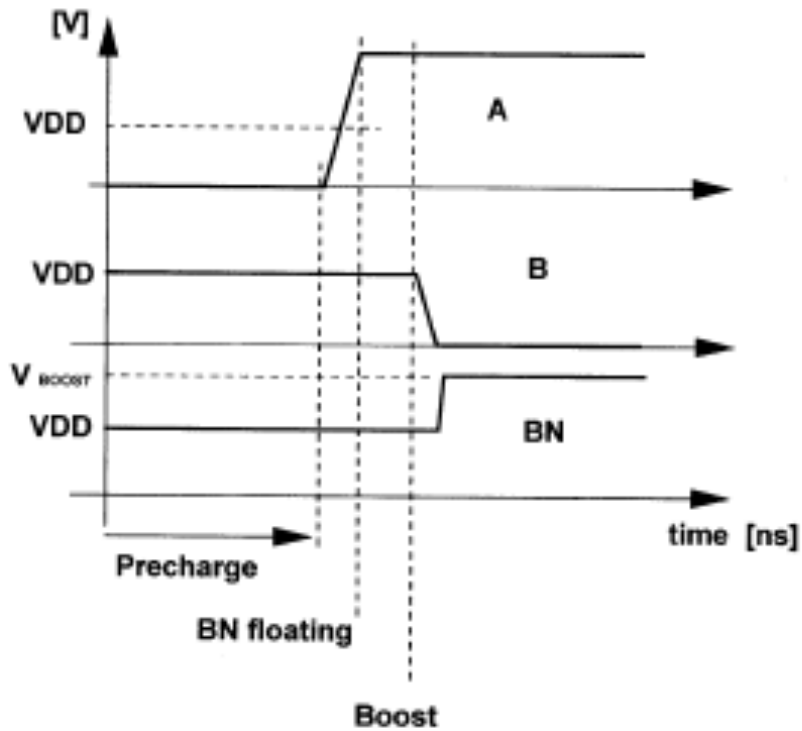
# Voltage Boost Technique: Basic Principal



Why need  
 $V_A \geq V_{BN}$   
 during boost?

Due to charge conservation  
 Initial charge = final charge

$$Q_i = Q_f$$


$$Q_i = (C_B + C_L) \cdot VDD$$

$$Q_f = C_B \cdot (V_{BN} - VDD) + C_L \cdot V_{BN}$$


$$V_{BN} = VDD + \frac{C_B}{C_B + C_L} \cdot VDD$$
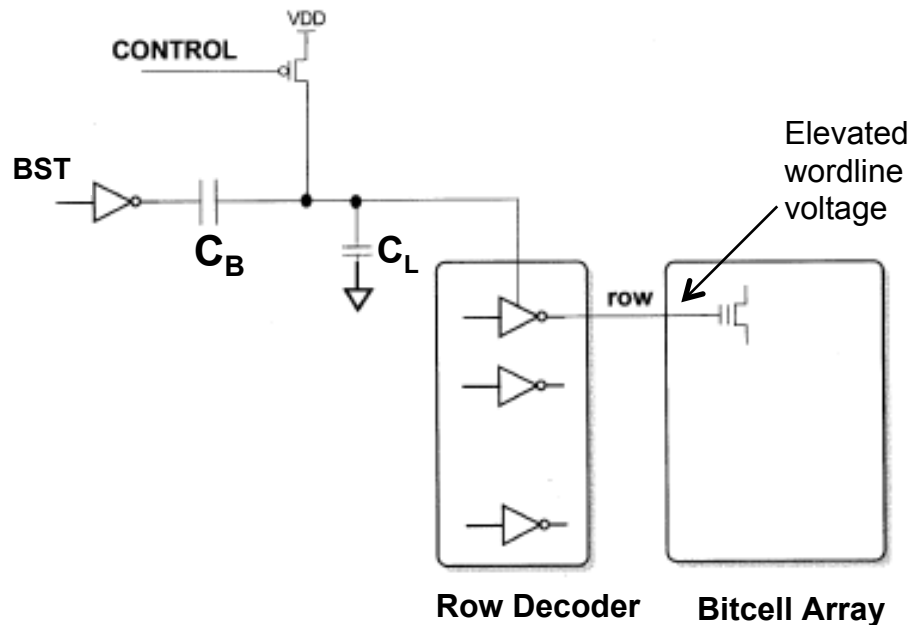
# Voltage Boost Techniques in Use

Boosted voltage and charge pumped voltage are used in row (word line) decoders for reading and writing.



A boosted voltage supply generator

 


One shot boost circuit for row decoders:

- Find required  $C_B$  for  $C_L$ .  $C_B$  can be large!
- Can use local boost circuit per row.




Further study: Ref. 1

Continuous boost circuit techniques

 

# Voltage Doubler Circuit

Basic Operating Principal:

   

Voltage doubler with PMOS output stage  
Key advantages:

- Cascade to pump to higher supply
- Simple clock phase generators
- Can use “low voltage” transistors. Why?

Further study: Dickson charge pump, Ref. 1

# Lecture Outline

---


- NVM Technology Overview
- NVM Chip Block Diagram
- Key Circuit Concepts Differentiating from SRAM
  - Array Architecture
  - Voltage Boosting and Charge Pump Techniques
  - **Write Driver Design**
  - Sensing Schemes and Circuit
- NVM Interface and Applications

# Basic Write Driver Scheme

Applies to wide range of resistive memories:

Bi-direction writes in STT-MRAM, ReRAM / Memristor and uni-direction writes in PCM


## Example Write Driver for STT-MRAM

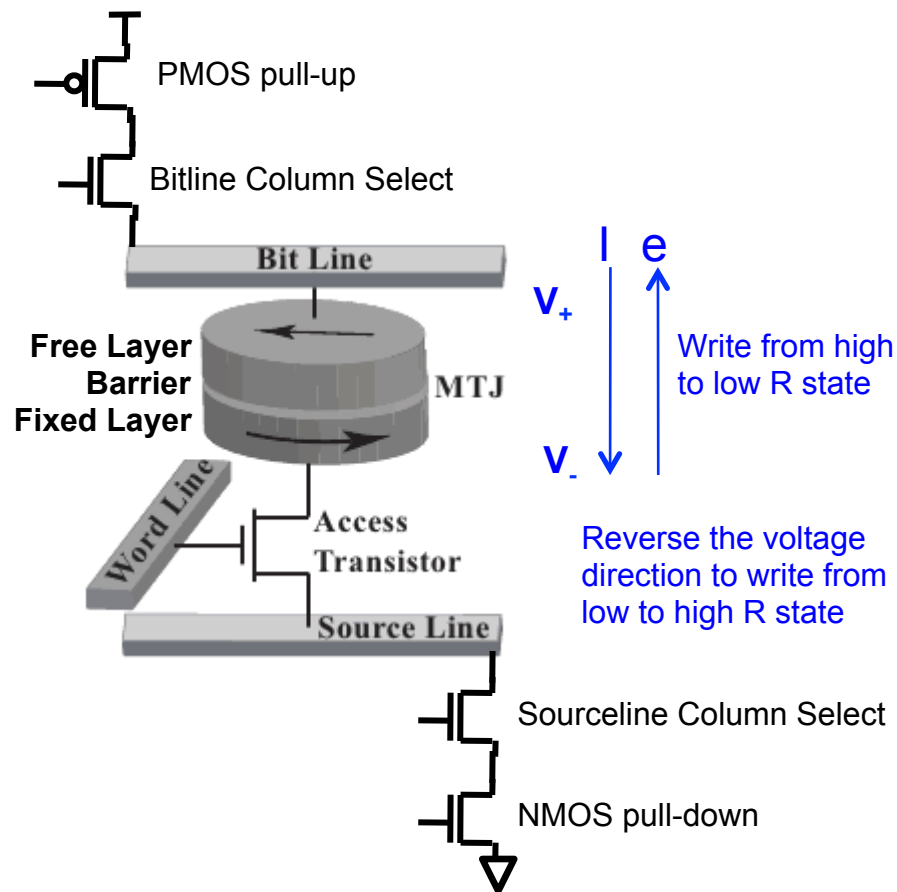

Bitline Column Select Drive strength:

- Want  $V_{\text{bitline}}$  as close to VDD

However

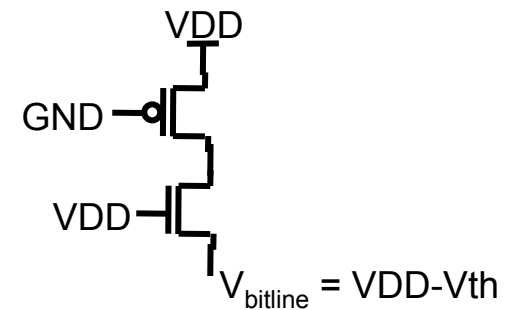


Can use PMOS for uni-direction writes.

Need a solution for bi-direction writes


- Charged pumped Column Select signals.
- Auto-bootstrap
 
# Auto-Bootstrapped Column Selection

2-step  $V_{gate}$  during column selection:  
 $VDD \rightarrow \text{Float}$




Step 1

 

Step 2

Column Select transistor MN I-V Curve:

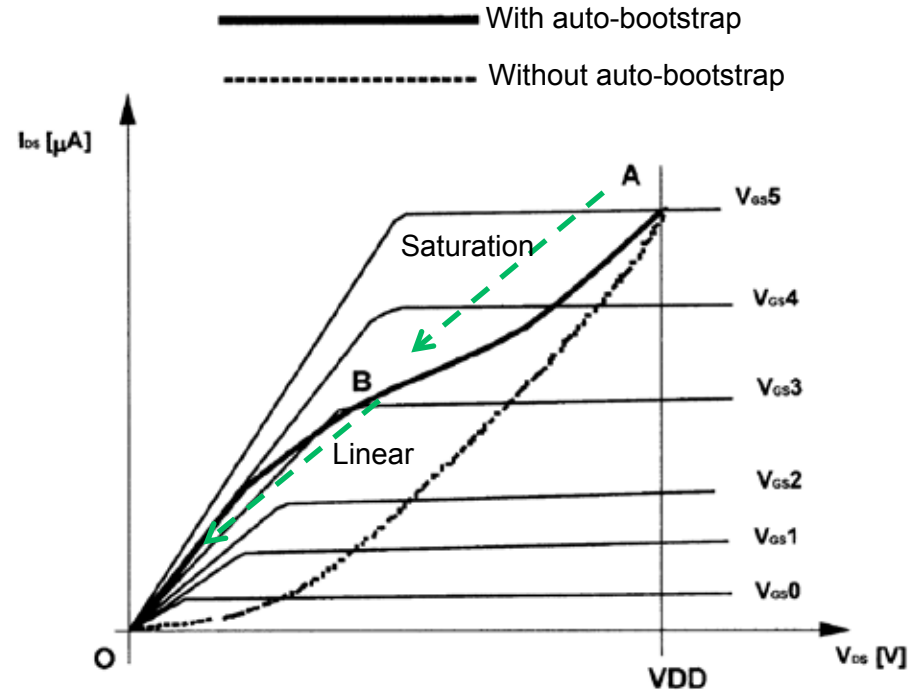

Can apply in single stage column selection.

Why not in 2-stage column selection?

- Additional  $C_{load}$  to fixed nodes at the gate.


Further study: Ref. 1

General bootstrap concept

Bootstrapped Output Drivers

Still do not follow the ideal I-V curve. Why?

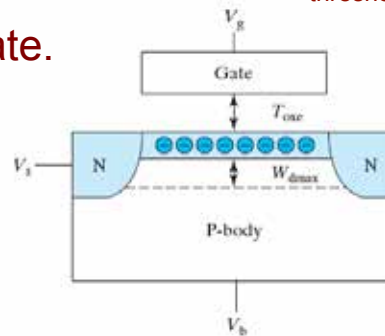- $V_{threshold}$  increases due to body effect.






$$V_{th}(V_{sb}) = V_{th0} + \frac{C_{dep}}{C_{oxe}} V_{sb}$$

Ref. 8



# Fundamental Approach 1: Voltage Sensing

Basic operating principal: Sense the voltage difference from any one of

   - 1) a fixed current bias through different bit states in for e.g. resistive memories.
- 2) voltage swing due to charge sharing in for e.g. DRAM.
- 3) differential voltage swing in bitline and bitline\_b from active driver in for e.g. SRAM.
- 4) RC time constants of charging or discharging bitcell in for e.g. resistive memories


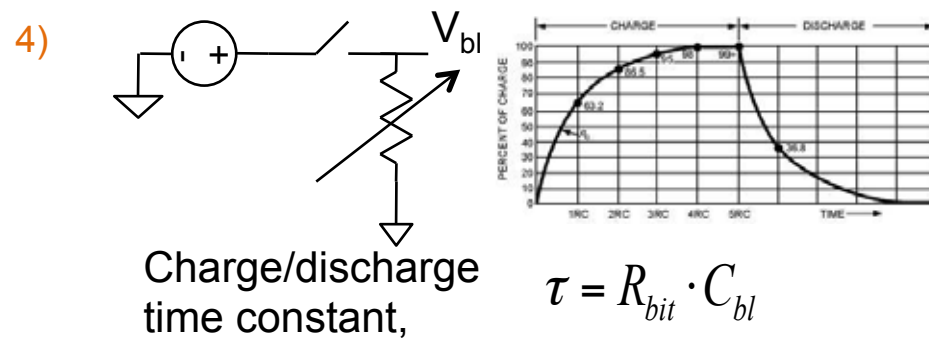 
## Example Differential Voltage Sense Amplifier



# Fundamental Approach 2: Current Sensing


Basic operating principal:

- Apply a fixed voltage bias across the bit.
- Sense the resulting current.
- Resolve the bit state by comparison with reference current.

Used for sensing in:



- Flash memory: fixed drain bias for flash cells of different  $V_{th}$ .
- MRAM: Control Magnetic Tunnel Junction (MTJ) bias for high MR and to avoid bit flipping.
- Any resistive memory for controlled bias across the bit to avoid stress and bit flipping.

Current Sensing Amplifier Circuit

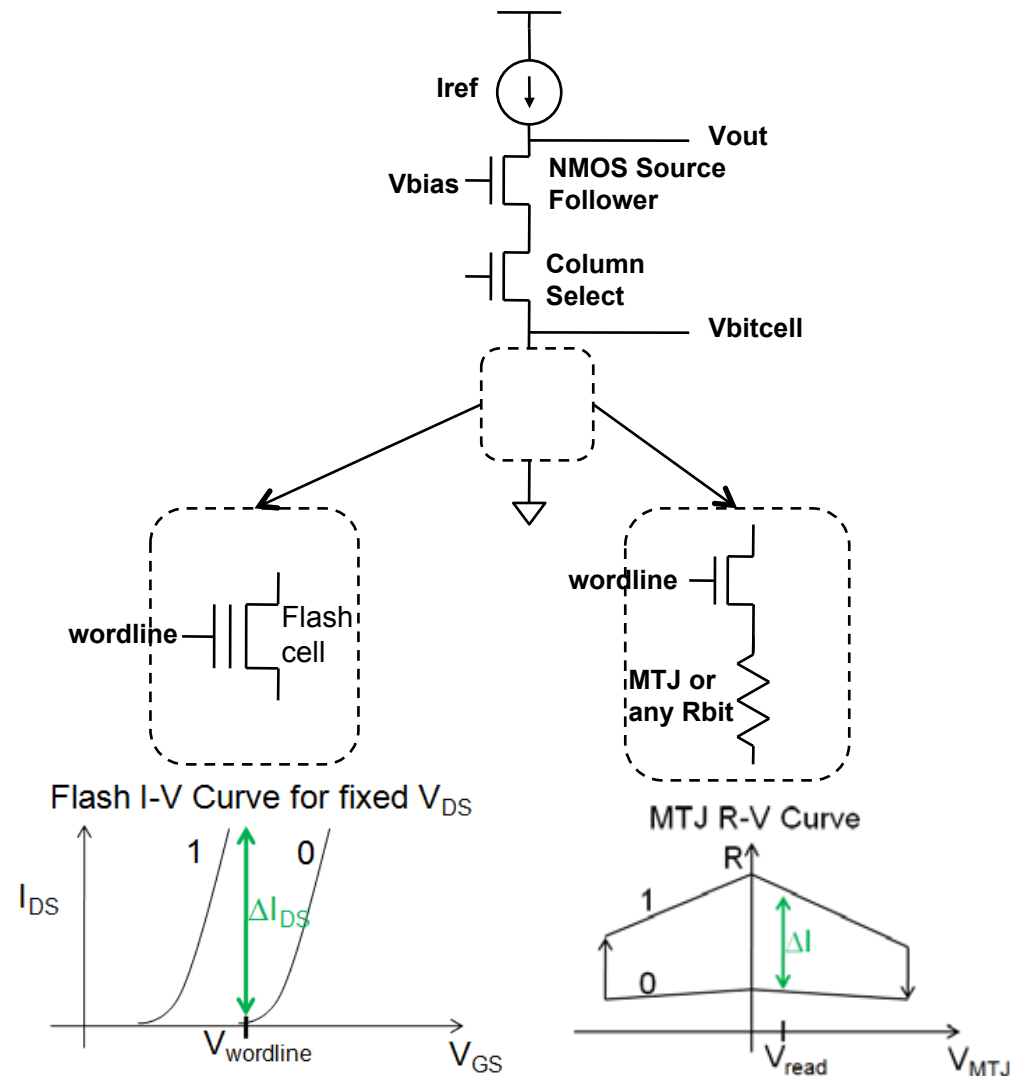

# Current Sensing Amplifier Circuit Approach

Current Sensing Amplifier Circuit

 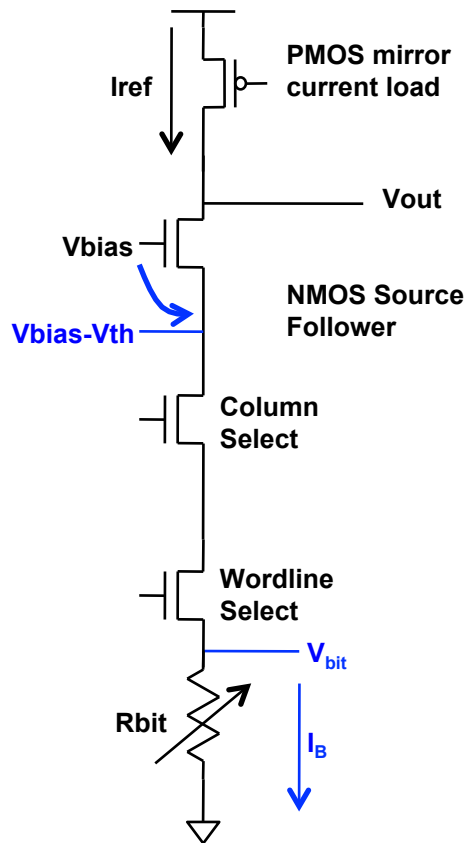

With very long sensing time,  $I_{ref}$  and  $I_B$  equalizes due to  $V_{out}$  stabling to final value.

Design requirements for best sensing margin:


- $V_{pre}$  is the DC voltage for  $I_{ref}$ .
- $I_{ref}$  is the mid-point of  $I_{high}$  and  $I_{low}$ .

Ref. 1
 
# Generating Reference for Sensing


- **Referenced Read Scheme**

- Generate a mid-point reference from high and low bits
- Need separation between high and low states
  - High and low states have distributions due to shape and thickness variation. Increases with smaller geometry.
- Used in MRAM, PCM, and Flash memories



- **Self-referenced Read Scheme** due to overlapping distribution of high and low states


- Destructive read:
  - a) Sample and store the bit state variable as voltage on cap
  - b) Switch the bit to opposite or a known state
  - c) Resample the bit state variable and compare with a)
- Destructive read used in FeRAM and DRAM
- Non-destructive read scheme: Sample at two different bias voltages and compare the resulting bit state variable (e.g. voltage stored on a capacitor). Ref. 10.
- Non-destructive read can be used in STT-MRAM due to R-I slope differences in high and low bit states.

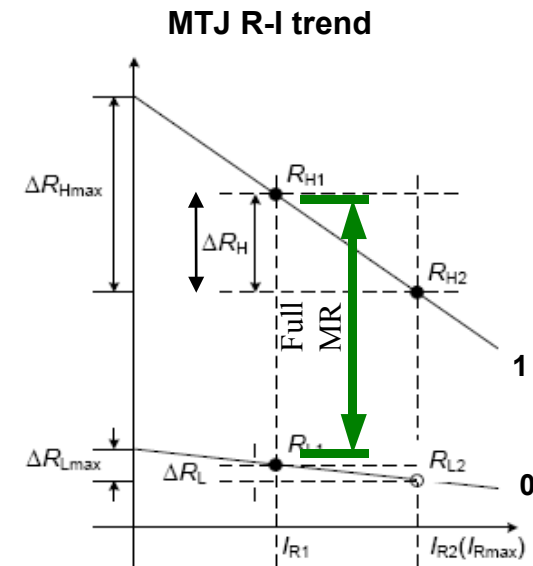



# Latch Type Sense Amplifier for Final Stage

Simplified LTSA Circuit

 

Positive feedback system with high gain.

Circuit operation

- Phase 1: CLK low  
OUT+ = OUT, OUT- = OUT\_B
- Phase 2: CLK high. Cross-coupled inverter pairs latch output.

LTSA used in SRAM and DRAM sensing.

NEED  $V(\text{OUT}) - V(\text{OUT}_B) > \text{LTSA offset}$

Statistical design for yield and speed:

Considering NMOS pair (N1, N2)  $V_{th}$  variation

$$\Delta V_{thN} = V_{th\_N1} - V_{th\_N2}$$

$$\sigma^2_{\Delta V_{thN}} = \sigma^2_{V_{th\_N1}} + \sigma^2_{V_{th\_N2}}$$

$$\sigma_{\Delta V_{thN}} = \sqrt{2} \cdot \sigma_{V_{thn}}$$

Similarly, for PMOS pair (P1, P2)

$$\sigma_{\Delta V_{thP}} = \sqrt{2} \cdot \sigma_{V_{thp}}$$

Further study: Ref. 11



# NVM Chip Interface and Applications

NVM Chip Interface facilitates interaction between application and NVM technology !!

You can exploit technology strength and hide technology weakness by choosing the right memory interface and application.

Asynchronous Interface Pins:


WE/	Write Enable
CE/	Chip Enable
OE/	Output Enable
DQ	Data Input/Output
A	Address

Additional Synchronous Interface Pins:

RAS/	Row Access Strobe
CAS/	Column Access Strobe
CLK	Clock

Differential Signals for high speed operation:

CLK, CLK/
DQS, DQS/

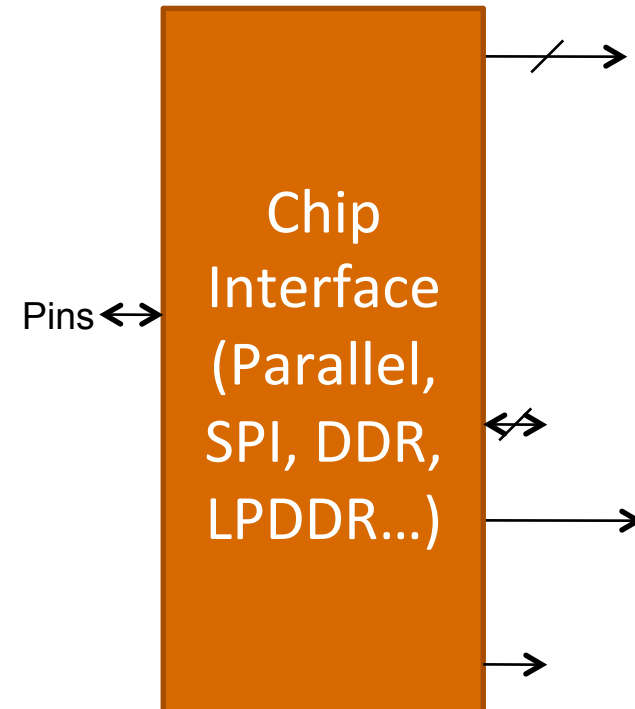


Common NVM Interfaces:

- Asynchronous Parallel interface, Ref. 13
- SPI (Serial Peripheral Interface) synchronous interface, Ref. 13
- DDR (Double data rate) synchronous interface, Ref. 12

# Asynchronous Parallel Read Access


Address-driven Read Cycle when Chip Enabled

 

Read 8-bit or 16-bit data (width of DQ bus) in response to address or chip enable.

Data access time would directly translate to memory read time (sensing time)

Chip Enable Driven Read Cycle

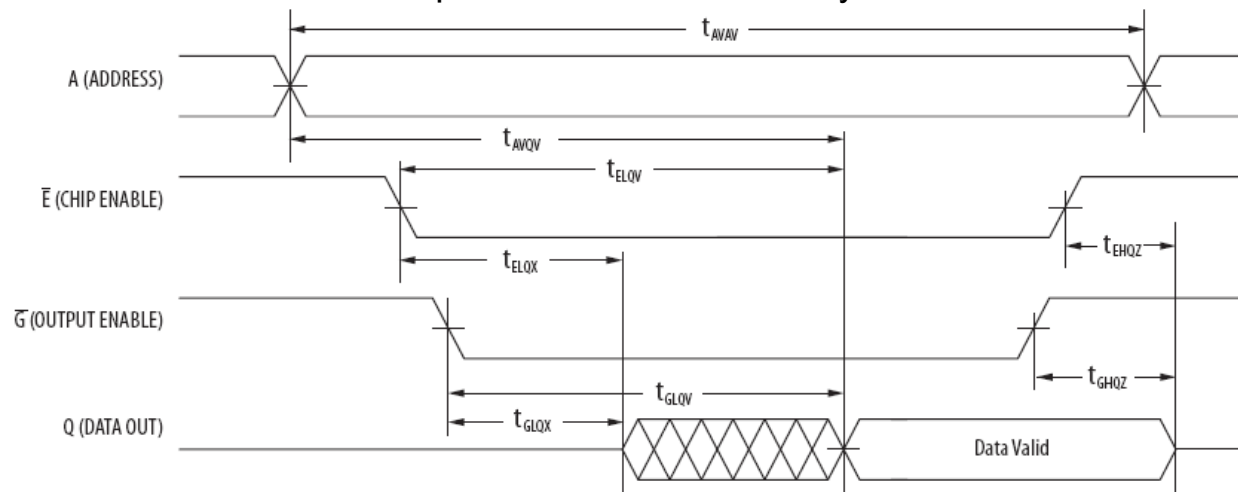


- Random data access
- Fast access time (for e.g. 10 – 40 ns)

Application: Ideal for code and non-stream data in industry automation, automotive, computing, networking
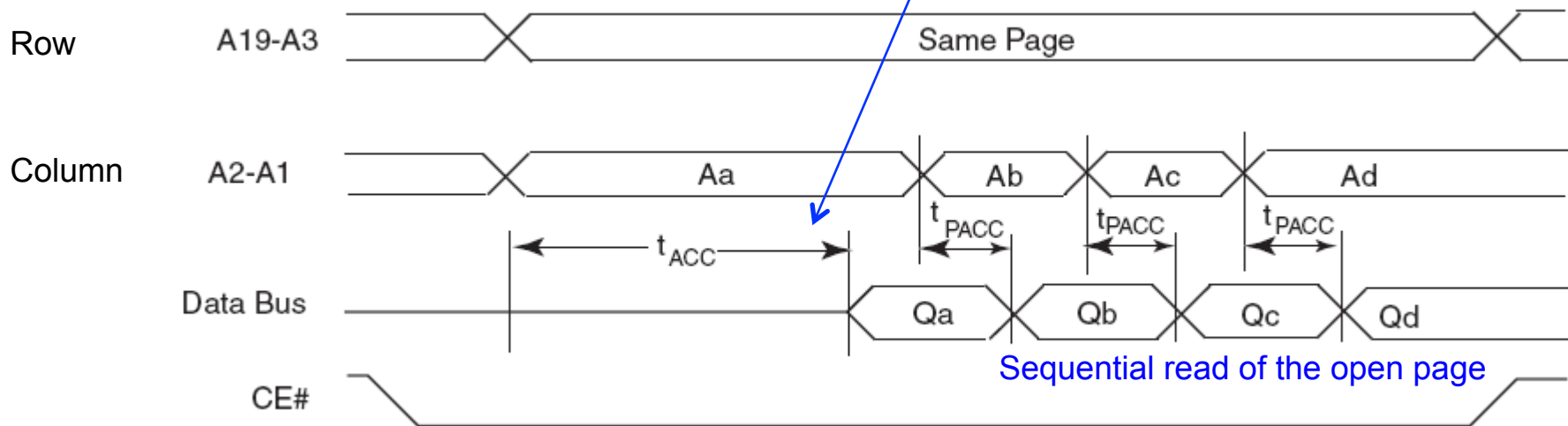
# Asynchronous Page Read Access

Address space divided into pages.  
Each page has a row and column address portion

Sensing operation of the whole page is complete



## Key Advantages:

- Timing cost of long sensing is amortized with sequential fast accesses. Suitable for memory with long sensing time e.g. NAND Flash.
- Page or block data access w/ narrow data bus: Ideal for code and stream data
- Increased bandwidth. Example bandwidth calculation with  $t_{ACC}=30\text{ns}$ ,  $t_{PACC}=5\text{ns}$  and 8-bit wide data bus:

### Random Access

$$4 \times 8 \text{ bits} = 4 \times t_{ACC} = 120\text{ns}$$

$$\text{Bandwidth} = 32 \text{ bit} / 120\text{ns}$$

$$= 266 \text{ Mbit/s}$$

### Page Access


$$4 \times 8 \text{ bits} = 1 \times t_{ACC} + 3 \times t_{PACC} = 45\text{ns}$$

$$\text{Bandwidth} = 32 \text{ bit} / 45\text{ns}$$

$$= 711 \text{ Mbit/s}$$

(almost 3x increase in bandwidth!)

# Asynchronous Write Access

 


Write 8-bit or 16-bit data (width of DQ bus) in response to write or chip enable.

Data write access time would directly translate to memory write time

- Random data write and fast write time (for e.g. 10 – 40 ns) in MRAM
- Write delay needed for Flash and PCM

Application: Ideal for code updates (cognitive computing, security) and non-stream data
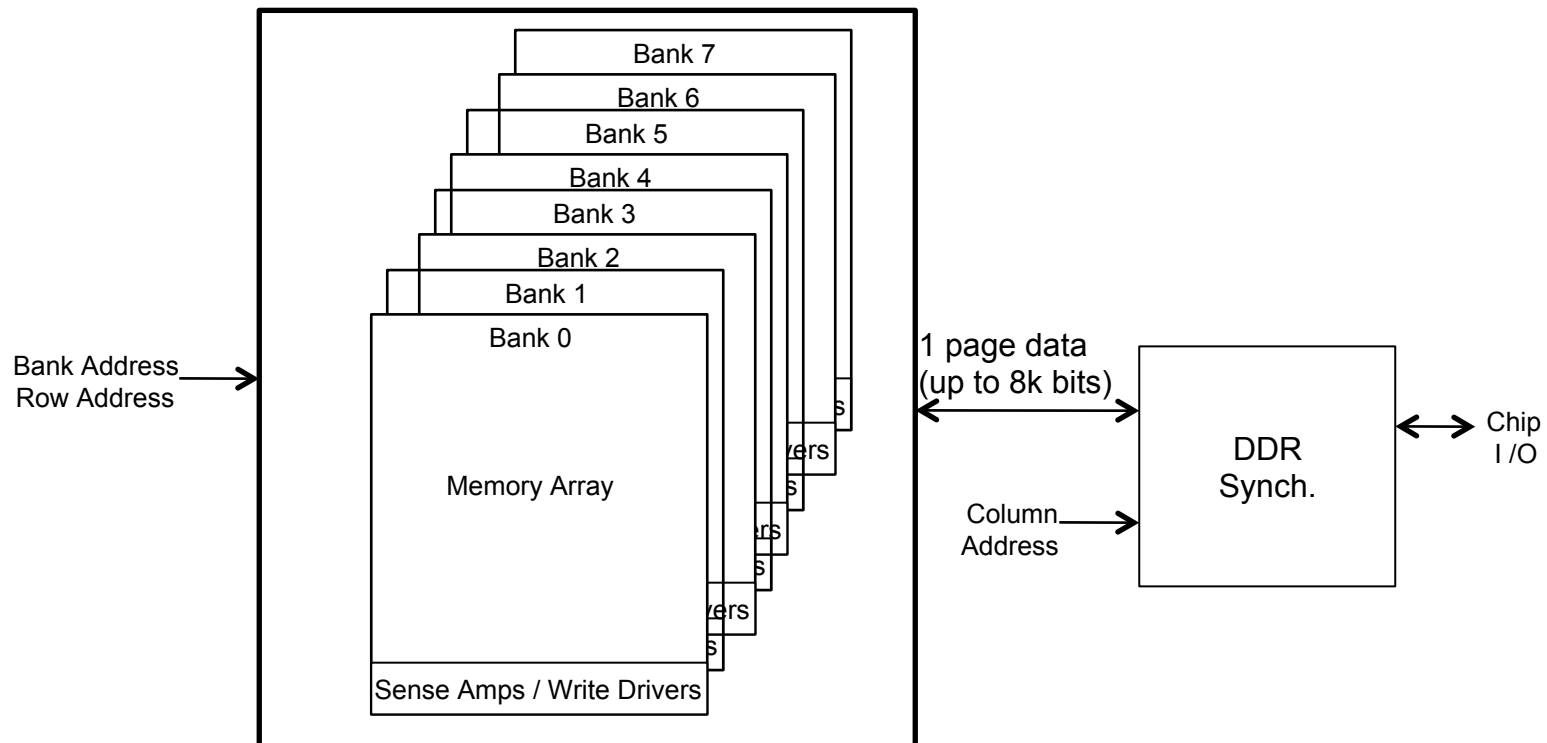
# Prefetch Architecture for DDR Interface



- Prefetch a page (up to 8k) of data from a Bank (8 banks) and store in local cache for fast read and write of cache.
- Parallel bank accesses for high data bandwidth.
- Differential clock (up to 800MHz) and data strobe.
- Data at both rising and falling edges of the clock.


Further study:  
Ref. 12

## Applications:


- Main memory (DRAM) in computing systems
- High speed buffer (non-volatility application) in storage systems
 
# High Speed DDR Interface Operations

Activate: Open a bank for read or write (row access)




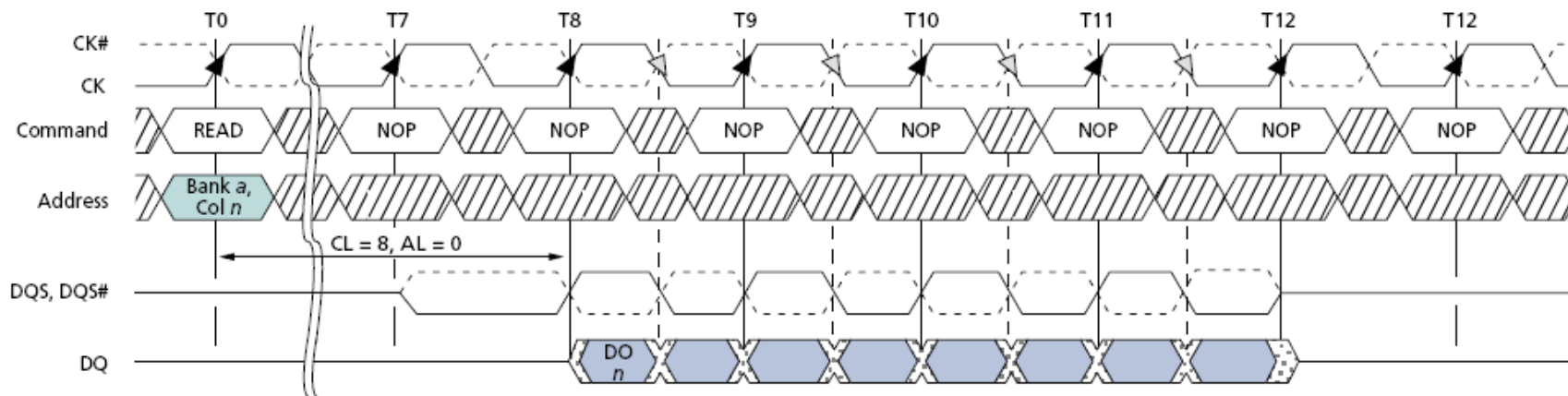Read: Read local cache bits using column address (column access)



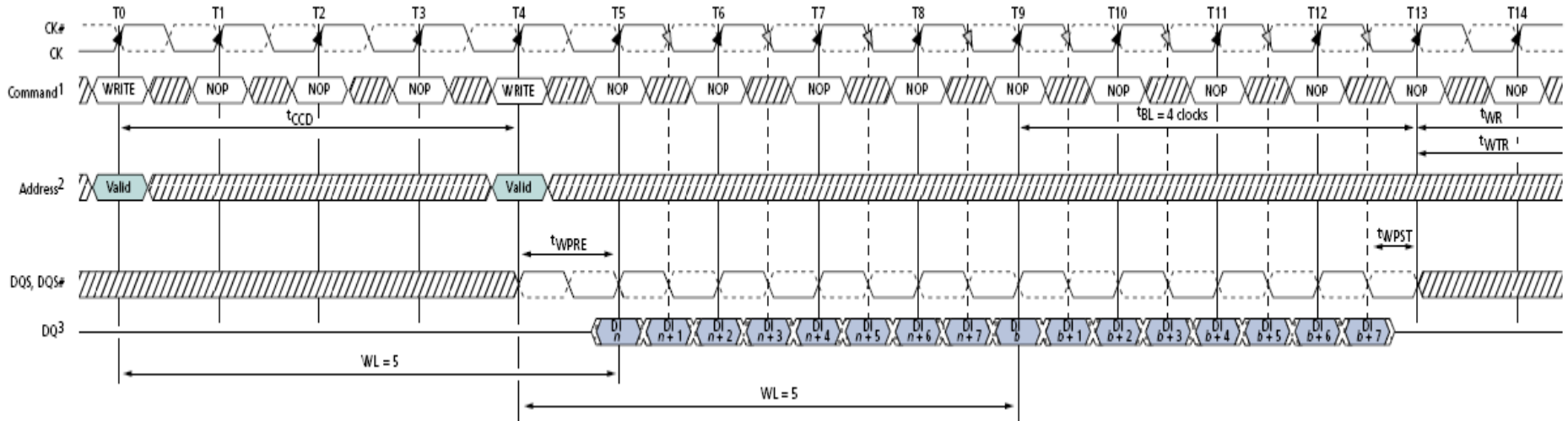
# High Speed DDR Interface Operations

Write: Write to local cache bits using column address (column access)



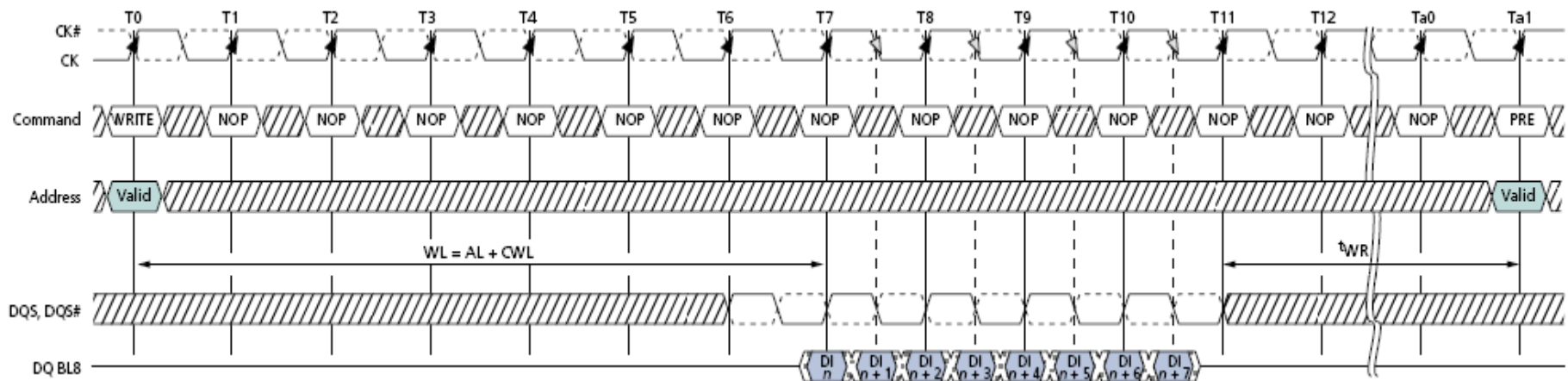Precharge: Close a bank using row address (row access)



- **Non-volatile memory designers need extensive interaction and co-design of technology, circuits, and application / market particularly for introducing emerging technologies.**
- **NVM chip design is similar to SoC design requiring analog, mixed-signal, and digital design skills.**
- **No one NVM technology (Flash, MRAM, FeRAM, ReRAM, PCM) has the best of all attributes (area, endurance, retention, cost ....) yet.**
- **Key circuit concepts differentiating from SRAM covered in the lecture are**
  - **Array Architecture**
  - **Voltage Boosting and Charge Pump Techniques**
  - **Write Driver Design**
  - **Sensing Schemes and Circuit**

# References

1. VLSI-Design of Non-Volatile Memories, G. Campardo et. al. Springer; 2005 edition (March 17, 2005)
2. International technology roadmap of semiconductors, ITRS, emerging device technologies, 2011 edition, public.itrs.net.
3. TN-29-19: NAND Flash 101 Introduction, Micron Technical Note. [download.micron.com/pdf/technotes/nand/tn2919.pdf](http://download.micron.com/pdf/technotes/nand/tn2919.pdf)
4. A. L. Lacaita, "Phase change memories: State-of-the-art, challenges and perspectives," Solid-State Electronics, vol. 50, pp. 24-31, 2006.
5. Wong et. al. "Phase Change Memories," Proceedings of the IEEE, vol. 98, no. 11, pp. 2201-2227, Dec. 2010.
6. R. Ranjan et. al., "Progress and Outlook for STT-MRAM," ICCAD Tutorial, 2011.
7. J.M. Slaughter et al, "High Density ST-MRAM Technology (Invited)," in *Proceedings of International Electronic Devices Meeting (IEDM)*, paper 29.3; San Francisco, CA (2012).
8. C. Hu, Chapter 6: MOS Transistors, [www.eecs.berkeley.edu/~hu/Chenming-Hu\\_ch6.pdf](http://www.eecs.berkeley.edu/~hu/Chenming-Hu_ch6.pdf)
9. T. Andre et. al., "A 4-Mb 0.18um 1T1MTJ Toggle MRAM With Balanced Three Input Sensing Scheme and Locally Mirrored Unidirectional Write Drivers," IEEE Journal of solid-state circuits, pp. 301-309, vol. 40, no. 1, 2005.
10. Y. Chen et. al, "A Nondestructive Self-Reference Scheme for Spin-Transfer Torque Random Access Memory (STT-RAM)," proceedings of IEEE Design and Test in Europe, 2010.
11. L. Pillegly et. al., "Mismatch Analysis and Statistical Design at 65 nm and Below," proceedings of IEEE Custom Integrated Circuit Design, 2008.
12. DDR3 SDRAM, Micron Technologies, <http://www.micron.com/products/dram/ddr3-sdram>
13. Everspin Technologies, product family, <http://www.everspin.com/products.php>
14. D. Sekar, Resistive RAM: Technology Status and Future Opportunities, 2014 IEEE Memory Symposium.