 


Problem 1 (20 Points)

Determine the capacitances for the following structures:


a) Diffusion capacitance



Where: $C_{\text{bottom}} = 23 \text{ ff}/\mu^2$ and $C_{\text{sidewall}} = 10 \text{ ff}/\mu$

Total DIFFUSION Capacitance = **10.86ff + 34.00ff = 44.86ff**

b) Gate and Diffusion Capacitances

 


Where: $C_{\text{bottom}} = 29 \text{ ff}/\mu^2$ $C_{\text{sidewall}} = 15.5 \text{ ff}/\mu$ $C_{\text{gate}} = 11.6 \text{ ff}/\mu^2$

Total DIFFUSION Cap = **128.34ff (sidewall) + 30.14ff (bottom) = 158.49ff**

Total GATE Cap = **2.1924ff + 2.1924ff = 4.3848ff**

Problem 2. Transistor Mapping & Sizing (20 Points)

 
a) What is the truth table for the following circuit?




A	B	C	OUT
0	0	0	1
0	1	0	1
1	0	0	1
1	1	0	0
0	0	1	1
0	1	1	0
1	0	1	0
1	1	1	0

b) Size the transistors so that they can drive a load which is 3X minimum size inverter. **PMOS = 6** **NMOS = 3** assuming a fanout of 3.

c) Draw the logic gate equivalent of this circuit

 

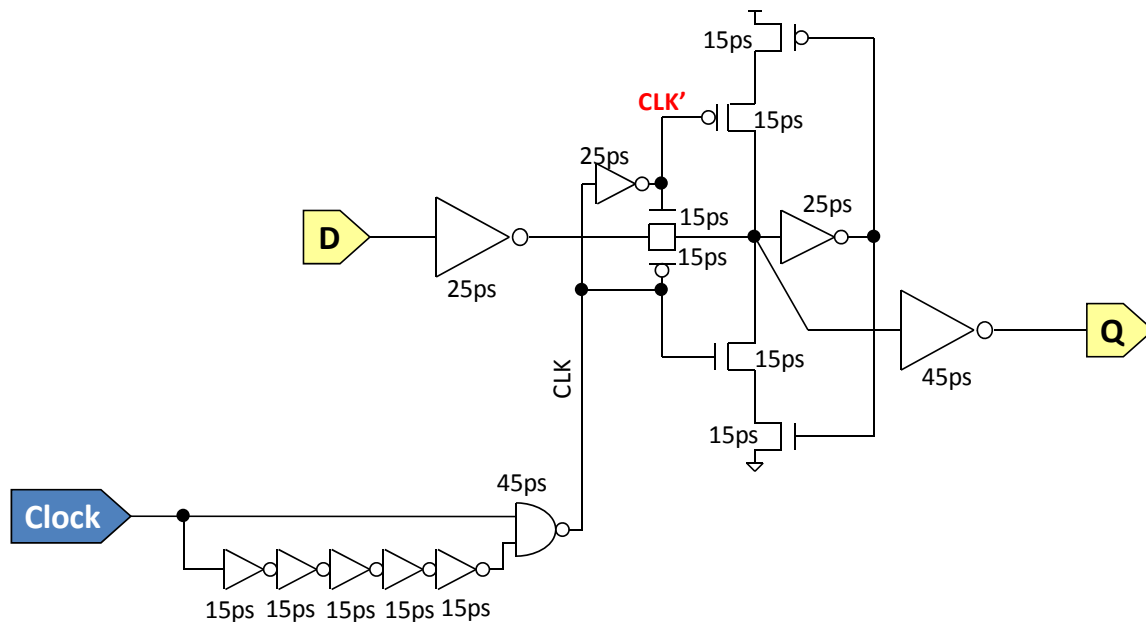Problem 3: Sequential Elements (20 Points)



NOTE: Critical timing is from Clock to CLK' Time from Clock to CLK' is **145ps** for CLK' going low and **70ps** for CLK' going high.

a) What is the T_{setup} time

$$25\text{ps} + 15\text{ps} + 25\text{ps} + 15\text{ps} - 145\text{ps} = -65\text{ps}$$

NOTE: negative setup time is typical of a pulse latch

b) What is the T_{hold} time?

$$145\text{ps} - 25\text{ps} = 120\text{ps}$$


NOTE: Excessive hold times are typical of a pulse latch

c) What is the $T_{\text{clock-q}}$ time?

$$70\text{ps} + 15\text{ps} + 45\text{ps} = 130\text{ps}$$

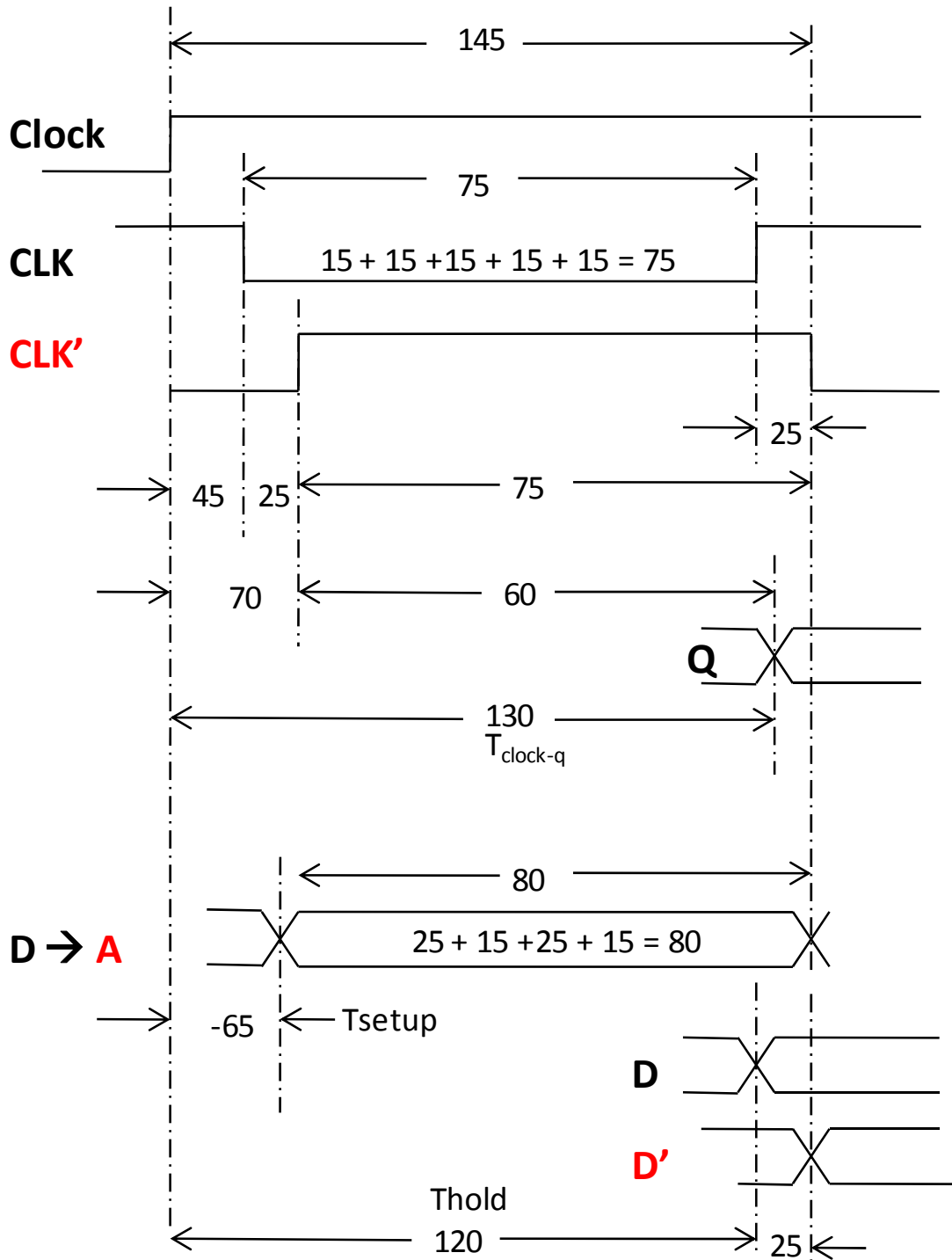d) What is the pulse width of the CLK signal?

$$15\text{ps} + 15\text{ps} + 15\text{ps} + 15\text{ps} + 15\text{ps} = 75\text{ps}$$



NOT TO SCALE (obviously 😊)

Problem 5. Logical Effort (20 Points)

Design a 10-input AND gate network for minimum delay using nothing more than the following standard cell gates:

Gate type	1x	2x	3x
INV	✓	✓	✓
2-NAND	✓	✓	✓
3-NAND	✓	✓	n/a
2-NOR	✓	✓	n/a
3-NOR	✓	✓	n/a

NOTE: n/a indicates not available

The network is driven by unit size inverters and the output is driving a load of 23 unit size inverters. Compute the delay using logical effort technique.

$H = 23$

$B = 1$ (No Branching)

Assume 5 stages (including unit size inverter)

INV -> NAND-3 -> NOR2 -> NAND2 -> INV

$G = 1 * 5/3 * 5/3 * 4/3 * 1 = 100/27$

$F = GBH = 23 * 1 * 100/27 = 106.48$

$f = F^{1/5} = 2.43$

$D = (5 * 2.54) + 1 + 3 + 2 + 2 + 1 = 21.71$ (if we use a fanout of 2.54)


Lets use 3.00 to size gates:

INV = $69/3 \approx 24 \rightarrow 16/8$ which is 8X device

NAND2 = $24/3 * 4/3 \approx 12$ which is a 3X device

NOR2 = $12/3 * 5/3 \approx 8$ which is a 2X device



NAND3 = $8/3 * 5/3 \approx 4$ which is a 1X device

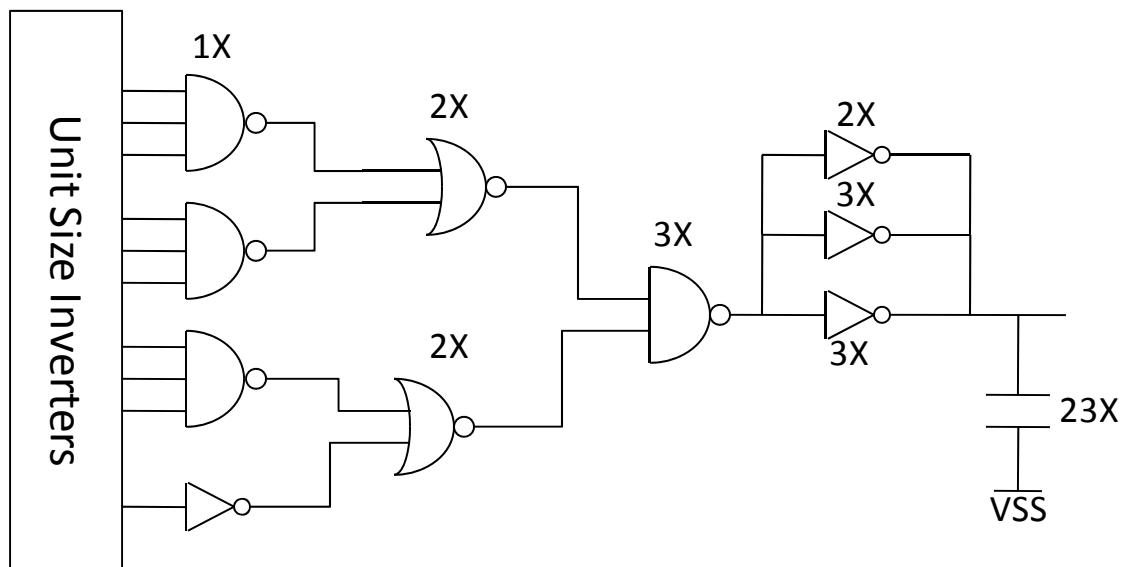

Problem 5. Device Operation (20 Points)

Derive the analytic expression for V_{sw} where $V_{out}=V_{in}=V_{sw}$ (switch point) for region C for the inverter transfer function shown to the right.

Assume that $|V_{tp}| = V_{tn}$ and $\beta_n = \beta_p$

  

Recall that the currents through each transistor are equal in the switch point region: $I_{dsn} = -I_{dsp}$

The current through the NMOS device in saturation is: $\frac{\beta_n}{2}(V_{in} - V_{tn})^2$

The current through the PMOS device in saturation is: $\frac{\beta_p}{2}(V_{in} - V_{DD} - V_{tp})^2$

The switching point where both transistors are saturated (region C) is found by solving for equal currents. Therefore

$$\frac{\beta_n}{2}(V_{in} - V_{tn})^2 = -\frac{\beta_p}{2}(V_{in} - V_{DD} - V_{tp})^2$$

Since $\beta_p = \beta_n$ and $|-V_{tp}| = V_{tn}$ we get:

$$V_{in} = \frac{V_{DD}}{2} \text{ which is what we expected}$$

The real gnarly solution when $\beta_p \neq \beta_n$ and $V_{tp} \neq V_{tn}$ is shown below

$$\begin{aligned} \frac{\beta_n}{2}(V_{in} - V_m)^2 &= \frac{\beta_p}{2}(V_{in} - V_{DD} - V_{tp})^2 \\ V_{in}^2(\beta_n - \beta_p) + V_{in}(-2\beta_n V_m + 2\beta_p(V_{DD} + V_{tp})) + (\beta_n V_m^2 - \beta_p(V_{DD} + V_{tp})^2) &= 0 \\ V_{in} &= \frac{\beta_n V_m - \beta_p(V_{DD} + V_{tp}) + (V_{DD} + V_{tp} - V_m)\sqrt{\beta_n \beta_p}}{\beta_n - \beta_p} \\ &= \frac{V_{DD} + V_{tp} + \sqrt{\frac{\beta_n}{\beta_p}} V_m}{1 + \sqrt{\frac{\beta_n}{\beta_p}}} \end{aligned}$$