
Lecture 5: CMOS Transistor Theory

Mark McDermott





**Electrical and Computer Engineering
The University of Texas at Austin**

Outline

- **Introduction**
- **MOS Capacitor**
- **nMOS I-V Characteristics**
- **pMOS I-V Characteristics**
- **Gate and Diffusion Capacitance**
- **MOS Channel resistance**
- **Resistors & RC approximation**

Introduction

    - So far, we have treated transistors as ideal switches
- An ON transistor passes a finite amount of current
 - Depends on terminal voltages
 - Derive current-voltage (I-V) relationships
- Transistor gate, source, drain all have capacitance
 - $I = C (\Delta V / \Delta t) \rightarrow \Delta t = (C / I) \Delta V$
 - Capacitance and current determine speed




Electrical Properties of MOS Devices


- **Necessary to understand the basic electrical properties of the MOS transistor (geometry => electrical), e.g., delay/power**
 - Ensure that the circuits are robust
 - Create working layouts
 - Predict delays and power consumption
- **As technology advances and circuit dimensions scale down, electrical effects become more important**
 - Secondary/non-ideal effects (next lecture)

MOS Capacitor

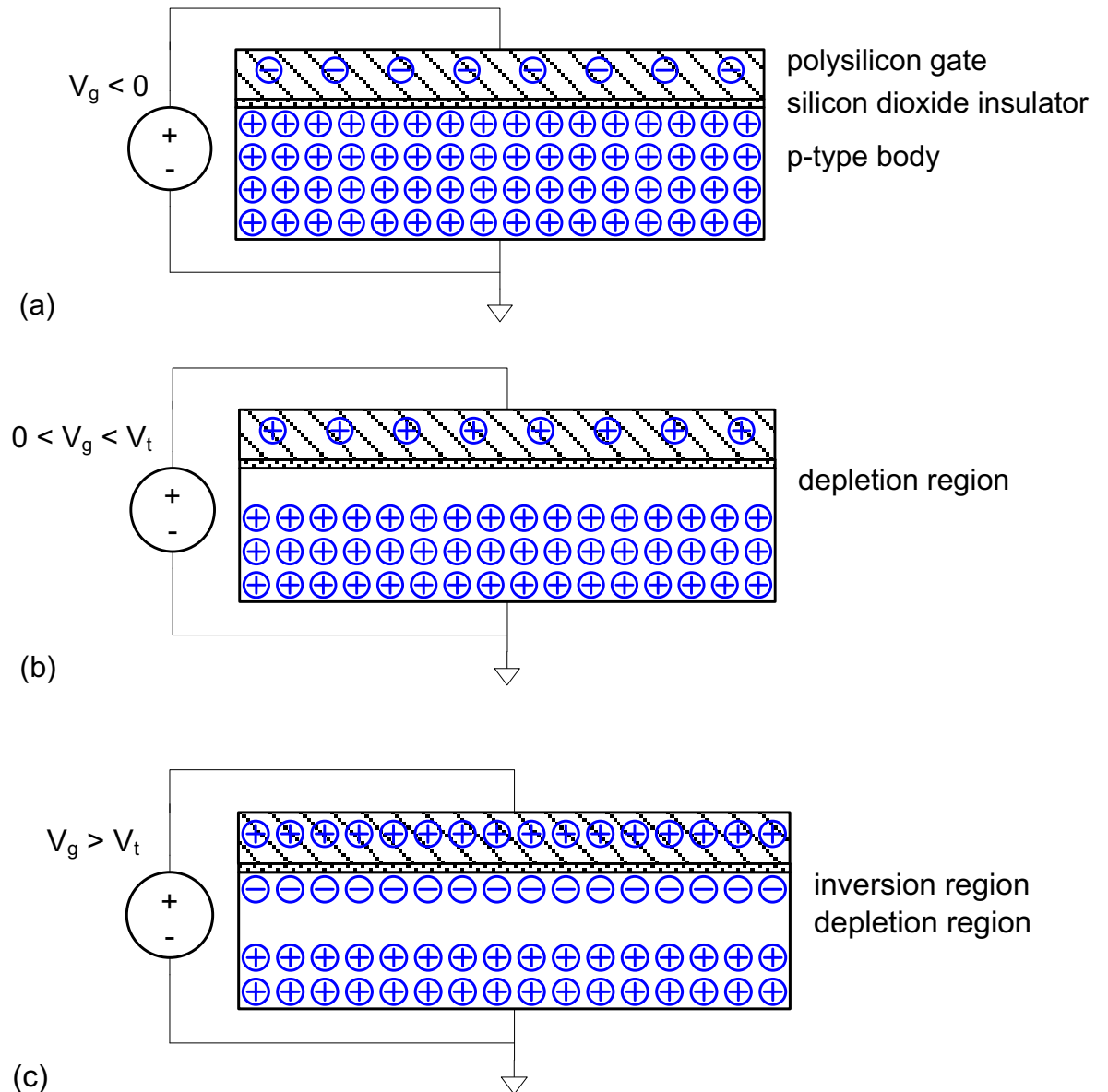- Gate and body form MOS capacitor
- Operating modes
 - Accumulation
 - Depletion
 - Inversion



The nMOS Transistor

 

Moderately doped p- type substrate (or well) in which two heavily doped n+ regions, the **Source** and **Drain** are diffused

- **Gate is insulated from substrate by thin oxide**
 - Resistance of oxide is $> 10^{12} \Omega$, so current ~ 0
- **Two types of nMOS transistor**
 - Enhancement mode: non conducting when gate voltage $V_{gs} = V_{sb}$ (source voltage) (**normally used**)
 - Depletion mode: conducting when $V_{gs} = V_{sb}$


Terminal Voltages

- Mode of operation depends on V_g , V_d , V_s

$$V_{gs} = V_g - V_s$$

$$V_{gd} = V_g - V_d$$

$$V_{ds} = V_d - V_s = V_{gs} - V_{gd}$$

 


- Source and drain are symmetric diffusion terminals
 - By convention, **source is terminal at lower voltage**
 - Hence $V_{ds} \geq 0$
- nMOS body is grounded; for simple designs, assume source is grounded too
- Three regions of operation
 - *Cutoff*
 - *Linear*
 - *Saturation*

nMOS Cutoff

- No channel


$$I_{ds} \approx 0$$

 

nMOS Linear


- Channel forms
- Current flows from **d** to **s**
 - e^- from **s** to **d**
- I_{ds} increases with V_{ds}
 - Similar to linear resistor
- Since there is a threshold voltage (V_t) required to invert the charge under the gate, this means that the effective gate voltage is:

$$V_g = V_{gs} - V_t$$

 


nMOS Saturation

 - Channel pinches off
- I_{ds} independent of V_{ds}
- Current saturates
- Similar to current source



The pMOS Transistor

 


Moderately doped n- type substrate (or well) in which two heavily doped p+ regions, the **Source** and **Drain** are diffused

- Application of a negative gate voltage (w.r.t. source) draws holes into the region below the gate; channel changes from n to p-type (source-drain conduction path)
- Conduction due to holes; negative V_d sweeps holes from source (through channel) to drain

I-V Characteristics

 - In Linear region, I_{ds} depends on
 - How much charge is in the channel?
 - How fast is the charge moving?



Channel Charge

- MOS structure looks like parallel plate capacitor while operating in inversion



Gate – oxide – channel

$$Q_{\text{channel}} = CV$$

$$C = C_g = \epsilon_{\text{ox}} WL / t_{\text{ox}} = C_{\text{ox}} WL$$

$$V = V_{\text{gc}} - V_t = (V_{\text{gs}} - V_{\text{ds}}/2) - V_t$$

  where $C_{\text{ox}} = \epsilon_{\text{ox}} / t_{\text{ox}}$



Carrier Velocity

- Charge is carried by e-
- Carrier velocity v proportional to lateral E-field between source and drain:


$$v = \mu E_{ds} \quad \text{where } \mu \text{ is the electron/hole mobility}$$

where $E_{ds} = \frac{V_{ds}}{L}$

- Time for carrier to cross channel:

$$\tau_{sd} = \frac{\text{Length of the channel } (L)}{\text{Velocity } (v)}$$

 or
$$\tau_{sd} = \frac{L^2}{\mu V_{ds}}$$



nMOS Linear I-V


■ Now we know

- How much charge Q_{channel} is in the channel
- How much time “ τ ” each carrier takes to cross

$$I_{ds} = \frac{Q_{\text{channel}}}{t}$$

$$= \mu C_{\text{ox}} \frac{W}{L} \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$
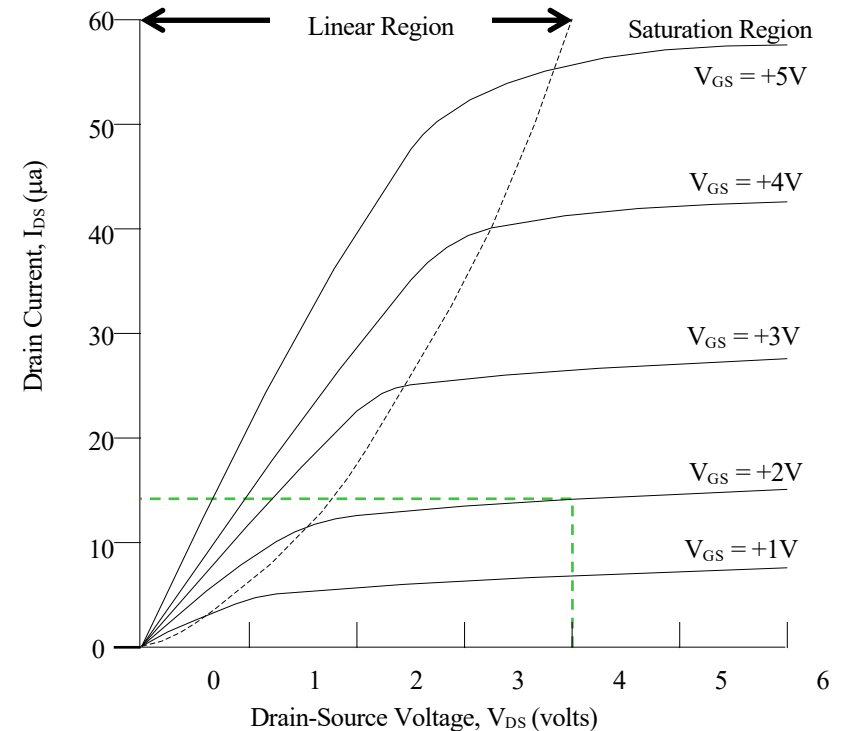
$$= \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} \quad \text{where} \quad \beta = \mu C_{\text{ox}} \frac{W}{L}$$




nMOS Saturation I-V

- If $V_{gd} < V_t$, channel pinches off near drain

— When $V_{ds} > V_{dsat} = V_{gs} - V_t$

- Now drain voltage no longer increases current

$$I_{ds} = \beta \left(V_{gs} - V_t - \frac{V_{dsat}}{2} \right) V_{dsat}$$
$$= \frac{\beta}{2} (V_{gs} - V_t)^2$$

 

nMOS I-V Summary

■ Shockley 1st order transistor models

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{ds} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_t)^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$


Example

■ Example: a 0.6 μm process from AMI semiconductor

- $t_{\text{ox}} = 100 \text{ \AA}$
- $\mu = 350 \text{ cm}^2/\text{V}\cdot\text{s}$
- $V_t = 0.7 \text{ V}$

■ Plot I_{ds} vs. V_{ds}

 - $V_{\text{gs}} = 0, 1, 2, 3, 4, 5$
- Use $W/L = 4/2 \lambda$



$$\beta = \mu C_{\text{ox}} \frac{W}{L} = (350) \left(\frac{3.9 \cdot 8.85 \cdot 10^{-14}}{100 \cdot 10^{-8}} \right) \left(\frac{W}{L} \right) = 120 \frac{W}{L} \mu\text{A}/\text{V}^2$$

pMOS I-V


- All dopings and voltages are inverted for pMOS
- Mobility μ_p is determined by holes
 - Typically 2-3x lower than that of electrons μ_n for older technologies.
 - Approaching 1 for gate lengths $< 20\text{nm}$.
- Thus pMOS must be wider to provide the same current
 - Simple assumption, $\mu_n / \mu_p = 2$ for technologies $> 20\text{nm}$

Capacitance

- **Any two conductors separated by an insulator have capacitance**
- **Gate to channel capacitor is very important**
 - Creates channel charge necessary for operation
- **Source and drain have capacitance to body**
 - Across reverse-biased diodes
 - Called diffusion capacitance because it is associated with source/drain diffusion


Gate Capacitance

 - Approximate channel as connected to source
- $C_{gs} = \epsilon_{ox} WL / t_{ox} = C_{ox} WL = C_{per/micron} W$
- $C_{permicron}$ is typically about 2 fF/ μm for minimum channel length device



Capacitance Estimation

 - The **dynamic response** (switching speed) of a CMOS circuit is very dependent on **parasitic capacitances** associated with the circuit




Parasitic Capacitances:

C_{gs} , C_{gd} = gate-to-channel capacitances lumped at source and drain regions

C_{sb} , C_{db} = source and drain diffusion capacitances to bulk (substrate)


Add **routing capacitances** to get total capacitance.

Gate Capacitance of MOS Transistor

 


$W = 49.2 \mu$,
 $L = 0.75 \mu$

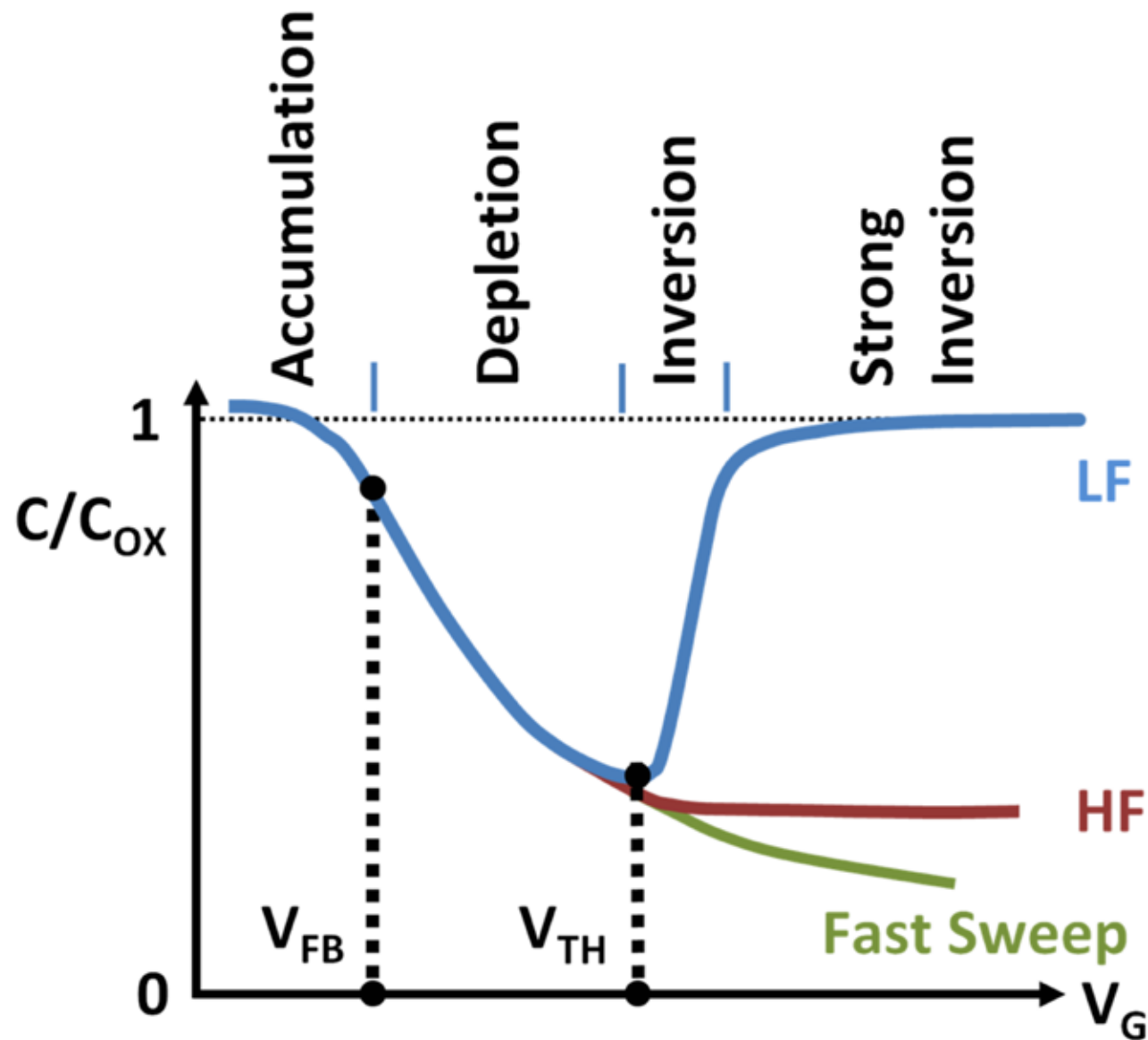
Gate Capacitance of MOS Transistor (cont.)



 
Gate Capacitance: Operation Region Dependence



Cut-off

 

Linear (Triode)

 


Saturation

Operation Region	C_{gb}	C_{gs}	C_{gd}
Cutoff	$C_{ox}WL_{eff}$	0	0
Triode	0	$C_{ox}WL_{eff}/2$	$C_{ox}WL_{eff}/2$
Saturation	0	$(2/3)C_{ox}WL_{eff}$	0


Diffusion Capacitance

 - C_{sb} , C_{db} from Source/Drain
- Undesirable, called *parasitic* capacitance
- Capacitance depends on area and perimeter
 - Use small diffusion nodes
 - Comparable to C_g for contacted diff
 - $\frac{1}{2} C_g$ for uncontacted
 - Varies with process



Area and Periphery Capacitance


C_{jp} = Periphery capacitance (pf/ μ)

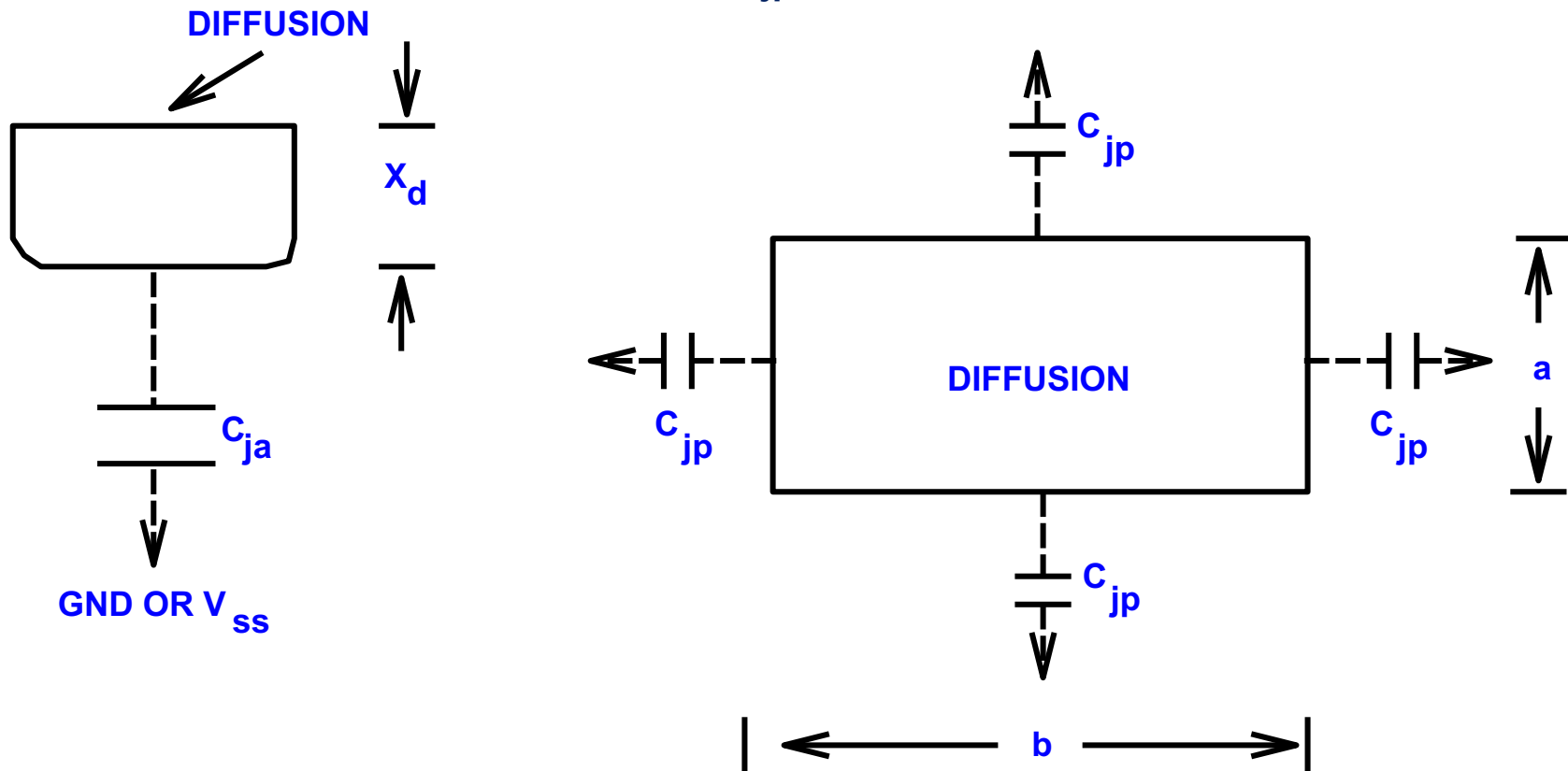

C_{ja} = Area capacitance (pf/ μ^2)


Pass Transistors

 - We have assumed source is grounded
- What if source > 0 ?
 - e.g. pass transistor passing V_{DD}







Pass Transistors

 - We have assumed source is grounded
- What if source > 0 ?
 - e.g. pass transistor passing V_{DD}
- $V_g = V_{DD}$
 - If $V_s > V_{DD} - V_t$, $V_{gs} < V_t$
 - Hence transistor would turn itself off
- nMOS pass transistors pull no higher than $V_{DD} - V_{tn}$
 - Called a degraded “1”
 - Approach degraded value slowly (low I_{ds})
- pMOS pass transistors pull no lower than V_{tp}




Pass Transistor Circuits

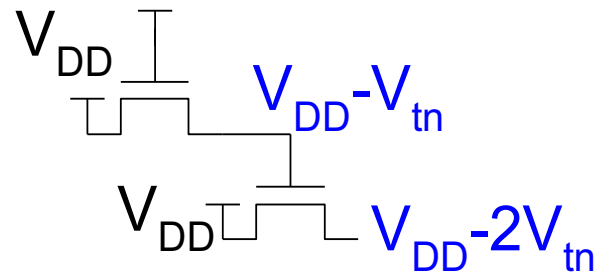 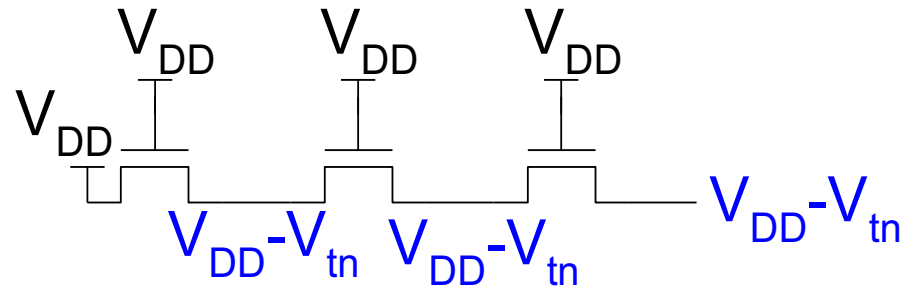 


NOTE: These values are for steady state conditions only.

Effective Resistance

- **Shockley models have limited value**
 - Not accurate enough for modern transistors
 - Too complicated for hand analysis
- **Simplification: treat transistor as resistor**
 - Replace $I_{ds}(V_{ds}, V_{gs})$ with effective resistance R
 - $I_{ds} = V_{ds}/R$
 - R averaged across switching of digital gate
- **Too inaccurate to predict current at any given time**
 - But good enough to predict RC delay

 

The MOS Resistor

 

- **Resistance of a bar of uniform material**

$$R = \frac{\rho \times L}{A} = \left(\frac{\rho}{t}\right)\left(\frac{L}{W}\right)$$

where ρ = resistivity of the material,

A = cross-section of the resistor

t, W = thickness, width of the material

- **The channel resistance of a MOS transistor in the linear region**

$$R_c = k\left(\frac{L}{W}\right),$$

$$\text{where } k = \frac{1}{\mu C_{ox}(V_{gs} - V_t)}$$

Resistance of Turned-On Transistor


W/L ratio defines size of N and P channel transistors

Channel resistance of turned-on transistor is:

$$R_c = k\left(\frac{L}{W}\right), \text{ where } k = \frac{1}{\mu C_{ox}(V_{gs} - V_t)}$$


k is in the range of 1000 -- 30,000 Ω / \square

 Resistance increases by about 0.25%/°C above 25°C





$\downarrow \rightarrow R = 3 \square s$

$$R = L/W * \square$$

 


$\downarrow \rightarrow R = 1/3 \square s$

Resistors Connected in Series

  

$$R = R_1 + R_2 = 2\Box s$$

 
Sheet Resistance, R_s : Any material on the chip can be divided into squares W on a side with $(R_s \Omega/\Box)$ $R = R_s(L/W)\Omega$



Typical sheet resistances (Ω/\Box) for 0.25 μ TSMC process:
4.7 for N+, 3.5 for P+, 4.2 for Poly, 0.06 for Metal1,
0.08 for Metal2 - Metal4, 0.03 for Metal5, and 1190 for the N-well
Increase of about 0.3%/° C (metal, poly), 1%/° C (diffusion)

Resistors Connected in Parallel
 
$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$



For two squares in parallel, the equivalent resistance is $\frac{1}{2} \square$

Expressing sheet resistance in \square s simplifies the calculations

Contact resistance becomes more important as processes scale down

About 6 Ω for N+, P+, Poly, Metal 4

2 Ω for Metal2

4 Ω for Metal3



8 Ω for Metal5

in a 0.25 μ m TSMC process

Use multiple contacts/vias for low resistance connections


RC Delay Model

  - **Use equivalent circuits for MOS transistors**
 - Ideal switch + capacitance and ON resistance
 - Unit nMOS has resistance R , capacitance C
 - Unit pMOS has resistance $2R$, capacitance C
- **Capacitance proportional to width**
- **Resistance inversely proportional to width**



Inverter Delay Estimate

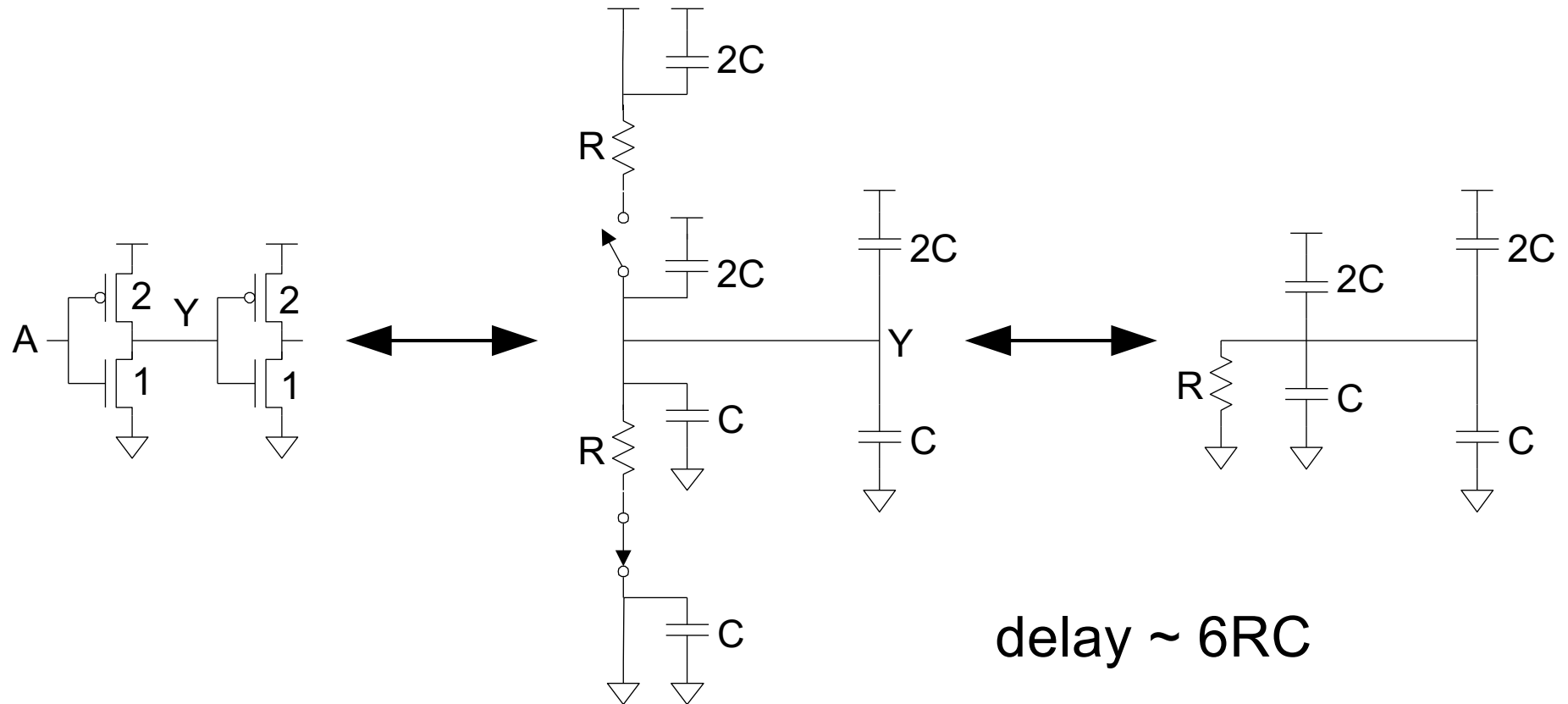- Estimate the delay of a fanout-of-1 inverter



Backup

Example of SPICE Deck

```
*file asic3.sp  test of 10 stage lumped mos model
* comments
.option scale=1e-6 post=2 nomod
vin in 0 pl 0v 0n 5v 100ps
.param rpoly=40 wt=100 lt=1.2
m1 single in 0 0 n w=wt l=lt
xm1 lumped in 0 0 lrgtp xw=wt xl=lt
vsingle single 0 5v
vlumped lumped 0 5v
.tran 25ps 4ns
.graph tran model=time1 single=par('-i(vsingle) ') lumped=par('-i(vlumped)')
.model time1 plot xmin=0ps xmax=800ps

* subckt and model on next page
*.subckt lrgtp drain gate source bulk
```

Example of SPICE Deck, Cont' d

```
.subckt lrgtp drain gate source bulk
m1 drain gate source bulk n w='xw/18' l=xl
m2 drain g1 source bulk n w='xw/9' l=xl
m3 drain g2 source bulk n w='xw/9' l=xl
m4 drain g3 source bulk n w='xw/9' l=xl
m5 drain g4 source bulk n w='xw/9' l=xl
m6 drain g5 source bulk n w='xw/9' l=xl
m7 drain g6 source bulk n w='xw/9' l=xl
m8 drain g7 source bulk n w='xw/9' l=xl
m9 drain g8 source bulk n w='xw/9' l=xl
m10 drain g9 source bulk n w='xw/18' l=xl
```


Example of SPICE Deck, Cont' d

r1 gate g1 'xw/xl*rpoly/9'

r2 g1 g2 'xw/xl*rpoly/9'

r3 g2 g3 'xw/xl*rpoly/9'

r4 g3 g4 'xw/xl*rpoly/9'

r5 g4 g5 'xw/xl*rpoly/9'

r6 g5 g6 'xw/xl*rpoly/9'

r7 g6 g7 'xw/xl*rpoly/9'

r8 g7 g8 'xw/xl*rpoly/9'

r9 g8 g9 'xw/xl*rpoly/9'

.ends lrgtp

** model section *

.model n nmos level=3 vto=0.7 uo=500 kappa=.25 kp=30u

eta=.03 theta=.04 +vmax=2e5 nsub=9e16 tox=250e-10


gamma=1.5 pb=0.6 js=.1m xj=0.5u ld=0.0

+nfs=1e11 nss=2e10 cgso=200p cgdo=200p cgbo=300p


.end

Spice Simulation: NAND Gate

 SPICE "deck" has "measure", print statements; parameters, netlist
Model: 0.18 micron



Modes in MOS Structures

 

Greek alphabet

GREEK ALPHABET

By Ben Crowder • bencrowder.net • Last modified 2 May 2012

Αα

ALPHA [a]
ἄλφα

Ββ

BETA [b]
βῆτα

Γγ

GAMMA [g]
γάμμα

Δδ

DELTA [d]
δέλτα

Εε

EPSILON [e]
ἒ ψιλόν

Ζζ

ZETA [dz]
ζῆτα

Ηη

ETA [e:]
ἦτα

Θθ

THETA [tʰ]
θῆτα

Ιι

IOTA [i]
ἰῶτα

Κκ

KAPPA [k]
κάππα

Λλ

LAMBDA [l]
λάμβδα

Μμ

MU [m]
μῦ

Νν

NU [n]
νῦ

Ξξ

XI [ks]
ξεῖ

Οο

OMICRON [o]
ὀ μικρόν

Ππ

PI [p]
πεῖ

Ρρ

RHO [r]
ῥῶ

Σσς

SIGMA [s]
σίγμα

Ττ

TAU [t]
ταῦ

Υυ

UPSILON [u]
ῥ ψιλόν

Φφ

PHI [pʰ]
φεῖ

Χχ

CHI [kʰ]
χεῖ

Ψψ

PSI [ps]
ψεῖ

Ωω

OMEGA [ɔ:]
ὦ μέγα