

---

# **Lecture 8:**

## **Combinational Circuit Design**

**Mark McDermott**

**Electrical and Computer Engineering  
The University of Texas at Austin**

# Verilog to Gates


---

```
module mux(input  s, d0, d1,  
           output y);
```

```
    assign y = s ? d1 : d0;
```

```
endmodule
```

 
**Sketch a design using AND, OR, and NOT gates.**



## Example

---

 
2) Sketch the design using NAND, NOR, and NOT gates. Assume  $\sim S$  is available.



## Example 3

---

 3) Sketch a design using one compound gate and one NOT gate.  
Assume  $\sim S$  is available.





# Sizing Compound Gates

## ■ Inverter equivalence



unit inverter

$$Y = \overline{A}$$

  



AOI21

$$Y = \overline{A \cdot B + C}$$

  



AOI22

$$Y = \overline{A \cdot B + C \cdot D}$$

  


Complex AOI
  
$$Y = \overline{A \cdot (B + C) + D \cdot E}$$



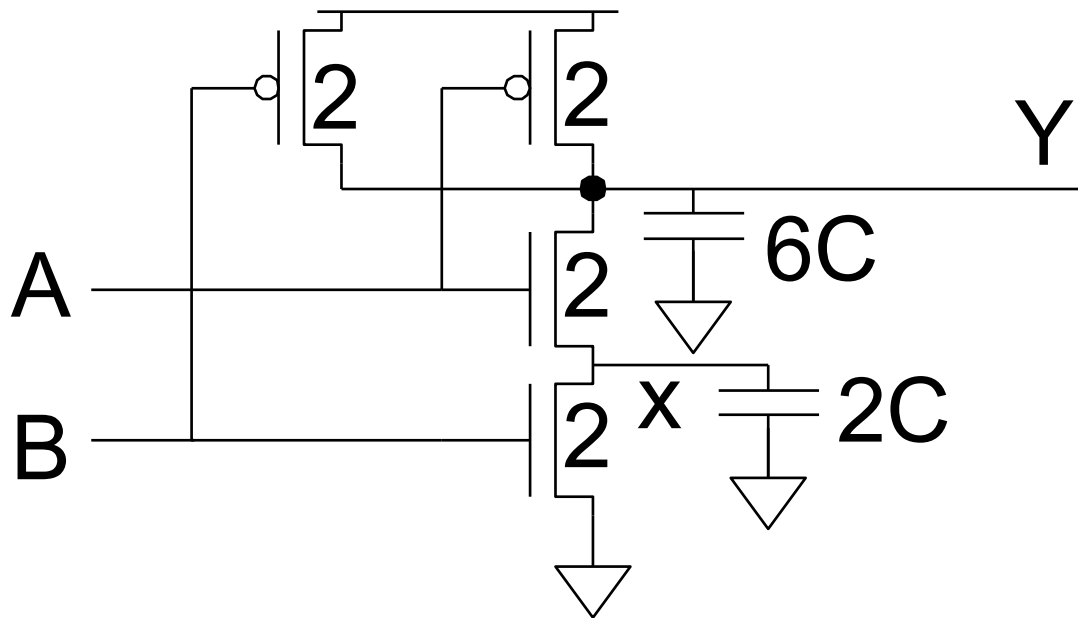
# Input Order Matters

- **Our parasitic delay model was too simple**
  - Calculate parasitic delay for Y falling
    - If A arrives latest?
      - $2\tau$
    - If B arrives latest?
      - $2.33\tau$


 
# Inner & Outer Inputs



- *Outer* input is closest to rail (B)
- *Inner* input is closest to output (A)



- **If input arrival time is known**
  - Connect latest input to inner terminal
  
# Asymmetric Gates


- **Asymmetric gates favor one input over another**
- **Example: Suppose input A of a NAND gate is most critical**
  - Use smaller transistor on A (less capacitance)
  - Boost size of noncritical input
  - So total resistance is same





# Symmetric Gates


- Inputs can be made perfectly symmetric

 


# Skewed Gates

- **Skewed gates favor one edge over another**
- **Ex: suppose rising output of inverter is most critical**
  - **Downsize noncritical NMOS transistor**


HI-skew  
inverter

 

 unskewed inverter  
(equal rise resistance)



 unskewed inverter  
(equal fall resistance)



# HI- and LO-Skew

---

- Logical effort of a skewed gate for a particular transition is the ratio of the input capacitance of that gate to the input capacitance of an unskewed inverter delivering the same output current for the same transition
- **Skewed gates reduce size of noncritical transistors**
  - HI-skew gates favor rising output (small nMOS)
  - LO-skew gates favor falling output (small pMOS)
- **Logical effort is smaller for favored direction**
- **But larger for the other direction**




# Catalog of Skewed Gates

Inverter




NAND2

NOR2




unskewed

   

HI-skew

  
 


LO-skew

   

  
# Asymmetric Skew

- **Combine asymmetric and skewed gates**
  - Downsize noncritical transistor on unimportant input
  - Reduces parasitic delay for critical input


 
# Best P/N Ratio

- We have selected P/N ratio for equivalent rise and fall resistance
  - ( $\mu = 2-3$  for an inverter).
- Alternative: choose ratio for least average delay
- Ex: inverter
  - Delay driving identical inverter
  - $t_{pdf} = (P+1)$
  - $t_{pdr} = (P+1)(\mu/P)$
  - $t_{pd} = (P+1)(1+\mu/P)/2 = (P + 1 + \mu + \mu/P)/2$
  - Differentiate  $t_{pd}$  w.r.t.  $P$
  - Least delay for  $P = \sqrt{\mu}$




# P/N Ratios


- In general, best P/N ratio is square root of that giving equal delay
  - Only improves average delay slightly for inverters
  - But significantly decreases area and power

Inverter


fastest  
P/N ratio

 

NAND2

 

NOR2

 

# Device Sizing

---

- **Device sizing is one of the key techniques for circuit optimization**
  - **For standard cell type of designs, gate sizing**
    - **For example of inverters, INV-A, INV-B, INV-C, ..., INV-N, ..., each having a different driving capabilities.**
  - **For microprocessor or custom designs, more fine-grained control, transistor sizing**
    - **For each transistor**



# Driver Sizing


## ■ Given:

- A chain of cascaded drivers driving a load
- Ignore the interconnect between drivers (i.e. assume driver and load CL is closer enough)

## ■ Obtain:


- Optimize the driver sizes to minimize delay, or minimize total area while meeting target delay

## ■ Delay and area/power tradeoff

 

# Driver Sizing using stage ratios

---

 


**Constant stage ratio:**  $\frac{D_{i+1}}{D_i} = \left(\frac{C_L}{C_g}\right)^{1/k}$

**where**  $\frac{D_{i+1}}{D_i} \approx e$  (i.e. 2.78)

**We will use 3-4 in this class**




# Stage ratio example

---

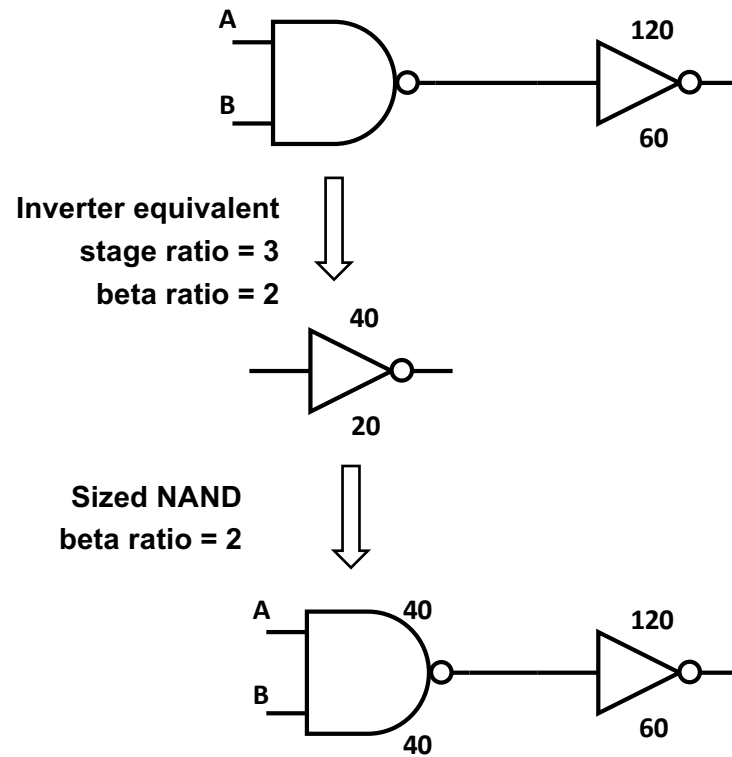
   
# Sizing example


- **Size these three circuits.**
  - Load on node Y: 40/20 inverter
  - Use stage ratio of 4
  - Use beta ratio of 2



## Stage ratio example HW #3

Use stage ratio of 3

Use beta ratio of 2

 

---

## **Backup: Logical Effort**

# Introduction

---

- **Chip designers face a plethora of choices**
  - What is the best circuit topology for a function?
  - How many stages of logic give least delay?
  - How wide should the transistors be?
- **Logical effort is one method to make these decisions**
  - Uses a simple model of delay
  - Allows back-of-the-envelope calculations
  - Helps make rapid comparisons between alternatives
  - Emphasizes remarkable symmetries

# Example


## ■ Design the decoder for a register file.

### Decoder specifications:

- 16 word register file
- Each word is 32 bits wide
- Each bit presents load of 3 unit-sized transistors
- True and complementary address inputs  $A[3:0]$
- Each input may drive 10 unit-sized transistors
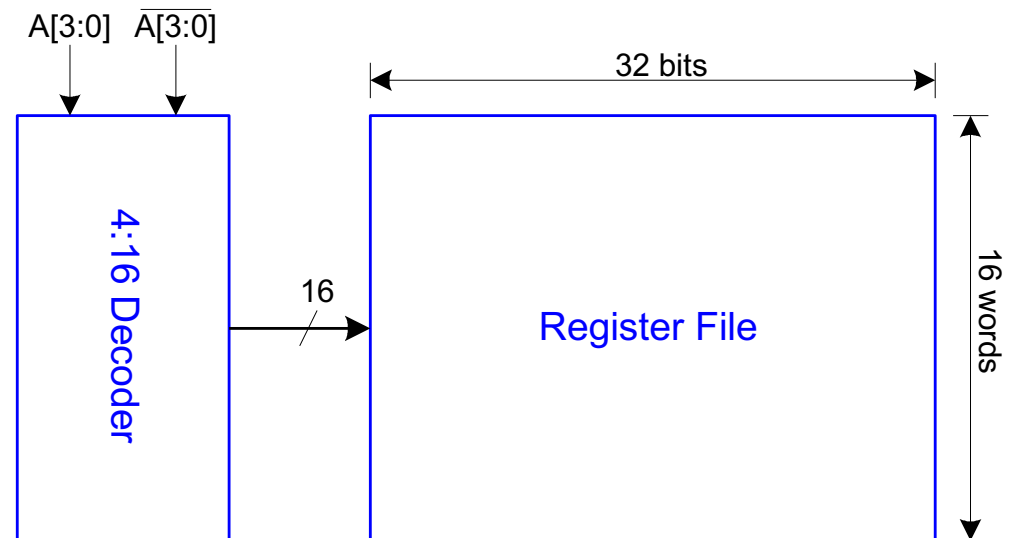
## ■ Need to decide:

- How many stages to use?
- How large should each gate be?
- How fast can decoder operate?





# Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

$$\tau = 3RC$$

$\approx$  12 ps in 180 nm process

3 ps in 65nm  $\mu$ m process

- Delay has two components:  $d = f + p$
- Effort delay  $f = gh$  (a.k.a. stage effort)

$g$ : logical effort

Measures relative ability of gate  
to deliver current  
 $g = 1$  for inverter

$h$ : electrical effort =  $C_{out} / C_{in}$


Ratio of output to input caps.  
Sometimes called fanout effort

- Parasitic delay  $p$ 
  - Represents “intrinsic” delay of gate driving no load
  - Set by internal parasitic capacitance

# Delay Plots

$$d = f + p$$


$$d = gh + p$$

 


**What about a NOR2?**
 
# Computing Logical Effort


- *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current*
- **Measure from delay vs. fanout plots**
- **Or estimate by counting transistor widths**



$$C_{in} = 3$$
$$g = 3/3$$

 

$$C_{in} = 4$$
$$g = 4/3$$

 


$$C_{in} = 5$$
$$g = 5/3$$

# Computing Logical Effort for a NAND2 Gate

Recall that  $\text{delay} = t_{pd}/\tau$  and  $\tau \approx 3RC$

For the 2-NAND gate below

 


The 'rising' propagation delay is:  $t_{pdr} = (6 + 4h)RC$

Therefore  $d = t_{pd}/\tau = (6 + 4h)RC/3RC = 4/3h + 2$

Recall  $d = gh + p$  therefore  $g=4/3$
 
## Computing Logical Effort for a NAND2 Gate (cont)

The logical effort for the 'falling' signal is the same, however the intrinsic delay is not.



$$t_{pdf} = (2C)\left(\frac{R}{2}\right) + \left[(6 + 4h)C\right]\left(\frac{R}{2} + \frac{R}{2}\right)$$

$$= (7 + 4h)RC$$

**Where**  $d = t_{pd}/\tau = (7 + 4h)RC/3RC = 4/3h + 7/3$

# Catalog of Gates

---

## Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		$4/3$	$5/3$	$6/3$	$(n+2)/3$
NOR		$5/3$	$7/3$	$9/3$	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	

# Catalog of Gates


---

- **Parasitic (intrinsic) delay of common gates**
  - In multiples of  $p_{inv}$  ( $\approx 1$ )

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	
 
## Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



**Logical Effort:**  $g = 1$

**Electrical Effort:**  $h = 1$

**Parasitic Delay:**  $p = 1$

**Stage Delay:**  $d = 2$

**Frequency:**  $f_{osc} = 1 / (2 * N * d) = 1 / 4N$

31 stage ring oscillator in  
0.6  $\mu\text{m}$  process has  
frequency of  $\sim 200$  MHz

***Recall that the signal has to propagate through the inverter chain twice to make a complete waveform***



# Example: FO4 Inverter


- Estimate the delay of a fanout-of-4 (FO4) inverter

**Logical Effort:**  $g = 1$

**Electrical Effort:**  $h = 4$

**Parasitic Delay:**  $p = 1$

**Stage Delay:**  $d = 5$

 

The FO4 delay is about

200 ps in 0.6  $\mu\text{m}$  process

60 ps in a 180 nm process

$f/3$  ns in an  $f$   $\mu\text{m}$  process

( $f/3$  ps in an  $f$  nm process)


# Multistage Logic Networks

- Logical effort generalizes to multistage networks

*Path Logical Effort*  $\rightarrow G = \prod g_i$

*Path Electrical Effort*  $\rightarrow H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

 *Path Effort*  $\rightarrow F = \prod f_i = \prod g_i h_i$



- Can we write  $F = GH$  in general?

# Paths that Branch

- No! Consider paths that branch:

$$G = 1$$


$$H = 90 / 5 = 18$$

$$GH = 18$$

$$h_1 = (15 + 15) / 5 = 6$$

$$h_2 = 90 / 15 = 6$$

$$F = g_1 g_2 h_1 h_2 = 36 = 2GH$$

 

# Branching Effort

---

- Introduce *branching effort*
  - Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- We compute the path effort
  - $F = GBH$

# Multistage Delays

---

- **Path Effort Delay**

$$D_F = \sum f_i$$

- **Path Parasitic Delay**

$$P = \sum p_i$$

- **Path Delay**

$$D = \sum d_i = D_F + P$$

# Designing Fast Circuits

---

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is

$$D = NF^{\frac{1}{N}} + P$$

- This is a **key** result of logical effort
  - Find fastest possible delay
  - Doesn't require calculating gate sizes

# Gate Sizes

---

- How wide should the gates be for least delay?


$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$

$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives
- Check work by verifying input cap spec is met

 
## Example: 3-stage path

- Select gate sizes  $x$  and  $y$  for least delay from  $A$  to  $B$





## Example: 3-stage path

 

**Logical Effort**

$$G = (4/3) * (5/3) * (5/3) = 100/27$$

**Electrical Effort**

$$H = 45/8$$

**Branching Effort**

$$B = 3 * 2 = 6$$

**Path Effort**

$$F = GBH = 125$$

**Best Stage Effort**

$$\hat{f} = \sqrt[3]{F} = 5$$

**Parasitic Delay**

$$P = 2 + 3 + 2 = 7$$

**Delay**


$$D = 3 * 5 + 7 = 22 = 4.4 \text{ FO4}$$

## Example: 3-stage path

- Work backward for sizes

$$y = 45 * (5/3) / 5 = 15$$


$$x = (15 * 2) * (5/3) / 5 = 10$$

 
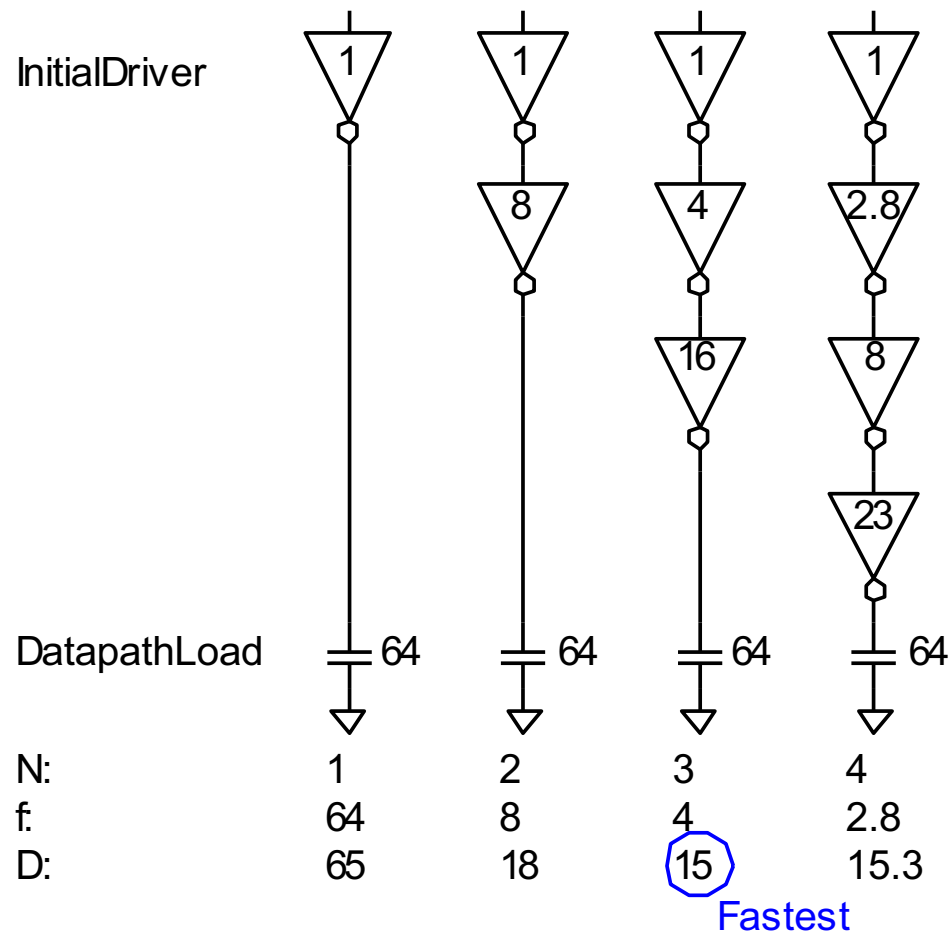
# Best Number of Stages


- How many stages should a path use?
  - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

$$D = NF^{1/N} + P$$
$$= N(64)^{1/N} + N$$



# Derivation

- **Consider adding inverters to end of path**
  - How many give least delay?
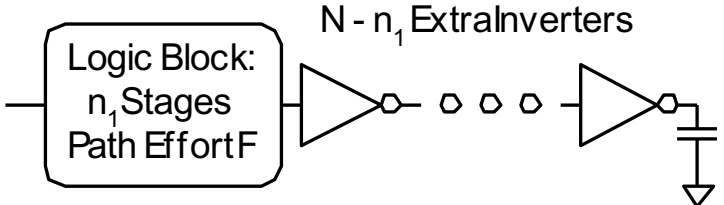
$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$


The diagram illustrates a digital circuit path. It begins with a rectangular block labeled "Logic Block: n<sub>1</sub> Stages Path Effort F". This block is connected to a series of inverters. The first inverter is shown in detail, followed by three small circles representing intermediate inverters, and then another detailed inverter. The entire chain of inverters is labeled "N - n<sub>1</sub> Extra Inverters" above them. The final output of the inverters is connected to a ground symbol.

- **Define best stage effort**  $\rho = F^{\frac{1}{N}}$

$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

$$p_{inv} + \rho(1 - \ln \rho) = 0$$


## Best Stage Effort

---

- $p_{inv} + \rho(1 - \ln \rho) = 0$  has no closed-form solution
- Neglecting parasitics ( $p_{inv} = 0$ ), we find  $\rho = 2.718$  (e)
- For  $p_{inv} = 1$ , solve numerically for  $\rho = 3.59$
 
# Sensitivity Analysis

- How sensitive is delay to using exactly the best number of stages?



- $2.4 < \rho < 6$  gives delay within 15% of optimal
  - We can be sloppy!
  - For example, use  $\rho = 4$

# Let's revisit the decoder specifications


## ■ Design the decoder for a register file.

### Decoder specifications:

- 16 word register file
- Each word is 32 bits wide
- Each bit presents load of 3 unit-sized transistors
- True and complementary address inputs  $A[3:0]$
- Each input may drive 10 unit-sized transistors
 
## ■ Need to decide:

- How many stages to use?
- How large should each gate be?
- How fast can decoder operate?



## Decoder Ex: Number of Stages

---

- **Decoder effort is mainly electrical and branching**

**Electrical Effort:**  $H = (32 * 3) / 10 = 9.6$

**Branching Effort:**  $B = 8$

- **If we neglect logical effort (assume  $G = 1$ )**

**Path Effort:**  $F = GBH = 76.8$

**Number of Stages:**  $N = \log_4 F = 3.1$

- **Try a 3-stage design based on rough estimation**



# Decoder: Gate Sizes & Delay


**Logical Effort:**  $G = 1 * 6/3 * 1 = 2$  (not an estimation)

**Path Effort:**  $F = GBH = 154$

**Stage Effort:**  $\hat{f} = F^{1/3} = 5.36$

**Path Delay:**  $D = 3\hat{f} + 1 + 4 + 1 = 22.1$

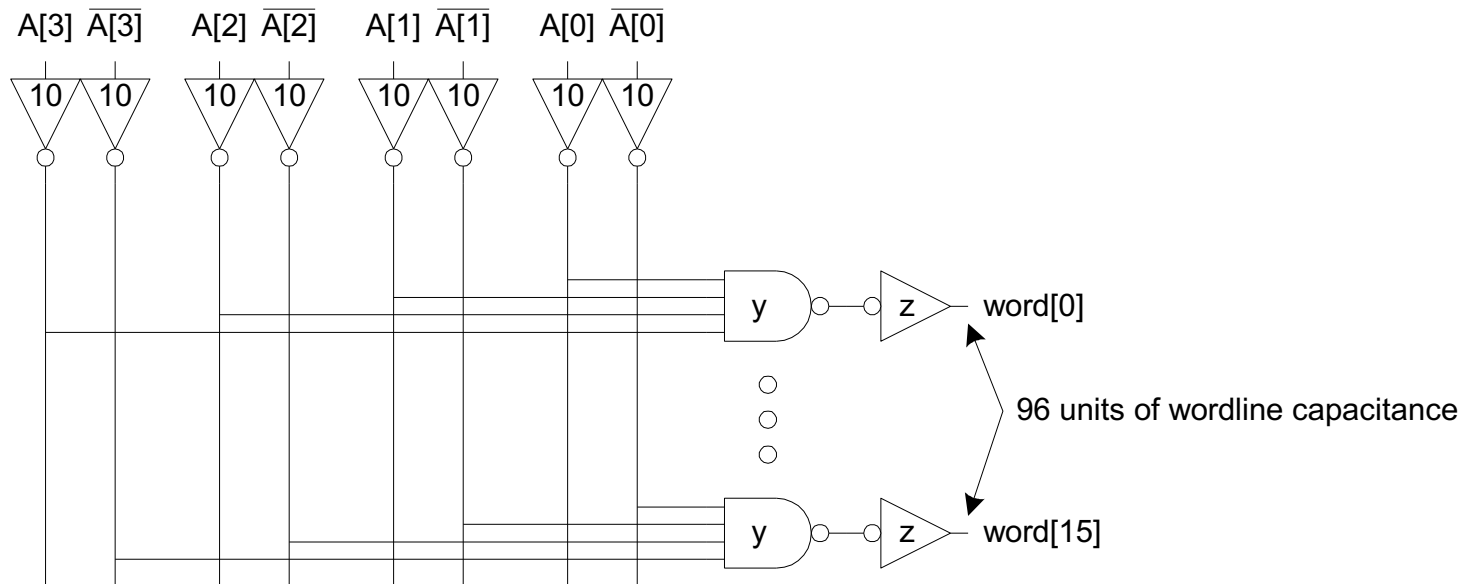**Gate sizes:**  $z = 96 * 1/5.36 = 18;$   $y = 18 * 2/5.36 = 6.7$



# Decoder: Comparison

---

Compare many alternatives with a spreadsheet

Design	N	G	P	D
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

# Review of Definitions

Term	Stage	Path
number of stages	1	$N$
logical effort	$g$	$G = \prod g_i$
electrical effort	$h = \frac{C_{out}}{C_{in}}$	$H = \frac{C_{out-path}}{C_{in-path}}$
branching effort	$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	$f$	$D_F = \sum f_i$
parasitic delay	$p$	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$

# Logical Effort Methodology Summary

---

- **Compute path effort**  $F = GBH$
- **Estimate best number of stages**  $N = \log_4 F$
- **Sketch path with N stages**
- **Estimate least delay**  $D = NF^{\frac{1}{N}} + P$
- **Determine best stage effort**  $\hat{f} = F^{\frac{1}{N}}$
- **Find gate sizes**  $C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$

# Limits of Logical Effort

---

- **Chicken and egg problem**
  - Need path to compute  $G$
  - But don't know number of stages without  $G$
- **Simplistic delay model**
  - Neglects input rise time effects
- **Interconnect**
  - Iteration required in designs with wire
- **Maximum speed only**
  - Not minimum area/power for constrained delay

# Summary

---

- **Logical effort is useful for thinking of delay in circuits**
  - Numeric logical effort characterizes gates
  - NANDs are faster than NORs in CMOS
  - Paths are fastest when effort delays are  $\sim 4$
  - Path delay is weakly sensitive to stages, sizes
  - But using fewer stages doesn't mean faster paths
  - Delay of path is about  $\log_4 F$  FO4 inverter delays
  - Inverters and NAND2 best for driving large caps
- **Provides language for discussing fast circuits**
  - But requires practice to master







