 


9/8/25

(1)





CATS

0, 1




p-type

n-type

  


9/8/25

(2)

   


IN	OUT
0	1
1	0

INVERTER
NOT-gate

 


9/8/25

③

 

A	B	OUT
0	0	1
0	1	1
1	0	1
1	1	0

NAND-AND
NAND

 





AND GATES

A	B	OUT
0	0	0
0	1	0
1	0	0
1	1	1


TRANSMISSION
VOLTAGES

9/8/25

(4)

    

DECODE

 


01

10



11

0001
1010

 


9/8/25
(5)

3/.


 
 


↑↑↑
Source

 


9/8/25

(6)

   

ONE
BIT
ADDRESS

FULL
ADDRESS

 

A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1