

VLSI I

Spring 2009 (Prof. David Pan)

Homework #8: Due May 7 in class

(this is an optional Homework, which will replace the lowest homework 1-7)

1. Problem 3.1 from the Exercises for Chapter 3 (page 154).
2. Problem 12.1 from the Exercises for Chapter 12 (page 845).
3. Find a test vector for the node N stuck-at-0 in the circuit below.

